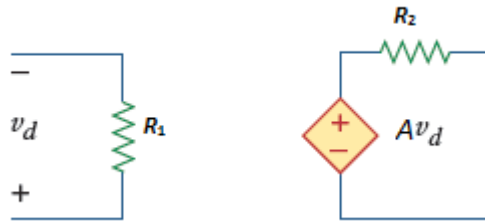


The equivalent model of a certain op amp is shown in the figure given below, where $R_1 = 2.8 \text{ M}\Omega$, $R_2 = 39 \text{ }\Omega$, and $A = 10 \times 10^4$.



References

Section Break

Difficulty: Easy

Learning Objective: Understand how real operational amplifiers (op amps) function.

1.Award: **10.00 points**

Calculate the input resistance of the given circuit.

The input resistance of the circuit is MΩ.

Explanation:

The input resistance is the Thevenin equivalent resistance seen at the input terminals, that is $R_{in} = 2.8$ MΩ.

The input resistance of the circuit is 2.8 MΩ.

Hints[Hint #1](#)**References****Worksheet**

Difficulty: Easy

Learning Objective: Understand how real operational amplifiers (op amps) function.

2.Award: **10.00 points**

Calculate the output resistance of the given circuit.

The output resistance of the given circuit is Ω.

Explanation:

The output resistance is the Thevenin equivalent resistance seen at the output terminals, that is $R_{\text{out}} = 39 \Omega$.

The output resistance of the given circuit is 39 Ω.

Hints[Hint #1](#)**References****Worksheet**

Difficulty: Easy

Learning Objective: Understand how real operational amplifiers (op amps) function.

3.

Award: 10.00 points

The open-loop gain of an op amp is 75000. Calculate the output voltage when there are inputs of +10 μV on the inverting terminal and +20 μV on the noninverting terminal.

The output voltage is mV.

Explanation:

The output voltage is calculated as follows:

$$v_o = A v_d = A(v_2 - v_1) = 75000 \times (20 \mu\text{V} - 10 \mu\text{V}) = 750 \text{ mV}$$

The output voltage is 750 mV.

Hints[Hint #1](#)**References****Worksheet**

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

4.Award: **10.00 points**

The output voltage of an op amp is -1 V when the noninverting input is 1 mV. If the open-loop gain of the op amp is 2×10^6 , what is the inverting input?

The inverting input of the op amp is mV.

Explanation:

The inverting input of the op amp is calculated as follows:

$$v_0 = Av_d = A(v_2 - v_1)$$

$$v_2 - v_1 = \frac{v_0}{A} = \frac{-1}{2 \times 10^6} = -0.50 \mu\text{V}$$

$$v_2 - v_1 = -0.50 \mu\text{V} = -0.000 \text{ mV}$$

$$1 \text{ mV} - v_1 = -0.000 \text{ mV}$$

$$v_1 = 1 \text{ mV} - (-0.000) = 1.000 \text{ mV}$$

The inverting input of the op amp is 1.000 mV.

Hints[Hint #1](#)**References****Worksheet**


Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

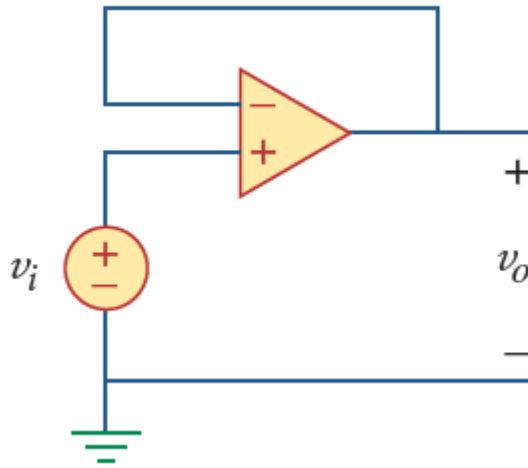5.

Award: 10.00 points


For the op amp circuit given below, the op amp has an open-loop gain of 90000, an input resistance of 14 k Ω , and an output resistance of 115 Ω . Find the voltage gain v_o/v_i using the nonideal model of the op amp.



The voltage gain v_o/v_i of the op amp is .

Explanation:

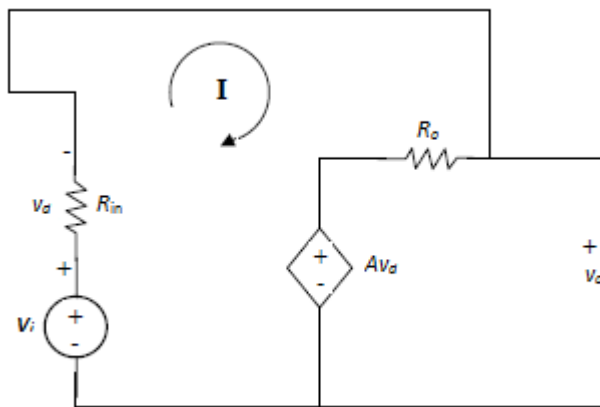The formula to find the voltage gain is derived as follows:



$$-v_i + Av_d + (R_i + R_o)I = 0$$

$$\text{But } v_d = R_i I$$

$$-v_i + (R_i + R_o + R_i A) I = 0$$

$$I = \frac{v_i}{R_o + (1 + A)R_i}$$

$$-Av_d - R_o I + v_o = 0$$

$$v_o = Av_d + R_o I = (R_o + R_i A) I = \frac{(R_o + R_i A)v_i}{R_o + (1 + A)R_i}$$

The voltage gain is calculated as follows:

$$\frac{v_o}{v_i} = \frac{R_o + R_i A}{R_o + (1 + A)R_i} = \frac{115\Omega + (14\text{ k}\Omega \times 90000)}{115\Omega + ((1 + 90000) \times 14\text{ k}\Omega)} = 0.999989$$

The voltage gain is 0.999989.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

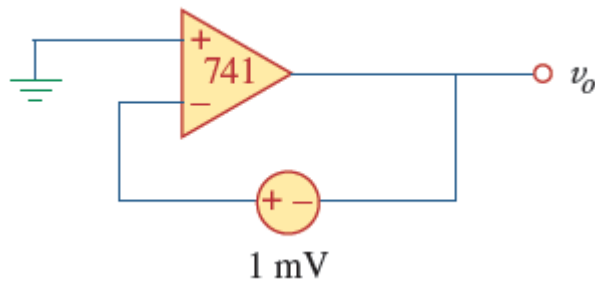6.

Award: 10.00 points


A 741 op amp shown in the circuit given below has an open-loop voltage gain of 80000, an input resistance of $2\text{ M}\Omega$, and an output resistance of $110\ \Omega$. Calculate the output voltage v_o in the op amp circuit.



The output voltage of the op amp is mV.

Explanation:

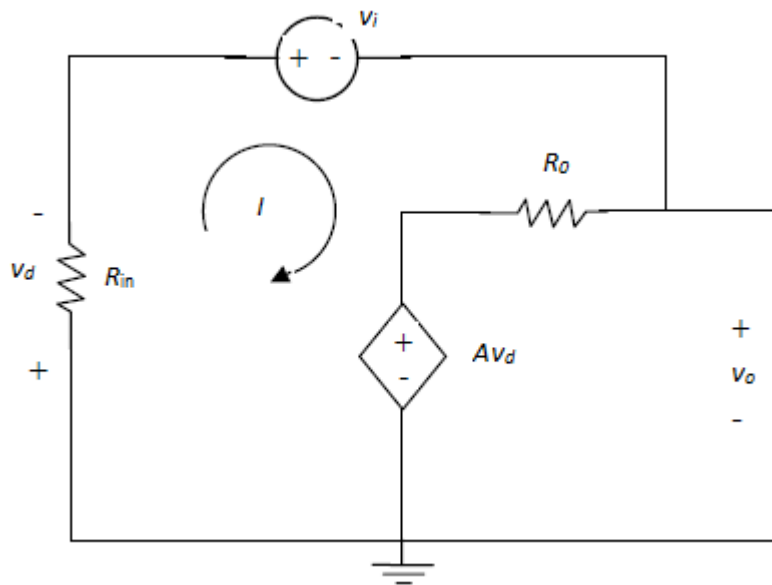The formula to find the output voltage is derived as follows:



$$(R_o + R_i)I + v_i + Av_d = 0$$

$$\text{But } v_d = R_i I$$

$$v_i + (R_o + R_i + R_i A)I = 0$$

$$I = \frac{-v_i}{R_o + (1 + A)R_i} \quad (1)$$

$$-Av_d - R_o I + v_o = 0$$

$$v_o = Av_d + R_o I = (R_o + R_i A)I$$

Substituting for I in equation (1),

$$v_o = - \left(\frac{R_o + R_i A}{R_o + (1 + A)R_i} \right) v_i$$

Then, the output voltage is calculated as follows:

$$v_o = - \left(\frac{R_o + R_i A}{R_o + (1 + A) R_i} \right) v_i$$

$$v_o = - \left(\frac{110 \Omega + (2 \text{ M}\Omega \times 80000)}{110 \Omega + (1 + 80000) \times 2 \text{ M}\Omega} \right) \times 1 \text{ mV}$$

$$v_o = - 0.999988 \text{ mV}$$

The output voltage is - 0.999988 mV.

Hints

[Hint #1](#)


References

Worksheet

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

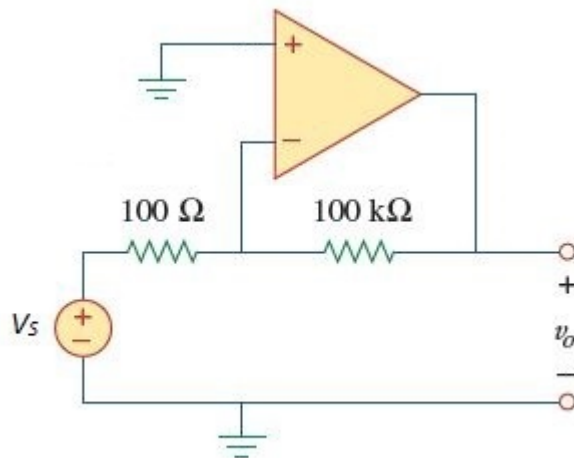The op amp in the circuit given below has $R_i = 100 \text{ k}\Omega$, $R_o = 100 \Omega$, $v_s = 1 \text{ mV}$, and $A = 100,000$.



References

Section Break

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.


7.

Award: 10.00 points

Calculate the output voltage v_o for the given op amp circuit.

The output voltage v_o for the given op amp circuit is mV.

Explanation:

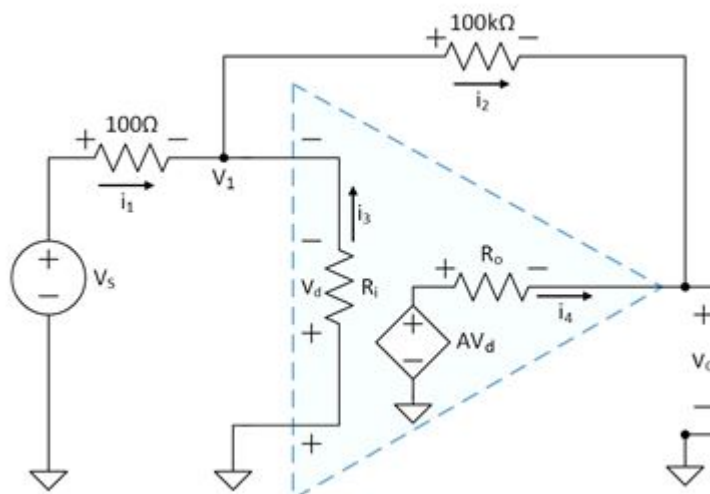

At node V_1 , $i_1 - i_2 + i_3 = 0\text{A}$

$$\frac{V_s - V_1}{100\Omega} - \frac{V_1 - V_o}{100\text{k}\Omega} + \frac{-V_1}{R_i} = 0\text{A}$$

which leads to $V_1 = \frac{1000V_s + V_o}{1002}$

At node V_o , $i_2 + i_4 = 0\text{A}$

$$\frac{V_1 - V_o}{100\text{k}\Omega} + \frac{AV_d - V_o}{R_o} = 0\text{A}$$

But, $V_d = -V_1$ and $A = 100,000$ so

$$V_1 - V_o + 1000(-100,000V_1 - V_o) = 0$$

$$V_o = \frac{-99,999,999}{1001} V_1 = \frac{-99,999,999}{1001} \left[\frac{1000V_s + V_o}{1002} \right]$$

This gives us $\frac{V_o}{V_s} = -990.07$

If $V_s = 1\text{ mV}$, then $V_o = -0.9901\text{ mV}$

The output voltage v_o for the given op amp circuit is -0.9901 mV .

Hints

[Hint #1](#)

References

Worksheet

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

8.

Award: 10.00 points

Calculate the differential voltage v_d .

The differential voltage v_d is nV.

Explanation:

The differential voltage is calculated as follows:

$$v_0 = A v_d = 100,000 v_d$$

$$\text{Then, } v_d = -\frac{v_o}{10^5} = -\frac{-0.99 \text{ mV}}{10^5} = -9.90 \text{ nV}$$

The differential voltage v_d is -9.90 nV .

Hints

[Hint #1](#)

References

Worksheet

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.


9.

Award: 10.00 points

Calculate the output voltage v_o for the given op amp circuit.

The output voltage v_o for the given op amp circuit is mV.

Explanation:

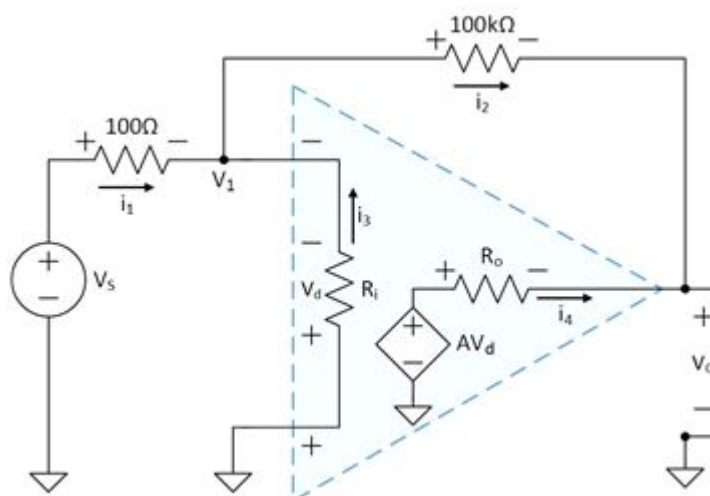

At node V_1 , $i_1 - i_2 + i_3 = 0\text{A}$

$$\frac{V_s - V_1}{100\Omega} - \frac{V_1 - V_o}{100\text{k}\Omega} + \frac{-V_1}{R_i} = 0\text{A}$$

which leads to $V_1 = \frac{1000V_s + V_o}{1002}$

At node V_o , $i_2 + i_4 = 0\text{A}$

$$\frac{V_1 - V_o}{100\text{k}\Omega} + \frac{AV_d - V_o}{R_o} = 0\text{A}$$

But, $V_d = -V_1$ and $A = 100,000$ so

$$V_1 - V_o + 1000(-100,000V_1 - V_o) = 0$$

$$V_o = \frac{-99,999,999}{1001} V_1 = \frac{-99,999,999}{1001} \left[\frac{1000V_s + V_o}{1002} \right]$$

This gives us $\frac{V_o}{V_s} = -990.07$

If $V_s = 1\text{ mV}$, then $V_o = -0.9901\text{ mV}$

The output voltage v_o for the given op amp circuit is -0.9901 mV .

Hints

[Hint #1](#)

References

Worksheet

Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

10.

Award: 10.00 points

Calculate the differential voltage v_d .

The differential voltage v_d is nV.

Explanation:

The differential voltage is calculated as follows:

$$v_0 = A v_d = 100,000 v_d$$

$$\text{Then, } v_d = -\frac{v_o}{10^5} = -\frac{-0.99 \text{ mV}}{10^5} = -9.90 \text{ nV}$$

The differential voltage v_d is -9.90 nV .

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Medium

Learning Objective: Understand how real operational amplifiers (op amps) function.

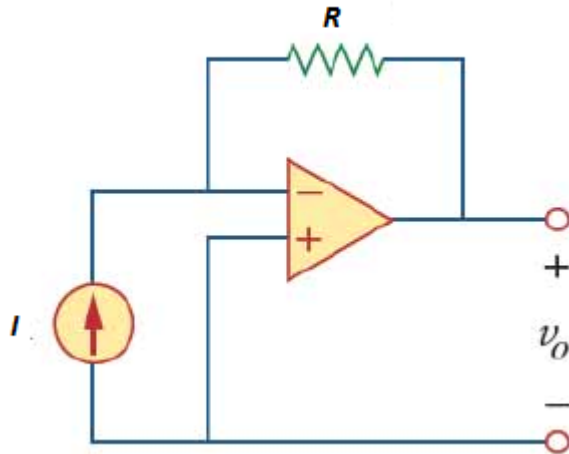11.

Award: 10.00 points

Calculate the output voltage v_o for the op amp circuit given below, where $I = 1 \text{ mA}$ and $R = 3 \text{ k}\Omega$. (Assume ideal op amp)



The output voltage v_o for the given op amp circuit is V.

Explanation:

If v_a and v_b are the voltages at the inverting terminal and noninverting terminals of the op amp,

$$v_a = v_b = 0$$

$$1 \text{ mA} = \frac{0 - v_o}{3 \text{ k}\Omega}$$

$$v_o = -3.00 \text{ V}$$

The output voltage v_o for the given op amp circuit is - 3.00 V.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Easy

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

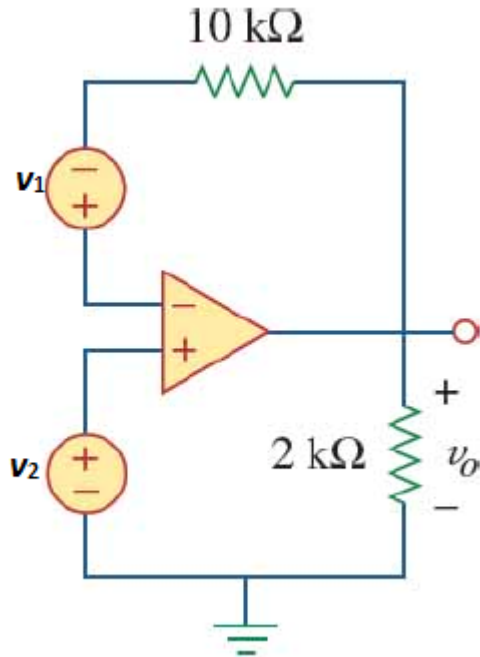12.

Award: 10.00 points

Calculate the output voltage of the op amp circuit given below, where $v_1 = 2.3 \text{ V}$ and $v_2 = 1.5 \text{ V}$.



The output voltage of the op amp circuit is V.

Explanation:

The output voltage is calculated as follows:

Since $v_a = v_b = 1.5 \text{ V}$ and $i_a = 0$, no current flows through the 10-kΩ resistance.

Using the compensatory circuit concept, from the given figure we get, $-v_a + 2.3 + v_o = 0$.

$$v_o = v_a - 2.3 = 1.5 \text{ V} - 2.3 \text{ V} = -0.8 \text{ V}$$

The output voltage of the op amp circuit is - 0.8 V.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Easy

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

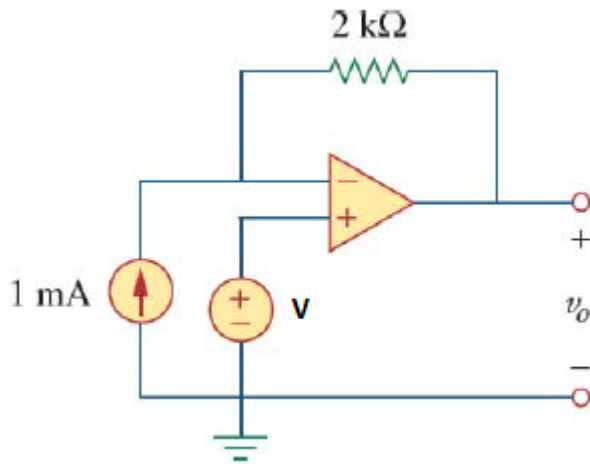13.

Award: 10.00 points

Find the output voltage v_o for the op amp circuit given below, where $V = 11$ V.



The output voltage v_o for the given op amp circuit is V.

Explanation:

Let v_a and v_b be respectively the voltages at the inverting and the noninverting terminals of the op amp.

$$v_a = v_b = 11 \text{ V}$$

At the inverting terminal,

$$1 \text{ mA} = \frac{11 \text{ V} - v_o}{2 \text{ k}\Omega}$$

$$v_o = 9 \text{ V}$$

The output voltage v_o for the given op amp circuit is 9 V.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Easy

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

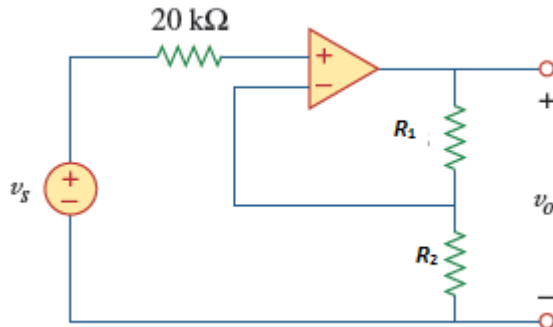14.

Award: 10.00 points

Find the voltage gain v_o/v_s of the circuit given below, where $R_1 = 17 \text{ k}\Omega$ and $R_2 = 14 \text{ k}\Omega$.



The voltage gain v_o/v_s of the circuit is .

Explanation:

Since no current enters the op amp, the voltage at the input of the op amp is v_s .

Hence,

$$v_s = v_o \left(\frac{14 \text{ k}\Omega}{17 \text{ k}\Omega + 14 \text{ k}\Omega} \right)$$

$$\frac{v_o}{v_s} = 2.21$$

The gain v_o/v_s of the circuit is 2.21.

Hints

[Hint #1](#)

References**Worksheet**


Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

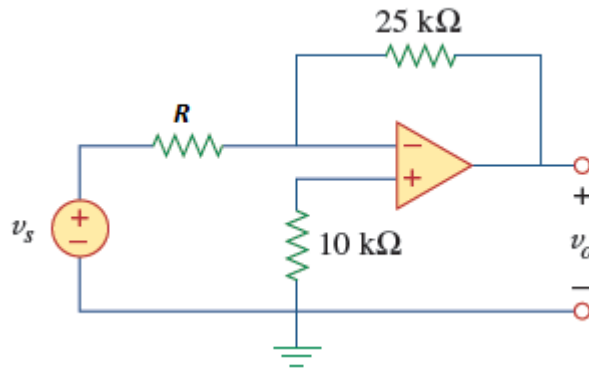15.

Award: 10.00 points


Calculate the voltage ratio v_o/v_s for the op amp circuit given below, where $R = 11 \text{ k}\Omega$. Assume that the op amp is ideal.



The voltage ratio v_o/v_s for the op amp circuit is .

Explanation:

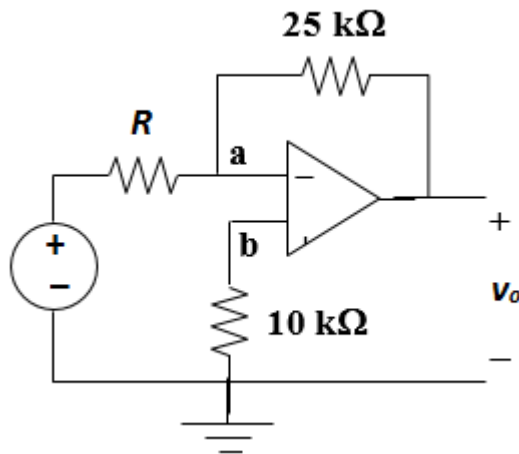Step 1: Label the unknown nodes in the op amp circuit. Next we write the node equations and then apply the constraint $v_a = v_b$. Finally, solve for v_o in terms of v_s .



Step 2:

$$\frac{v_a - v_s}{11 \text{ k}\Omega} + \frac{v_a - v_o}{25 \text{ k}\Omega} + 0 = 0 \quad \text{and} \quad \frac{v_b - 0}{10 \text{ k}\Omega} + 0 = 0 \quad \text{or} \quad v_b = 0 = v_a$$

$$\text{Thus,} \quad \frac{-v_s}{11 \text{ k}\Omega} + \frac{-v_o}{25 \text{ k}\Omega} = 0$$

or

$$v_o = \frac{-25 \text{ k}\Omega}{11 \text{ k}\Omega} v_s$$

or

$$v_o/v_s = -2.27$$

The voltage ratio v_o/v_s is -2.27.

Hints

[Hint #1](#)


References

Worksheet

Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

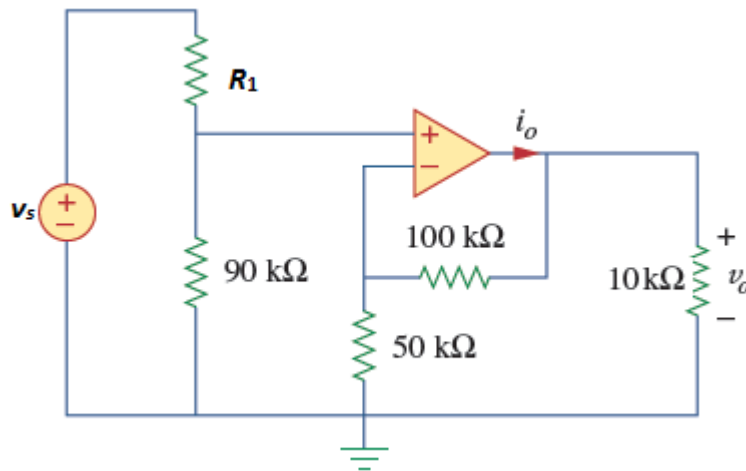Consider the op amp circuit given below, where $R_1 = 19 \text{ k}\Omega$ and $v_s = 1 \text{ V}$.



References

Section Break

Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.


16.

Award: 10.00 points

Calculate the output voltage v_o for the given circuit.

The output voltage v_o is V.

Explanation:

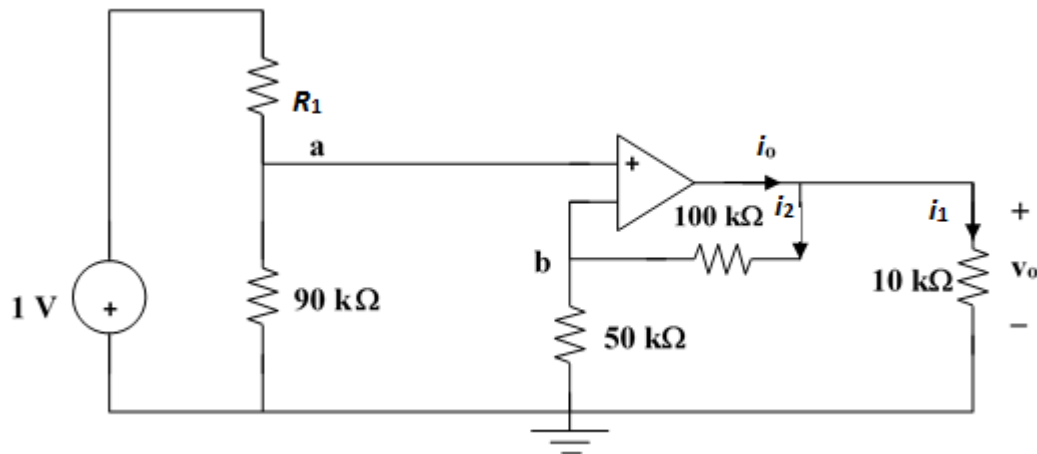

By voltage division,

$$v_a = \frac{90 \text{ k}\Omega}{90 \text{ k}\Omega + 19 \text{ k}\Omega} \times 1 \text{ V} = 0.83 \text{ V}$$

$$v_b = \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 100 \text{ k}\Omega} = \frac{v_o}{3}$$

$$\text{But } v_a = v_b \rightarrow \frac{v_o}{3} = 0.83 \text{ V}$$

$$v_o = 2.48 \text{ V}$$

The output voltage v_o is 2.48 V.

Hints

[Hint #1](#)

References

Worksheet

Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

17.

Award: 10.00 points

Calculate the output current in the circuit.

The output current in the circuit is μA .

Explanation:

The output current is calculated as follows:

$$i_o = i_1 + i_2 = \frac{v_o}{10\text{k}\Omega} + \frac{v_o}{50\text{k}\Omega + 100\text{k}\Omega} = \frac{2.48\text{ V}}{10\text{k}\Omega} + \frac{2.48\text{ V}}{50\text{k}\Omega + 100\text{k}\Omega} = 264.22\ \mu\text{A}$$

The output current in the circuit is 264.22 μA .

Hints[Hint #1](#)**References****Worksheet**


Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

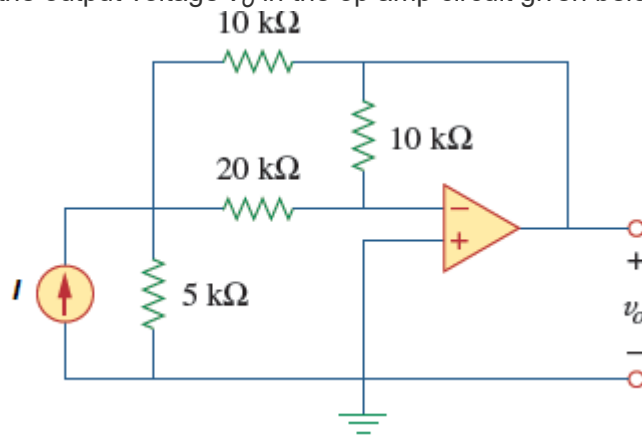18.

Award: 10.00 points


Determine the output voltage v_o in the op amp circuit given below, where $I = 7$ mA.



The output voltage v_o is V.

Explanation:

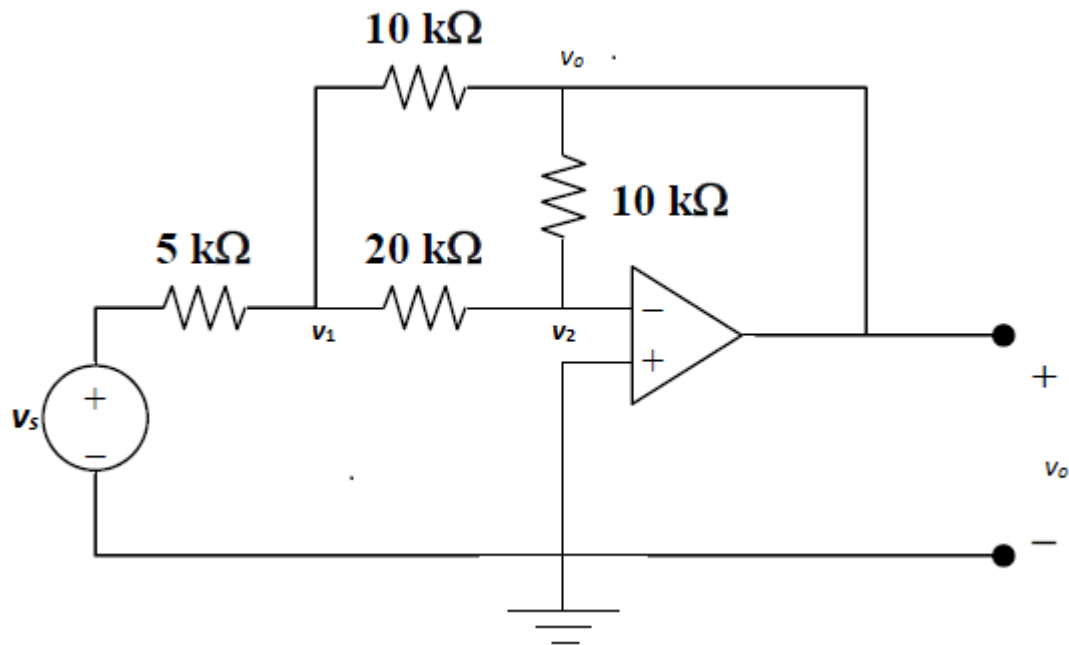The transformation of a current source to a voltage source is shown below, where $v_s = 35$ V.



$$\text{At node 1,} \\ \frac{35 \text{ V} - v_1}{5 \text{ k}\Omega} = \frac{v_1 - v_2}{20 \text{ k}\Omega} + \frac{v_1 - v_o}{10 \text{ k}\Omega}$$

But $v_2 = 0$. Hence, $140 \text{ V} - 4v_1 = v_1 + 2v_1 - 2v_o$

$$140 \text{ V} = 7v_1 - 2v_o \quad \text{----- (1)}$$

$$\text{At node 2, } \frac{v_1 - v_2}{20 \text{ k}\Omega} = \frac{v_2 - v_o}{10 \text{ k}\Omega}, \quad v_2 = 0 \text{ or } v_1 = -2v_o \quad \text{----- (2)}$$

$$\text{From (1) and (2), } 140 = -14v_o - 2v_o$$

$$v_o = -8.75 \text{ V}$$

The output voltage is - 8.75 V.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Medium

Learning Objective: Understand that ideal op amps function nearly identical to real ones and that they can be used to effectively model them in a variety of circuit applications.

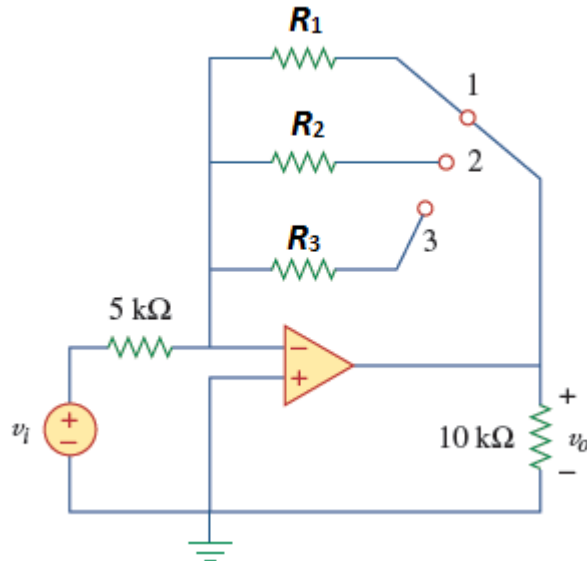19.

Award: 10.00 points

In the circuit given below, $R_1 = 20\text{ k}\Omega$, $R_2 = 66\text{ k}\Omega$, and $R_3 = 2\text{ M}\Omega$. Calculate the gain $\frac{v_o}{v_i}$ when the switch is in position 1, position 2, and position 3.



The gain $\frac{v_o}{v_i}$ at the position 1 is .

The gain $\frac{v_o}{v_i}$ at the position 2 is .

The gain $\frac{v_o}{v_i}$ at the position 3 is .

Explanation:

The gain is calculated as follows:

Position 1:

$$G = \frac{v_o}{v_i} = -\frac{R_f}{R_i} = -\frac{20\text{ k}\Omega}{5\text{ k}\Omega} = -4.0$$

Position 2:

$$G = \frac{v_o}{v_i} = -\frac{66\text{ k}\Omega}{5\text{ k}\Omega} = -13.2$$

Position 3:

$$G = \frac{v_o}{v_i} = -\frac{2\text{ M}\Omega}{5\text{ k}\Omega} = -400$$

The gain $\frac{v_o}{v_i}$ at the position 1 is - 4.0.

The gain $\frac{v_o}{v_i}$ at the position 2 is - 13.2.

The gain $\frac{v_o}{v_i}$ at the position 3 is - 400.

Hints

[Hint #1](#)

References


Worksheet

Difficulty: Medium

Learning Objective: Understand how the basic inverting op amp is the workhorse of the op amp family.

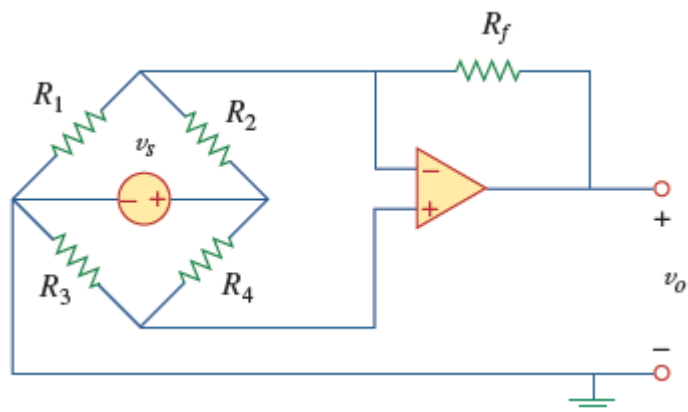20. Award: 10.00 points

In the circuit given below, find k in the voltage transfer function $v_O = kv_S$.



- $k = \left[\left(\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_F} \right) \left(\frac{R_3}{R_3 + R_4} \right) + \frac{1}{R_2} \right]$
 $k = R_f \left(\left(\frac{R_3}{R_1} + \frac{R_3}{R_f} + \frac{R_4}{R_2} \right) \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_1} \right)$
 $k = R_f \left(\left(\frac{R_3}{R_1} - \frac{R_3}{R_f} + \frac{R_4}{R_2} \right) \left(\frac{R_3 + R_4}{R_3} \right) + \frac{1}{R_2} \right)$
 $k = R_F \left[\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_2} \right]$

From the figure, $v_1 = v_2$.

Node 1 is the inverting input and node 2 is the non-inverting input.

Applying KCL at node 1 gives

$$\frac{v_o - v_1}{R_F} = \frac{v_1 - v_s}{R_2} + \frac{v_1}{R_1} \quad \text{-----(1)}$$

Applying KCL at node 2 gives

$$\frac{0 - v_2}{R_3} + \frac{v_s - v_2}{R_4} = 0 \rightarrow v_1 = \frac{R_3}{R_3 + R_4} v_s \quad \text{-----(2)}$$

Substituting (2) into (1) yields

$$\frac{v_o}{R_F} = v_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) - \frac{v_s}{R_2}$$

Therefore,

$$\frac{v_o}{v_s} = k = R_F \left[\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_2} \right]$$

The expression for $k = R_F \left[\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) \left(\frac{R_3}{R_3 + R_4} \right) - \frac{1}{R_2} \right]$

Hints

[Hint #1](#)[Hint #2](#)

References

Multiple Choice

Difficulty: Medium

Learning Objective: Understand how the basic noninverting op amp works and how they can be analyzed in electrical circuit applications.