
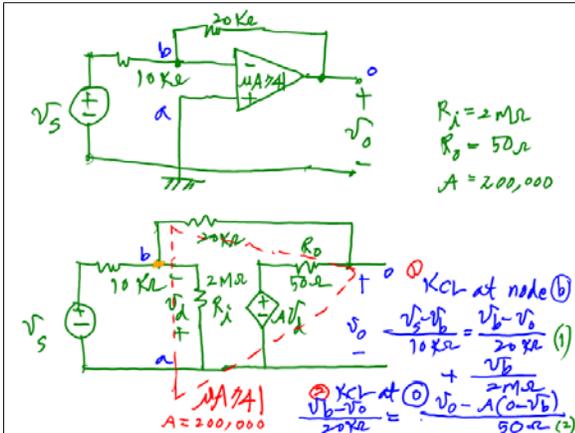


EE101 Lecture 13 Feb 7, 2018
 Op Amps continued

- Midterm Exam on Monday, Feb 12. (There will be 5 problems, covering up to chap 4)
- Ohm's law, KCL, KVL, node & mesh (loop) analyses, Thevenin's & Norton's equivalent ckt's, superposition principle, equivalent calculation (including Δ -Y, Y- Δ transformation), Maximum power transfer.
- office hour on Monday, Feb 12 cannot be held.
- please come to see me at 4 pm. Feb 7 (Friday) if you have any question.
- on Friday, Feb 9 we will review course materials.

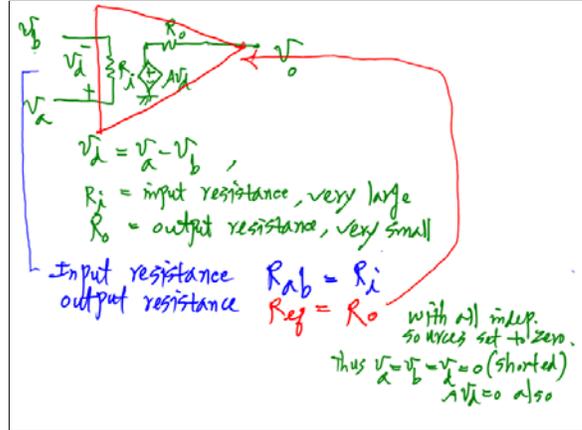

$(1) \times 2M \rightarrow 200(v_s - v_b) = 100(v_b - v_o) + v_b$ (1)
 $(2) \times 20k \rightarrow v_b - v_o = (v_o + A v_b) \cdot 400$ (2)



$$\begin{bmatrix} 301 & -100 \\ 400A-1 & 401 \end{bmatrix} \begin{bmatrix} v_b \\ v_o \end{bmatrix} = \begin{bmatrix} 200v_s \\ 0 \end{bmatrix}$$
 where $A = 200,000$

$$v_o = \frac{\begin{vmatrix} 301 & 200v_s \\ 400A-1 & 0 \end{vmatrix}}{\begin{vmatrix} 301 & -100 \\ 400A-1 & 401 \end{vmatrix}} = \frac{-200v_s(400A-1)}{301(401) - 100(400A-1)}$$

divide both sides by $(400A-1)$

$$1 + \frac{(301)(401)}{100(400A-1)} \approx -2 \frac{v_s}{v_o}$$

to be precise

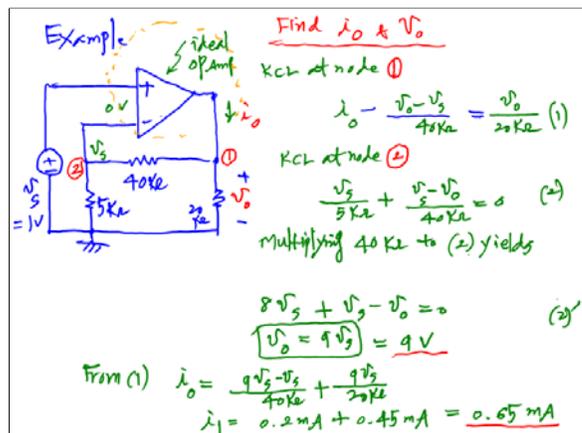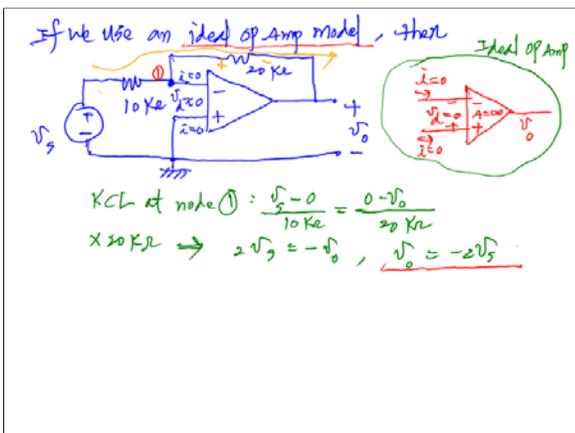

Inverting OP Amp

KCL at \odot $\frac{v_s}{R_s} = \frac{0 - v_o}{R_f}$ *sign inverting*

$$v_o = -\frac{R_f}{R_s} v_s$$

A circuit model

Example

KCL at \odot , $\frac{6-2}{20k} = \frac{2-v_o}{20k}$

$\times 40k \rightarrow 4 = 2 - v_o$ $v_o = -2$

Transresistance Amplifier

(Converts current input to voltage output)

$$v_o = -R i_s$$

Example

KCL at \odot , $\frac{v_i}{R_1} + \frac{v_i - v_o}{R_f} + \frac{v_i}{R_2} = 0$

also $v_i = -R_1 i_s$

$\Rightarrow -i_s + \frac{-R_1 i_s - v_o}{R_f} + \frac{-R_1 i_s}{R_2} = 0$

$v_o = -R_f \left(1 + \frac{R_1}{R_2} + \frac{R_1}{R_f}\right) i_s$

Summing OP Amp Circuit

output is a weighted sum of inputs - Artificial Neural network (ANN) circuit application

$$v_o = -\sum_{k=1}^N a_k v_k$$

$i_o = \sum_{k=1}^N \frac{v_k}{R_k}$ and

$$v_o = -R_f i_o = -\sum_{k=1}^N \left(\frac{R_f}{R_k}\right) v_k = a_k$$

Unity Gain Follower

$$v_o = A(v_i - v_o)$$

$$(1+A)v_o = Av_i$$

$$v_o = \frac{A}{1+A} v_i = \frac{1}{1+\frac{1}{A}} v_i$$


For A large, $v_o = v_i$

$$v_{o2} = -\left(\frac{v_{o1}}{R}\right) R = (+)v_{o1}$$

$$v_{o1} = (-) \sum_{k=1}^N \frac{R_f}{R_k} v_k$$

$$v_{o2} = (+) \sum_{k=1}^N \frac{R_f}{R_k} v_k = (+) \sum a_k v_k$$

weights

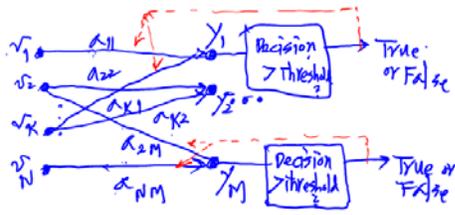


$$y_1 = a_{11}v_1 + a_{12}v_2 + w_{11}v_n$$

$$y_2 = a_{22}v_2 + a_{2k}v_k$$

$$y_M = a_{2M}v_2 + a_{NM}v_n$$

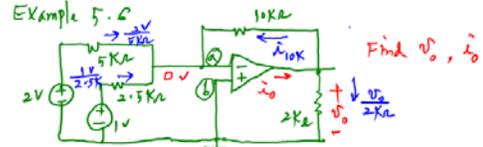Training of ANN \Rightarrow adjustment of $a_{ij} \propto \frac{y_j}{x_{ij}}$



$$i_{10k} = \frac{v_0}{10k\Omega} \quad i_0 = i_{10k} + \frac{v_0}{2k\Omega}$$

$$\text{At node } a, \quad i_{10k} + \frac{2}{5k} + \frac{1}{2.5k} = 0$$

$$i_{10k} = -0.4 \text{ mA} - 0.4 \text{ mA} = -0.8 \text{ mA}$$

$$v_0 = i_{10k} (10k\Omega) = -8 \text{ V}$$

$$i_0 = i_{10k} + \frac{-8 \text{ V}}{2k\Omega} = (-0.8 - 4) \text{ mA} = -4.8 \text{ mA}$$