

EE101 Final Examination, 4-7 p.m. March 20, 2018

Name _____ Student ID _____

2 pages of formulas and tables only are allowed. But, you must show all your work even when you apply formulas to get full credits. Otherwise, you will lose points.

Prob 1 [10] _____

Prob 2 [5] _____

Prob 3 [10] _____

Prob 4 [10] _____

Prob 5 [10] _____

Prob 6 [10] _____

Prob 7 [10] _____

Prob 8 [5] _____

Prob 9 [5] _____

Prob 10⁵[10] _____


Prob 11[5] _____

Prob 12[10] _____

TOTAL [100] _____

95

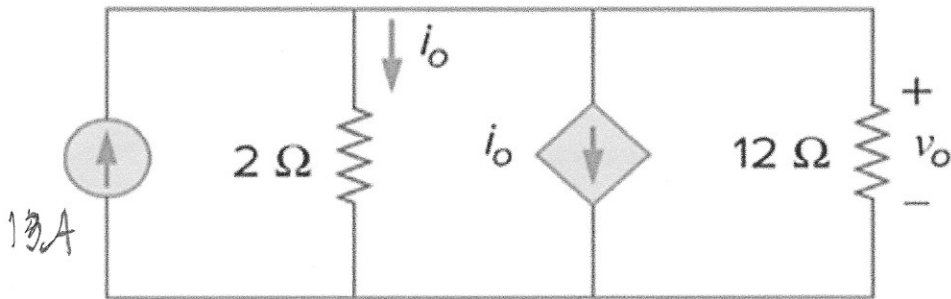[1] (10 points) Find the current i_o and v_o for a current source of 13 A.





KCL $13 = \frac{v_o}{2} \times 2 + \frac{v_o}{12}$
Multiplying both sides by 12 yields

$$13 \times 12 = 12 v_o + v_o = 13 v_o$$

$v_o = 12 \text{ V}$
$i_o = \frac{12}{2} = 6 \text{ A}$

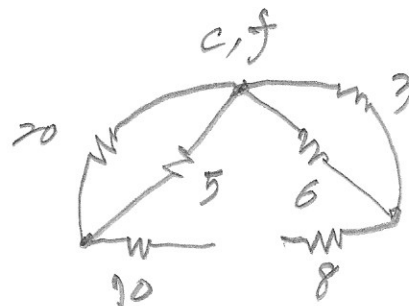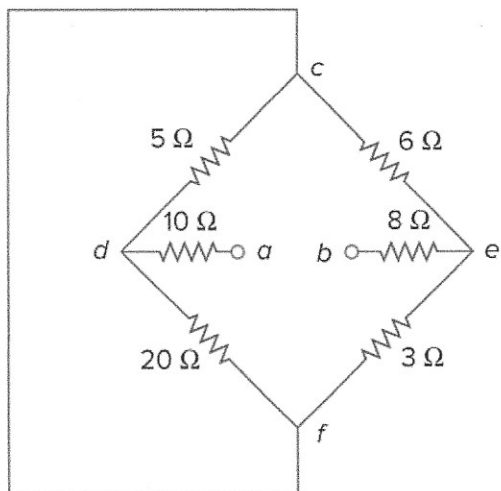[2] (5 points) Find the equivalent resistance between terminals a and b.




$$20 \parallel 5 = \frac{100}{25} = 4$$

$$3 \parallel 6 = \frac{18}{9} = 2$$



$$R_{ab} = 10 + 4 + 2 + 8$$

$$= \boxed{24 \Omega}$$

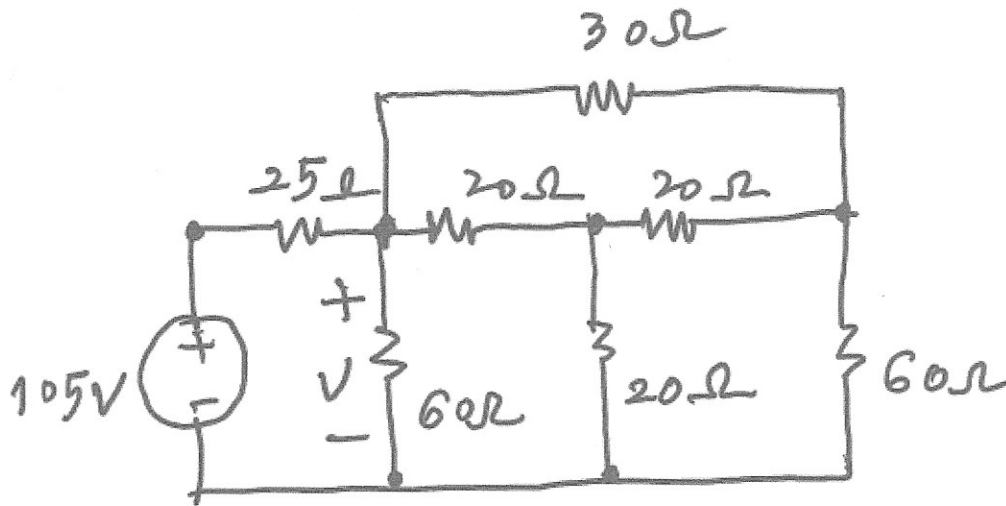[3] (10 points) Determine the voltage V in the circuit below.



$Y-\Delta$ transformation

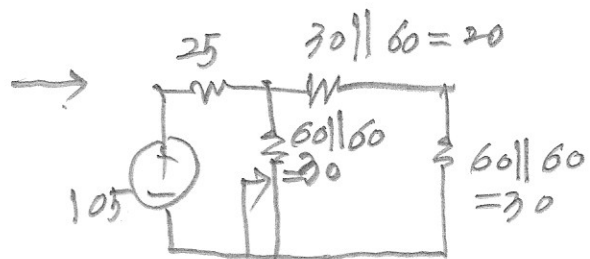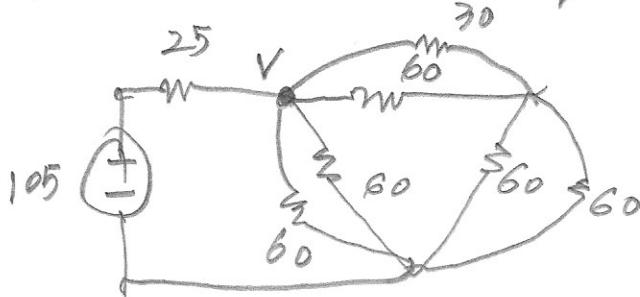


$$30 \parallel 50 = \frac{30 \times 50}{30 + 50} = \frac{1500}{80} = \frac{150}{8} \Omega$$

$$V = 105 \frac{\frac{150}{8}}{25 + \frac{150}{8}} = 18.52$$

$$= 105 \frac{150}{25 \times 8 + 150} = 105 \frac{3 \times 50}{350} = 45$$

$$= \boxed{45 \text{ V}}$$

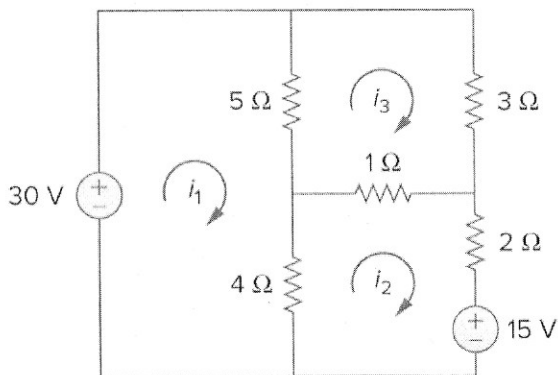[4] (10 points) Find the mesh current i_1 .



Mesh equations

$$\begin{aligned} \text{Mesh 1} \quad & -30 + 5(i_1 - i_3) + 4(i_1 - i_2) = 0 \\ \text{Mesh 2} \quad & 15 + 4(i_2 - i_1) + 1(i_2 - i_3) + 2i_2 = 0 \\ \text{Mesh 3} \quad & 3i_3 + 1(i_3 - i_2) + 5(i_3 - i_1) = 0 \end{aligned}$$

$$\begin{bmatrix} 9 & -4 & -5 \\ -4 & 7 & -1 \\ -5 & -1 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30 \\ -15 \\ 0 \end{bmatrix}$$

$$i_1 = \frac{\begin{vmatrix} 30 & -4 & -5 \\ -15 & 7 & -1 \\ 0 & -1 & 9 \end{vmatrix}}{\begin{vmatrix} 9 & -4 & -5 \\ -4 & 7 & -1 \\ -5 & -1 & 9 \end{vmatrix}} = \frac{1245}{199} = 6.26 \text{ amp.}$$

(Ans)


$$\begin{aligned} \text{denominator} &= 9 \times 7 \times 9 + (-1)(-4)(-5) + (-9)(-4)(-1) \\ &= 567 - 20 - 36 = 511 \\ \text{numerator} &= 30(7)(9) + (-15)(-1)(-5) + 0 - 0 - (-15)(-4)(9) - 30(-1)(-1) \\ &= 1245 - 60 - 540 - 30 = 515 \end{aligned}$$

$$\begin{aligned} \text{numerator} &= 30(7)(9) + (-15)(-1)(-5) + 0 - 0 - (-15)(-4)(9) - 30(-1)(-1) \\ &= 1245 \end{aligned}$$

(for continuation of problem 4 solution)

[5] (10 points) (a). (8 points) Find an expression for V_o in terms of V_1 , V_2 , and V_3 .

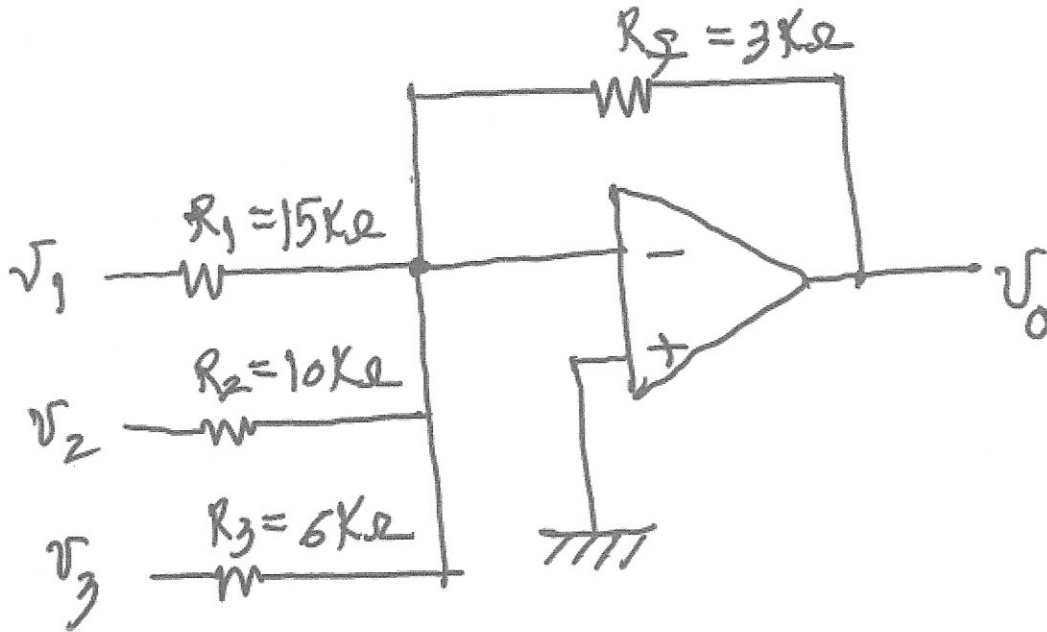
(b). (2 points) What is the value of V_o when $(V_1, V_2, V_3) = (75, 80, 90)$?




$$\begin{aligned} a) \quad V_o &= -\frac{3}{15} V_1 - \frac{3}{10} V_2 - \frac{3}{6} V_3 \\ &= -\underline{\underline{(0.2 V_1 + 0.3 V_2 + 0.5 V_3)}} \end{aligned}$$

$$\begin{aligned} b) \quad V_o &= -(0.2 \times 75 + 0.3 \times 80 + 0.5 \times 90) \\ &= -\underline{\underline{(15 + 24 + 45)}} = -\underline{\underline{84}} \end{aligned}$$

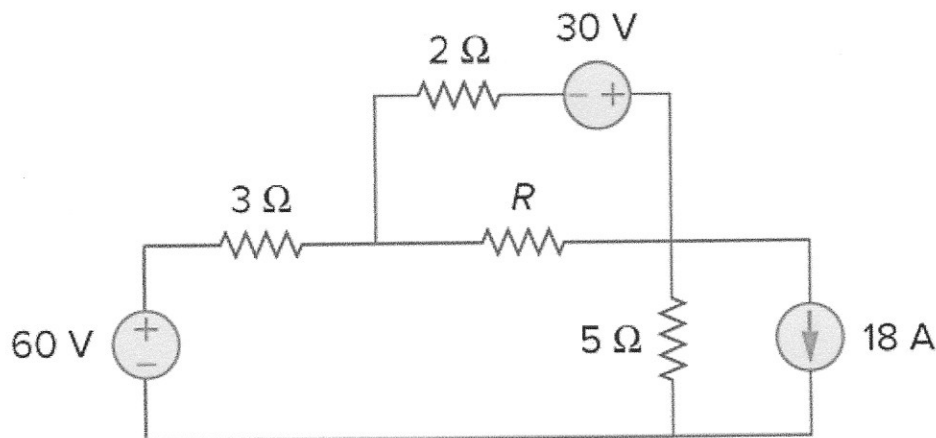[6] (10 points) Find the maximum power that can be transferred to resistor R in the circuit below and find its maximum power dissipation.



Theremin's equivalent circuit across R :

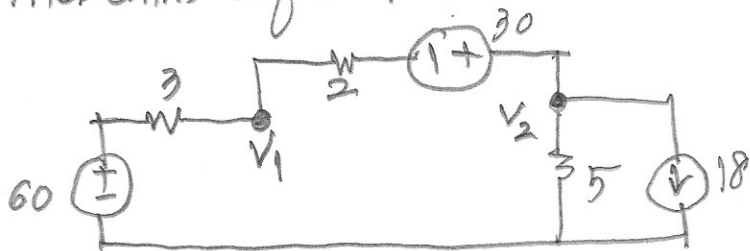



$$\text{KCL at } V_1 \text{ node} = \frac{60 - V_1}{3} = \frac{V_1 + 30 - V_2}{2} \rightarrow 120 - 2V_1 = 3V_1 + 90 - 3V_2 \quad (1)$$

$$\text{KCL at } V_2 \text{ node} = \frac{V_1 + 30 - V_2}{2} = \frac{V_2}{5} + 18 \rightarrow 5V_1 + 150 - 5V_2 = 2V_2 + 180 \quad (2)$$

$$(1) - (2) \rightarrow 4V_2 = 0 \quad \boxed{V_2 = 0}$$

$$\text{From (1)} \quad 5V_1 - 3(0) = 90 \quad \boxed{V_1 = 6}$$
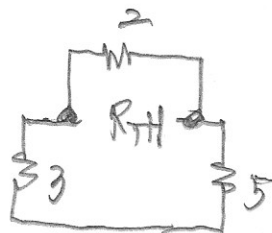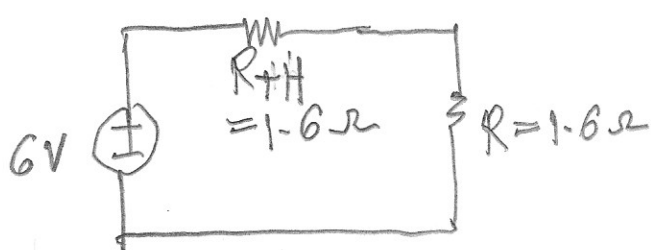
$$\left. \begin{array}{l} V_2 = 0 \\ V_1 = 6 \end{array} \right\} V_{OC} = 6 - 0 = \underline{\underline{6V}}$$



$$R_{TH} = 2 \parallel (3 + 5)$$


$$= \frac{2 \times 8}{2 + 8}$$

$$= \underline{\underline{1.6 \Omega}}$$

$$P_R = \frac{V_R^2}{R} = \frac{3^2}{1.6} = \frac{9}{1.6} = \underline{\underline{5.6 \text{ W}}}$$

ans

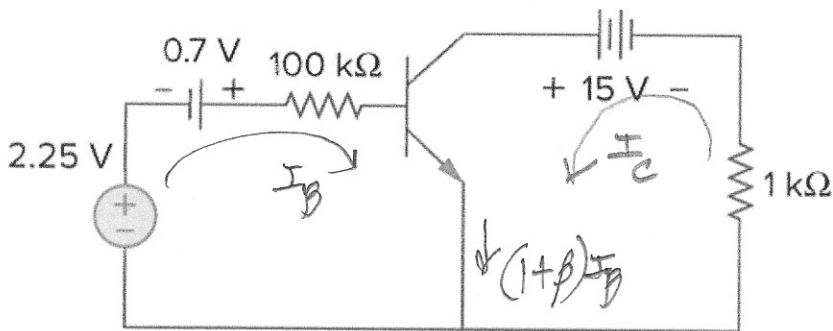[7] (10 points) Find the voltage across the collector and emitter terminals of the bipolar junction transistor (BJT) below with $\beta=100$ and $V_{BE}=0.7$ V for the circuit below.



Loop (Mesh) eq.


$$-2.25 - 0.7 + (100\text{k})I_B + 0.7 = 0$$

$$(100\text{k})I_B = 2.25 \Rightarrow I_B = \frac{2.25}{100\text{k}} = 22.5 \mu\text{A}$$

$$I_C = \beta I_B = 100 I_B = 2.25 \text{ mA}$$

$$V_{CE} = 15 - (1\text{k}\Omega) \cdot 2.25 \text{ mA} = \underline{12.75 \text{ V}} \quad \text{ans}$$

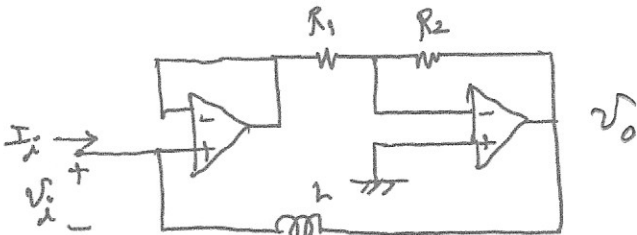[8] (5 points) Find an expression for L_{eq} in terms of R_1 , R_2 and L .



$$I_i(t) = \frac{1}{L} \int_{-\infty}^t v_i(t) dt$$

$$I_i = \frac{1}{L} \int_{-\infty}^{\infty} (v_i - v_o) dt \quad (1)$$


since $v_o = -\frac{v_i}{R_1} R_2 = -\frac{R_2}{R_1} v_i$

$$\begin{aligned} (1) \rightarrow I_i &= \frac{1}{L} \int_{-\infty}^{\infty} \left[v_i - \left(-\frac{R_2}{R_1} \right) v_i \right] dt \\ &= \frac{1}{L} \int_{-\infty}^{\infty} \left[1 + \frac{R_2}{R_1} \right] v_i dt \\ &= \frac{1}{\left(1 + \frac{R_2}{R_1} \right)} \int_{-\infty}^{\infty} v_i dt \end{aligned}$$


thus

$$L_{eq} = \frac{L}{1 + \frac{R_2}{R_1}} \quad \square$$

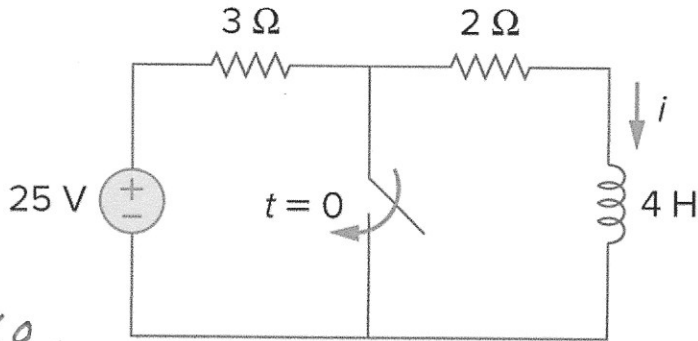
[10] (5 points) Find the inductor current $i(t)$ and $\frac{di(t)}{dt}$ for both $t < 0$ and $t > 0$.



For $t < 0$,

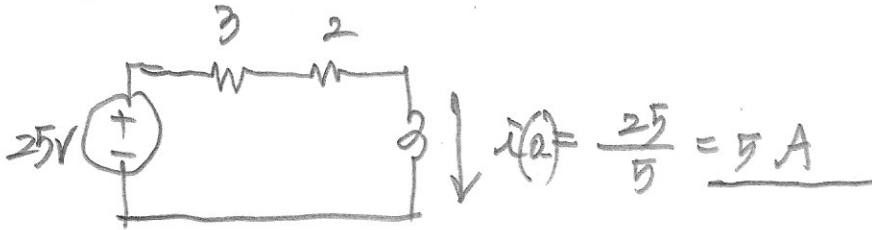


For $t > 0$

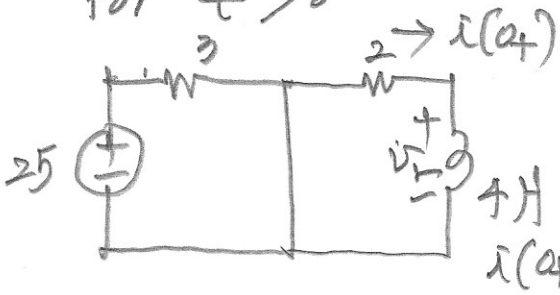

$$L \frac{di(t)}{dt} + i(t+) \cdot 2 = 0$$

$$\Rightarrow \frac{di(t)}{dt} = \frac{-5 \times 2}{4} = \underline{-2.5 [A/s]}$$

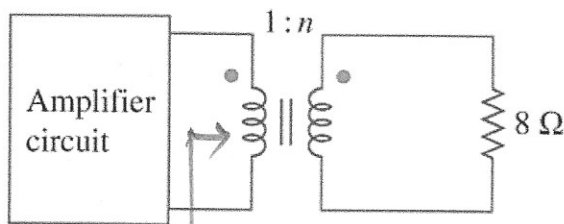[11] (5 points) Determine the transformer ratio n for maximum power transfer to the $8\ \Omega$ load when the Thevenin's equivalent voltage and the equivalent resistance for the amplifier circuit are 10V and $128\ \Omega$. Assume that the transformer is an ideal transformer and there is zero mutual coupling, i.e. $M=0$.



$$R_{eq} = \frac{8}{n^2}$$


For max power transfer

$$128 = R_{eq} = \frac{8}{n^2}$$

$$n^2 = \frac{8}{128}$$

$$n = \sqrt{\frac{8}{128}} = \frac{1}{4}$$

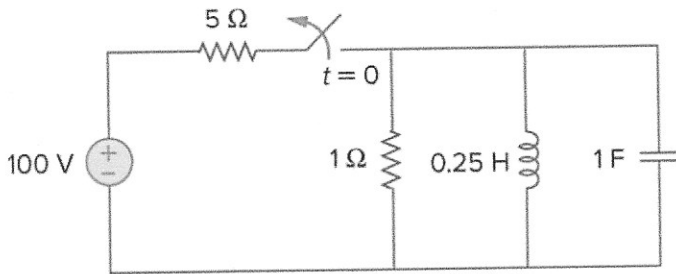
[12] (10 points) Find the voltage across 1F capacitor $v(t)$ for $t > 0$.



$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \frac{\sqrt{15}}{2}$$

$\omega_0 > \alpha \Rightarrow$ under damped

For $t \leq 0$

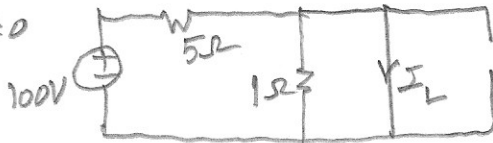


$$I_L(0) = 20 \text{ A}$$

$$V_C(0) = 0 \text{ V}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

For $t > 0$

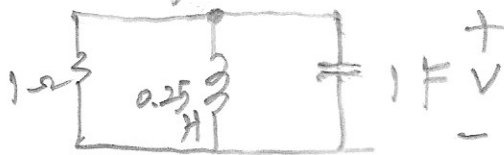

$$\text{KCL} \rightarrow \frac{V}{1} + \frac{1}{0.25} \int_0^t v(t) dt + \frac{dv}{dt} = 0$$

$$\frac{d}{dt} \rightarrow \frac{dv}{dt} + 4v + \frac{d^2v}{dt^2} = 0 \quad \text{characteristic eq} =$$

$$s^2 + 4s + 4 = 0$$

$$\alpha = 0.5 \quad \omega_0^2 = 4 \quad (\omega_0 = 2)$$

$\omega_0 > \alpha$ underdamped.

$$v(t) = M e^{-0.5t} \cos(\omega_d t - \theta), \text{ where } \omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{3.75}$$

$$v(0) = M \cos(-\theta) = 0 \Rightarrow \theta = 90^\circ$$

$$v'(0) = -0.5 M \cos(-\theta) + M(-\omega_d) \sin(-\theta) \overset{-20}{=} -20$$

$$M \sin(-\theta) = \frac{-20}{-\omega_d} \Rightarrow M = -\frac{20}{\omega_d} \quad \left. \begin{array}{l} \frac{dv}{dt} = -i \\ \text{at } t=0 \end{array} \right\}$$

$$v(t) = -\frac{20}{\omega_d} e^{-0.5t} \cos(\omega_d t - 90^\circ) = \sin \omega_d t$$

$$v(t) = -\frac{20}{\omega_d} e^{-0.5t} \sin \omega_d t$$

at $t=0$, $v(0) = 0$
 $v'(0) = \frac{1}{\omega_d}(0) - \frac{20}{\omega_d} (\cos \omega_d t)(\omega_d) = -20$

(Prob. 12 solution continued)