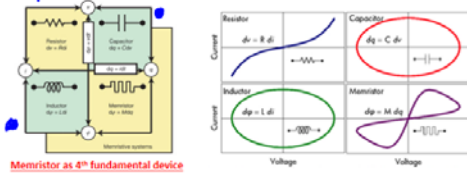


EE101 Lecture 15, Feb. 14, 2018

Q2 5 today
Capacitors & Inductors




Memristor as 4th fundamental device

4 Basic Variables
 v, i, q, ϕ ($\frac{dq}{dt} = i$
 $\frac{d\phi}{dt} = v$)

The Missing Link in Constitutive Relations

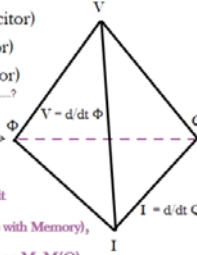- $Q = C V$ (Capacitor)
- $V = R I$ (Resistor)
- $\Phi = L I$ (Inductor)
- $\Phi = f(Q)$



- Capacitor (1745) by Ewald Georg von Kleist
- Resistor (1827) by Georg Simon Ohm
- Inductor (1831) by Michael Faraday

$\frac{d\Phi}{dt} = \frac{d f(Q)}{dt}$
 $= \frac{df(Q)}{dQ} \cdot \frac{dQ}{dt}$
 $V = M I$ (Resistance with Memory),
Thus Memristance $M = M(Q)$

Memristor-The missing circuit element

Sign In or Purchase
2585 Paper Citations
29 Patent Citations
13840 Full Text Views

1 L. Chua
View All Authors

Abstract Authors Figures References Citations Keywords Metrics Media

Abstract:
A new two-terminal circuit element called the memristor characterized by a relationship between the charge q and the flux ϕ is introduced as the fourth basic circuit element. An electromagnetic field interpretation of this relationship in terms of a quasi-static expansion of Maxwell's equations is presented. Many circuit-theoretic properties of memristors are derived. It is shown that this element exhibits some peculiar behavior different from that exhibited by resistors, inductors, or capacitors. These properties lead to a number of unique applications which cannot be realized with RLC networks alone. Although a physical memristor device without internal power supply has not yet been discovered, operational laboratory models have been built with the help of active circuits. Experimental results are presented to demonstrate the properties and potential applications of memristors.

IEEE Trans. on Circuit Theory, Sept. 1971

Memristive devices and systems

Sign In or Purchase
877 Paper Citations
20 Patent Citations
5000 Full Text Views

2 L. Chua, Bing Ma King
View All Authors

Abstract Authors Figures References Citations Keywords Metrics Media

Abstract:
A broad generalization of memristors—a recently postulated circuit element—to an interesting class of nonlinear dynamical systems called memristive systems is introduced. These systems are unconventional in the sense that while they behave like resistive devices, they can be endowed with a rather exotic variety of dynamic characteristics. While possessing memory and exhibiting small-signal inductive or capacitive effects, they are incapable of energy discharge and they introduce no phase shift between the input and output waveforms. The zero-crossing property gives rise to a Lissajous figure which always passes through the origin. Memristive systems are hysteretic in the sense that their Lissajous figures vary with the excitation frequency. At very low frequencies, memristive systems are indistinguishable from nonlinear resistors while at extremely high frequencies, they reduce to linear resistors. These anomalous properties have misled and prevented the identification of many memristive devices and systems including the thermistor, the Hodgkin-Huxley membrane circuit model, and the discharge tubes. Generic properties

Proc. of the IEEE, Feb. 1976

nature PDF

Letter

The missing memristor found

Dmitri B. Strukov, Gregory S. Snider, Duncan R. Stewart & R. Stanley Williams

Nature 453, 80–83 (01 May 2008)
doi:10.1038/nature06892
Download Citation

Received: 06 December 2007
Accepted: 17 March 2008
Published online: 01 May 2008
Corrigendum: 25 June 2009

Abstract


Anyone who ever took an electronics laboratory class will be familiar with the fundamental passive circuit elements: the resistor, the capacitor and the inductor. However, in 1971 Leon Chua reasoned from symmetry arguments that there should be a fourth fundamental element, which he called a memristor (short for memory resistor).

Capacitor

Dielectric with permittivity ϵ
Metal plates, each with area A
 d

Figure 6.1 A typical capacitor.

Capacitance C [F]

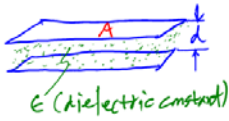

$$\epsilon = \epsilon_r \epsilon_0$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

$$\epsilon_r = \begin{cases} 3.9 & \text{for } \text{SiO}_2 \\ 11.68 & \text{for } \text{Si} \\ 7 \sim 8 & \text{for } \text{SiN} \end{cases}$$

$$C = \epsilon \frac{A}{d} \quad \text{For air, } \epsilon = \epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

If $d = 1 \text{ mm}$, $A = 1 \text{ cm}^2$, for air

$$C = \epsilon_0 \frac{1 \text{ cm}^2}{0.1 \text{ cm}} = 8.854 \times 10^{-14} \times 10 = 8.854 \times 10^{-13} \text{ F}$$

$$= 0.8854 \text{ pF}$$


$$v = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau, \quad C \frac{dv}{dt} = i$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$= \frac{1}{C} \left[\int_{-\infty}^{t_0} i(\tau) d\tau + \int_{t_0}^t i(\tau) d\tau \right]$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$$

(Example)

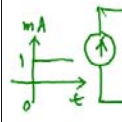

$$v(t) = 0 + \frac{1}{10^{-6}} \int_0^t (1 \times 10^{-3}) d\tau$$

$$= 10^3 t + 0$$

Inductor


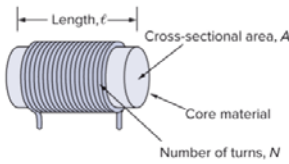


Figure 6.21 Typical form of an inductor.

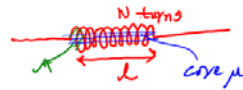

shown in Fig. 6.21.


$$L = \frac{N^2 \mu A}{l} \quad (6.19)$$

where N is the number of turns, l is the length, A is the cross-sectional area, and μ is the permeability of the core. We can see from Eq. (6.19) that inductance can

$$\mu_0 = \mu_{\text{air}} = 4\pi \times 10^{-7} \text{ henry/m}$$

$$= 1.257 \times 10^{-6} \text{ henry/m}$$
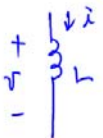
$$\mu = \mu_r \mu_0 = \begin{matrix} 6.3 \times 10^{-3} & (\mu_r = 5000) & \text{for iron} \\ 2.7 \times 10^{-3} & (\mu_r = 18000) & \text{for Cobalt iron} \end{matrix}$$



$$v(t) = L \frac{di(t)}{dt}$$

$$\int_{-\infty}^t v(\tau) d\tau = L [i(t) - i(-\infty)]$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

$$= \frac{1}{L} \left[\int_{-\infty}^{t_0} v(\tau) d\tau + \int_{t_0}^t v(\tau) d\tau \right]$$

$$= \frac{1}{L} \left[\phi(t_0) + \int_{t_0}^t v(\tau) d\tau \right]$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau$$

$$p(t) = v(t) i(t)$$

For capacitor,

$$\text{Power } p(t) = v(t) i(t)$$

$$= v(t) C \frac{dv(t)}{dt}$$

Energy stored in the capacitor


$$E(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t [v(\tau) C \frac{dv(\tau)}{d\tau}] d\tau$$

$$= C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C [v^2(t) - \underbrace{v^2(-\infty)}_{=0}] = \frac{1}{2} C v^2(t)$$

For inductor



$$p(t) = v(t) i(t) = L \frac{di(t)}{dt} \cdot i(t)$$
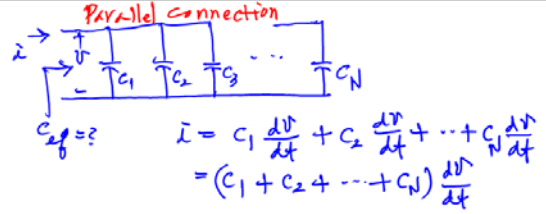
$$E(t) = \int_{-\infty}^t p(t) dt = L \int_{-\infty}^t i(t) \frac{di(t)}{dt} dt = L \int_{i(-\infty)}^{i(t)} i di = \frac{1}{2} L [i^2(t) - i^2(-\infty)] = \frac{1}{2} L i^2(t)$$



$$C_{\text{eq}} = C_1 + C_2 + \dots + C_N$$


Serial connection

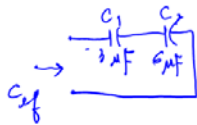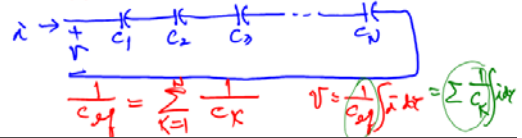

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_1 + C_2}{C_1 C_2}$$


$$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$

similar to

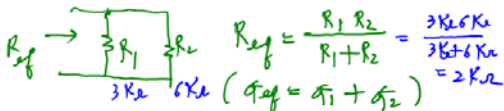


$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{3k\Omega \cdot 6k\Omega}{3k\Omega + 6k\Omega} = 2k\Omega$$
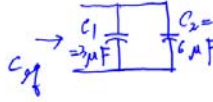
$$C_{\text{eq}} = \frac{3\mu\text{F} \cdot 6\mu\text{F}}{3\mu\text{F} + 6\mu\text{F}} = 2\mu\text{F}$$


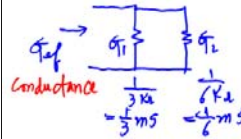
$$C_{\text{eq}} = C_1 + C_2 = 3\mu\text{F} + 6\mu\text{F} = 9\mu\text{F}$$




$$G_{\text{eq}} = G_1 + G_2 = \frac{1}{3\text{ms}} + \frac{1}{6\text{ms}} = \frac{2+1}{6} \text{ms} = \frac{1}{2} \text{ms}$$

$$v = \frac{1}{C_1} \int i(t) dt + \frac{1}{C_2} \int i(t) dt + \dots + \frac{1}{C_N} \int i(t) dt = \left[\sum_{k=1}^N \frac{1}{C_k} \right] \int i(t) dt = \frac{1}{C_{\text{eq}}} \int i(t) dt$$

$$\frac{1}{C_{\text{eq}}} = \sum_{k=1}^N \frac{1}{C_k}$$

$$\text{or } C_{\text{eq}} = \frac{1}{\sum_{k=1}^N \frac{1}{C_k}}$$


Example

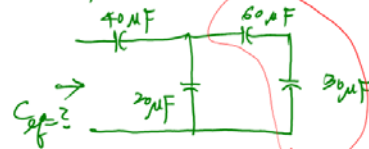

$$C_{\text{eq1}} = \frac{1}{\frac{1}{60\mu\text{F}} + \frac{1}{30\mu\text{F}}}$$

$$C_{\text{eq1}} = \frac{1}{\frac{1}{60\mu\text{F}} + \frac{1}{30\mu\text{F}}} = \frac{60\mu\text{F}}{1+2} = 20\mu\text{F}$$
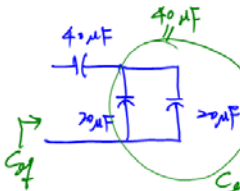
$$C_{\text{eq}} = \frac{1}{\frac{1}{40\mu\text{F}} + \frac{1}{20\mu\text{F}}} = \frac{40\mu\text{F}}{1+1} = 20\mu\text{F}$$



$$C_{\text{eq}} = \frac{1}{\frac{1}{40\mu\text{F}} + \frac{1}{20\mu\text{F}}} = \frac{40\mu\text{F}}{1+1} = 20\mu\text{F}$$

Series Connection of inductors

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$= \left(\sum_{k=1}^n L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = \sum_{k=1}^n L_k$$

parallel connection of inductors

$$i = \sum \frac{1}{L_k} \int v(t) dt$$

$$= \frac{1}{L_{eq}} \int v(t) dt$$

Thus
$$\frac{1}{L_{eq}} = \sum_{k=1}^n \frac{1}{L_k}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$= \frac{L_1 + L_2}{L_1 L_2}$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

$$= \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2H$$

$$L_{eq} = 2H$$

$$L_{eq} = 5H$$

	Capacitance	Inductance
Serial	$\frac{1}{C_{eq}} = \sum \frac{1}{C_k}$	$L_{eq} = \sum L_k$
Parallel	$C_{eq} = \sum C_k$	$\frac{1}{L_{eq}} = \sum \frac{1}{L_k}$
	↑ Like G	↑ Like R

TABLE 6.1

Important characteristics of the basic elements.[†]

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v-i:	$v = iR$	$v = \frac{1}{C} \int i(t) dt + v(t_0)$	$v = L \frac{di}{dt}$
i-v:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int v(t) dt + i(t_0)$
p or w:	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

[†] It is appropriate at this point to summarize the most important characteristics of the three basic circuit elements we have studied. The summary is given in Table 6.1.

$$v(t) = v(t) \int_0^t i(t) dt$$

$$= 0 + \frac{1}{10^3} \int_0^t 10^3 dt \quad t \leq 10ms$$

$$= 10^3 t$$

$$\text{for } t > 10ms, v(t) = 10^3 \times 10 = 10V$$

$$p(t) = v(t) i(t) = 10mW$$

$$E(t) = \int_0^t p(t) dt = \int_0^t (10^3 t) dt \quad t \leq 10ms$$

$$= 10^3 \left(\frac{1}{2} t^2 \right) \Big|_0^t$$

$$= 10^3 \left(\frac{1}{2} t^2 \right)$$

$$E(t=10^3) = \frac{1}{2} \times 10^3 \times 10^{-4} = 0.05J$$

* same for t > 10ms

$$10^3 \cdot \frac{1}{2} t^2$$

