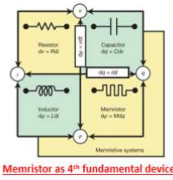


EE101 Lecture 18; Feb. 18, 2018
Qz 6 on Feb 21 (w)



	Resistor	Capacitor
Current	$dv = R di$	$dq = C dv$
Voltage	$dp = L di$	$dp = M dq$

TABLE 6.1

Important characteristics of the basic elements.†

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v-i:	$v = Ri$	$v = \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
i-v:	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w:	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

† It is appropriate at this point to summarize the most important characteristics of the three basic circuit elements we have studied. The summary is given in Table 6.1.

Quiz 5
weighted summing circuit

virtual ground

the current through R_f , $i_{Rf} = \sum_{i=1}^N \frac{v_i}{R_i}$

Thus, $v_o = -R_f i_{Rf} = -\sum_{i=1}^N \left(\frac{R_f}{R_i}\right) v_i$

$= -\sum_{i=1}^N w_i v_i$ (weight)

$i_{Rf} = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3}$

v_o (final grade score) = 20% Qz + 30% Mid + 50% Final

$= 0.2 v_1 + 0.3 v_2 + 0.5 v_3$

$= \left[\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right]$

neglect sign reversal

$\Rightarrow R_1 = R_f / 0.2 = 30k\Omega, R_2 = R_f / 0.3 = 20k\Omega, R_3 = R_f / 0.5 = 12k\Omega$

An Integrator circuit

$i_1 = \frac{v_s}{R_f}$

$v_o = -\frac{1}{C} \int i_1 dt$

$= -\frac{1}{C} \int \frac{v_s(t)}{R_f} dt$

$= -\frac{1}{C R_f} \int v_s(t) dt$



when $C R_f = 1$, $v_o = -\int v_s(t) dt$

$i_1 = -\frac{v_s}{R_f}$

$v_o = -\frac{1}{C} \int \left(-\frac{v_s(t)}{R_f}\right) dt$

when $C R_f = 1$, $v_o = \int v_s(t) dt$

A Differentiation Circuit

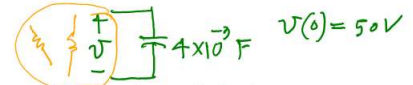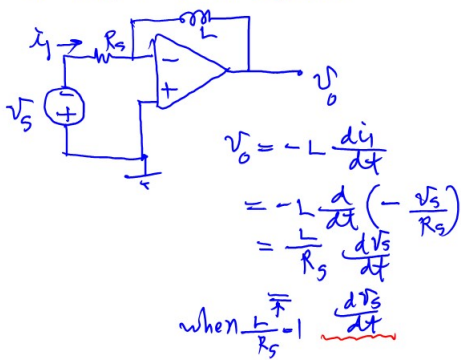

6.8 A 4-mF capacitor has the terminal voltage

$$v = \begin{cases} 50 \text{ V}, & t \leq 0 \\ Ae^{-100t} + Be^{-600t} \text{ V}, & t \geq 0 \end{cases}$$

If the capacitor has an initial current of 2 A, find:

- (a) the constants A and B , $i(t)|_{t=0} = 2 \text{ A}$
 (b) the energy stored in the capacitor at $t = 0$,
 (c) the capacitor current for $t > 0$.

$$i(t) = C \frac{dv(t)}{dt}$$

$$= 4 \times 10^{-3} [\text{F}] \frac{d}{dt} [Ae^{-100t} + Be^{-600t}] [\text{V}]$$

$$= 4 \times 10^{-3} [-100Ae^{-100t} - 600Be^{-600t}] \left[\frac{\text{V}}{\text{s}} \right]$$

$$i(0) = 4 \times 10^{-3} (-100A - 600B) = 2 \text{ [A]}$$

Also at $t=0$, $V = 50 \text{ [V]} = A + B$

$$\Rightarrow \begin{cases} A + B = 50 \\ -0.4A - 2.4B = 2 \end{cases} \begin{bmatrix} 1 & 1 \\ 1 & 6 \end{bmatrix} \begin{bmatrix} A \\ B \end{bmatrix} = \begin{bmatrix} 50 \\ -5 \end{bmatrix}$$

$$A = \frac{\begin{vmatrix} 50 & 1 \\ -5 & 6 \end{vmatrix}}{\begin{vmatrix} 1 & 1 \\ 1 & 6 \end{vmatrix}} = \frac{300 - (-5)}{6-1} = \frac{305}{5} = 61$$

$$B = 50 - A = -11$$

Energy stored in the capacitor at $t=0$

$$E = \frac{1}{2} C v^2 = \frac{1}{2} \times (4 \times 10^{-3} \text{ F}) (50 \text{ V})^2$$

$$= 2 \times 2500 \times 10^{-3} \text{ [F V V]}$$

$$= 5 \text{ J} \quad \left[\frac{\text{F V}}{\text{s}} \frac{\text{V s}}{\text{A}} \right] = \text{[J]}$$

$$i(t) = C \frac{dv(t)}{dt} = 4 \times 10^{-3} [-100 \times 61 e^{-100t} - 600(-11)e^{-600t}]$$

$$= -24.4 e^{-100t} + 26.4 e^{-600t}$$

6.11 A 4-mF capacitor has the current waveform shown in Fig. 6.48. Assuming that $v(0) = 10 \text{ V}$, sketch the voltage waveform $v(t)$.


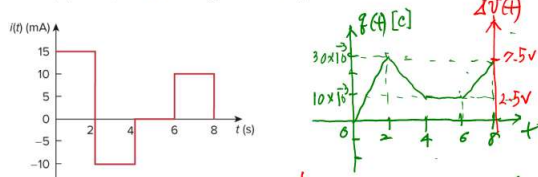


Figure 6.48 For Prob. 6.11.

$$v(0) = 10$$

$$v(t) = 10 + \frac{1}{4 \times 10^{-3}} \int_0^t i(\tau) d\tau = 10 + 250 \int_0^t i(\tau) d\tau$$
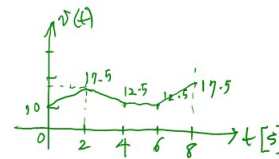
$$v(t) = 10 + \frac{1}{4} \int_0^t i(\tau) d\tau = 10 + \frac{1}{4 \times 10^{-3}} \int_0^t i(\tau) d\tau$$



6.13 Find the voltage across the capacitors in the circuit of Fig. 6.49 under dc conditions.

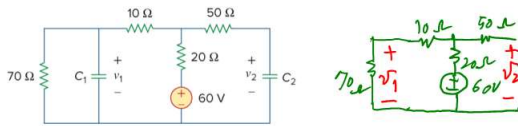


Figure 6.49
For Prob. 6.13.

C_1, C_2 are open circuited!
 $i_K = C_K \frac{dv_K}{dt} = 0 \text{ for } K=1,2$
 $V_1 = 60 \frac{70}{70+10+30} = 60 \times 0.7 = 42 \text{ V}$
 $V_2 = 60 - 60 \frac{20}{70+10+20} = 60 - 12 = 48 \text{ V}$

6.24 In the circuit shown in Fig. 6.58 assume that the capacitors were initially uncharged and that the current source has been connected to the circuit long enough for all the capacitors to reach steady state (no current flowing through the capacitors). Determine the voltage across each capacitor and the energy stored in each.



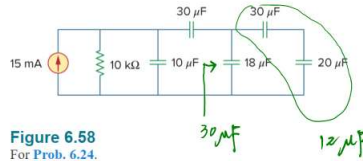


Figure 6.58
For Prob. 6.24.

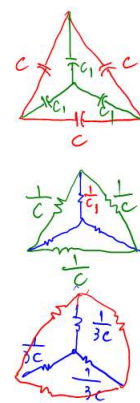

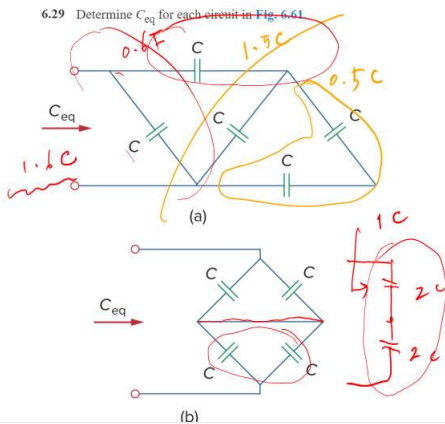6.29 Determine C_{eq} for each circuit in Fig. 6.61



$V = \left[\frac{1}{C} \right] \int i(t) dt$
 Treat $\frac{1}{C}$ as R
 $\frac{1}{C_1} = \frac{(\frac{1}{C})(\frac{1}{C})}{\frac{1}{C} + \frac{1}{C} + \frac{1}{C}} = \frac{\frac{1}{C^2}}{\frac{3}{C}} = \frac{1}{3C}$
 $C_1 = 3C$
 $C' = \frac{(\frac{1}{3C} \frac{1}{3C}) \times 3}{\frac{1}{3C} + \frac{1}{3C} + \frac{1}{3C}} = \frac{\frac{1}{3C} \frac{1}{3C} \times 3}{\frac{3}{3C}} = \frac{1}{C} \checkmark$ (original value)

6.29(a) \Rightarrow

$\frac{1}{C_{eq}} = \frac{1}{3C} + \frac{1}{C} + \frac{1}{C} = \frac{7}{3C}$
 $C_{eq} = \frac{3}{7} C$
 $C_{eq2} = 3C + \frac{3}{7} C = \frac{24}{7} C$
 $C_{eq} = \frac{3C (\frac{24}{7} C)}{3C + \frac{24}{7} C} = \frac{12C}{45}$

6.32 In the circuit in Fig. 6.64, let $i_1 = 4.5e^{-2t}$ mA and the voltage across each capacitor is equal to zero at $t = 0$. Determine v_1 and v_2 and the energy stored in each capacitor for all $t > 0$.

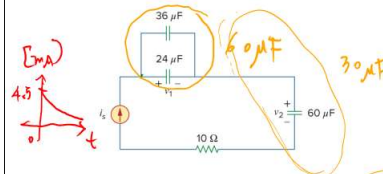


Figure 6.64
For Prob. 6.32.




$i_2 = C_2 \frac{dv_2}{dt} = 60 \mu F \frac{dv_2}{dt} = 4.5 e^{-2t} \times 10^{-3} \Rightarrow \frac{dv_2}{dt} = \frac{4.5 \times 10^{-3}}{60 \times 10^{-6}} e^{-2t} = 75 e^{-2t} \text{ V/s}$

$$\left[\frac{4.5 \times 10^{-3}}{60 \times 10^{-6}} \right] = A$$

$$\int_0^t \frac{t}{e^{2t}} dt = \frac{e^{-2t}}{-2} \Big|_0^t$$

$$= \frac{1}{2}(1 - e^{-2t})$$
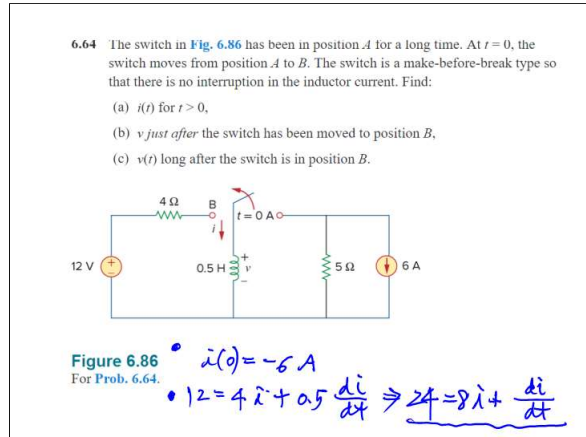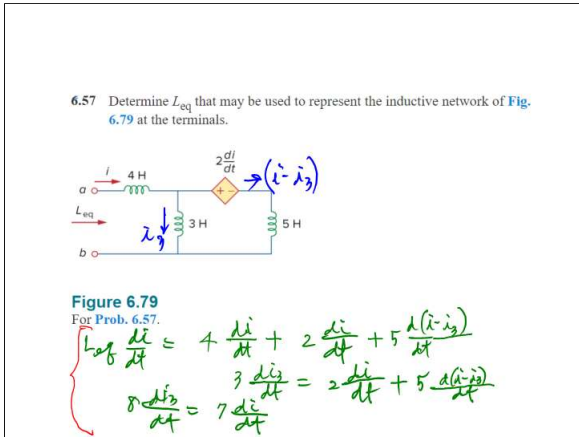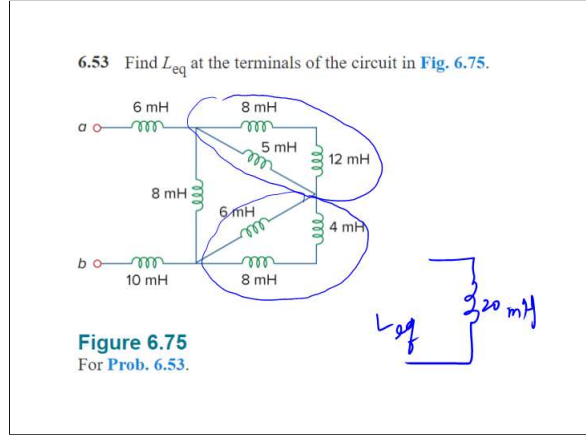
$$v_L(t) = A \frac{1}{2}(1 - e^{-2t}) \quad t=0 \quad v_L(0)=0$$



$$\frac{di}{dt} + 8i = 24 \quad i(0) = -6$$

$$\frac{di}{dt} = 24 - 8i$$

$$\frac{di}{24 - 8i} = dt$$

$$\frac{-1}{8} \ln(24 - 8i) = dt$$

$$\frac{d(24 - 8i)}{24 - 8i} = -8 dt$$

integration on both sides

$$\ln(24 - 8i)(t) = -8t \rightarrow \frac{24 - 8i(t)}{24 - 8(-6)} = e^{-8t}$$

$$24 - 8i(t) = 72 e^{-8t} \Rightarrow i(t) = 7.9 e^{-8t}$$

