


EE 101 Lecture 18, Feb. 23, 2018

Quiz 7 on Monday, Feb. 26

(HW 6 + Magnetically Coupled Circuits)

HW 7 is for RC, RL circuit analysis and would be covered in Quiz 8

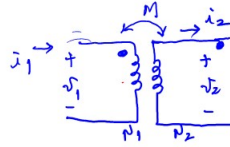Midterm papers to be returned on Monday, Feb. 26.





- convention
- 1) if both currents enters into terminals, M is +
- 2) if either current enters in opposite direction, M is -
- 3) if both currents leaves terminals, M is +.

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} L_1 & M_{12} \\ M_{21} & L_2 \end{bmatrix} \begin{bmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix}$$

here $M_{12} = M_{21} = M$

More on the direction convention

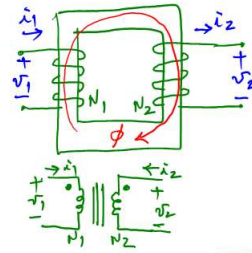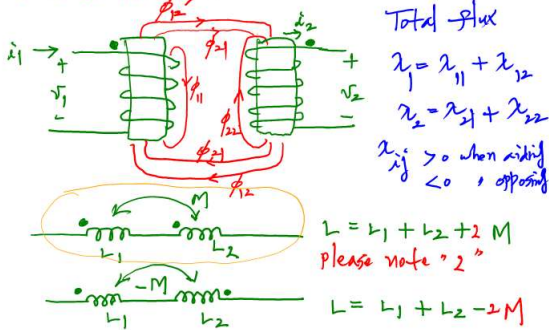


$$v_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = N_2 \frac{d\phi}{dt}$$


$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = n$$







(power conservation) $v_1 i_1 = v_2 i_2 \Rightarrow \frac{v_2}{v_1} = \frac{i_1}{i_2} = \frac{N_2}{N_1}$
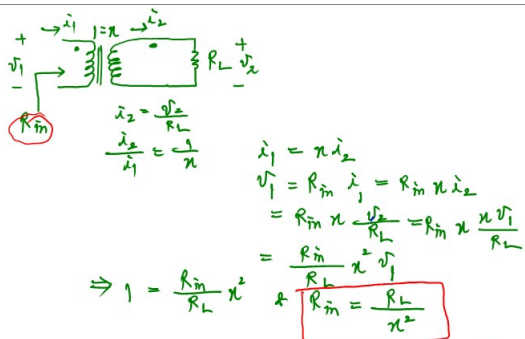
$$\frac{i_2}{i_1} = \frac{N_1}{N_2} = \frac{1}{n}$$




A case for Max. Power Transfer

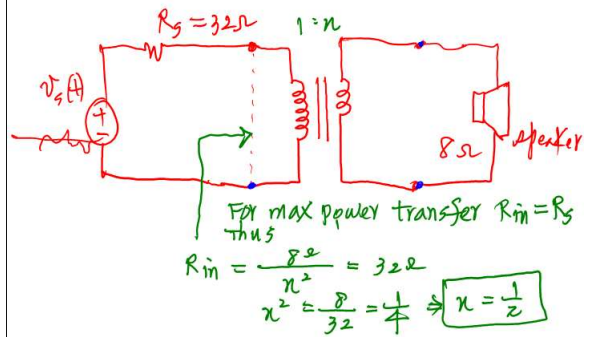

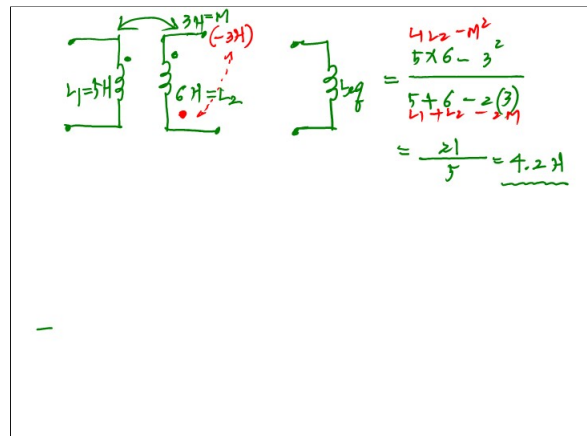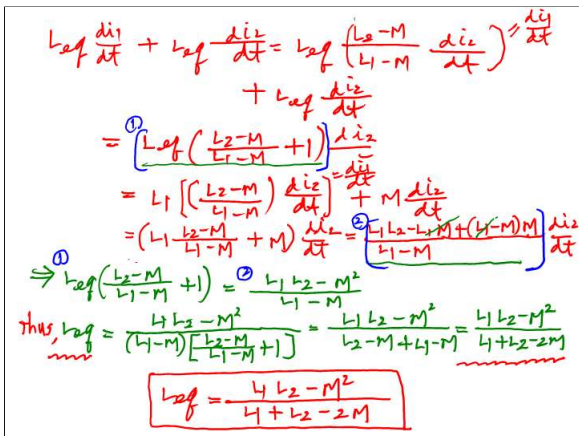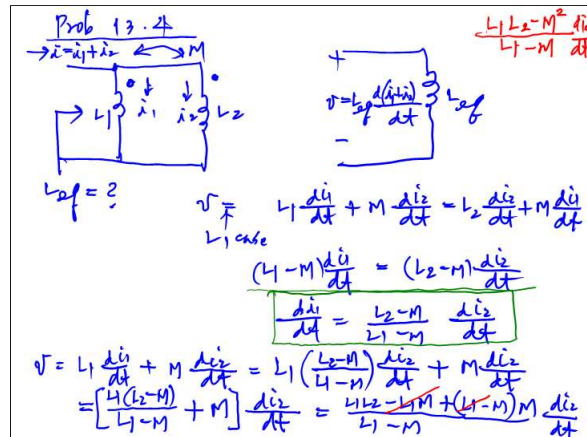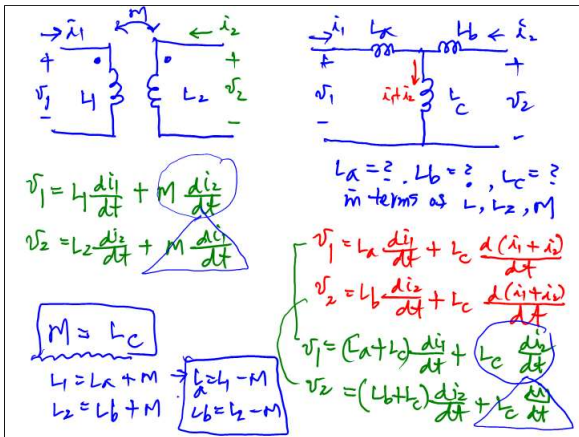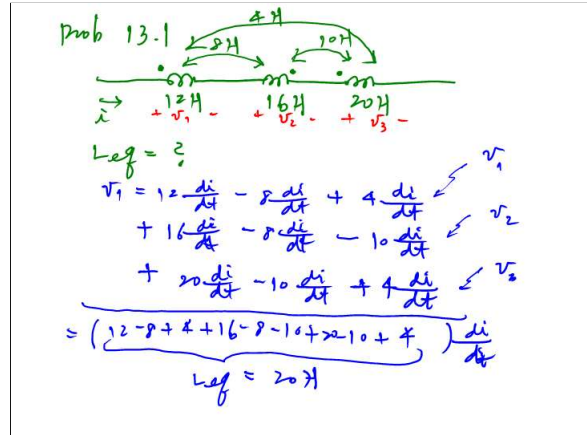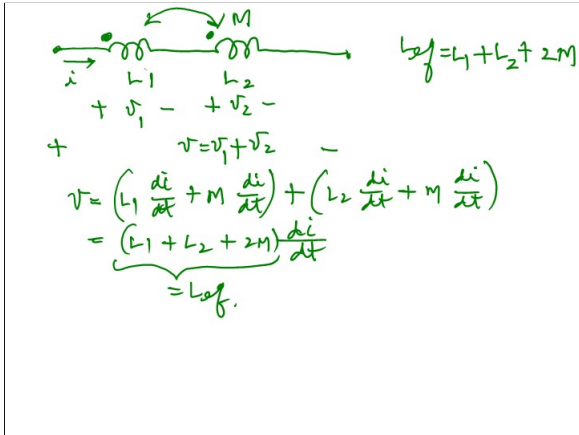

phasors (chap 9)

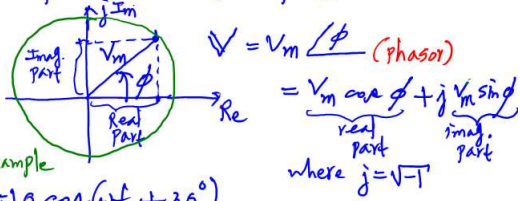

Example
 $V(t) = 10 \cos(\omega t + 30^\circ)$
 $V = 10 \angle 30^\circ$ (phasor)

$V_1(t) = 10 \sin(\omega t + 30^\circ)$
 $= 10 \cos(\omega t - 90^\circ + 30^\circ) = 10 \cos(\omega t - 60^\circ)$
 $V_1 = 10 \angle -60^\circ$ (phasor)

$\sin \omega t = \cos(\omega t - 90^\circ)$
 $= \cos \omega t \cos 90^\circ + \sin \omega t \sin 90^\circ$
 $= \sin \omega t$

$v = Ri + L \frac{di}{dt}$

If $i(t) = e^{j\omega t}$, then $v(t) = R e^{j\omega t} + j\omega L e^{j\omega t}$
 $= (R + j\omega L) e^{j\omega t}$

$V(j\omega) = (R + j\omega L) I(j\omega)$
 $\frac{V(j\omega)}{I(j\omega)} = Z(j\omega) = R + j\omega L$

$Z(j\omega) = R + j\omega L = Z \angle \phi_Z$ (phasor)
 $Z = \sqrt{R^2 + (\omega L)^2}$
 $\phi_Z = \tan^{-1} \frac{\omega L}{R}$

In general, $I = \frac{V}{Z} = \frac{V \angle \theta_V}{Z \angle \theta_Z} = \frac{V_m}{Z} \angle \theta_V - \theta_Z$
 $i(t) = \frac{V_m}{Z} \cos(\omega t + \theta_V - \theta_Z)$

Example If $R = 3 \Omega$ and $j\omega L = j4$
 $Z = 3 + j4 = 5 \angle 53.1^\circ$

If $R = 3$
 $j\omega L = j4$
 $Z = 3 + j4 = 5 \angle 53.1^\circ$
 $\phi_Z = \tan^{-1} \frac{4}{3} = 53.1^\circ$
 $Z = \sqrt{3^2 + 4^2} = 5$