

EE101 Lecture #2 Jan 10, 2018

rewebsite <https://courses.soe.ucsc.edu/courses/ee101/winter18/01>

TA's Emily Enlow eenlow@ucsc.edu
 Ibrahim Hossain ghossain@ucsc.edu
 Tae Sung Kim tksim@ucsc.edu
 Tuwin Lam tulam@ucsc.edu

Text C.K. Alexander & M.W.O. Sadiku Fundamentals of Electric Circuits


<connect>
<http://connect.mheducation.com/class/5-Kang-winter2018-mw5240>

Course Grading


Weekly Quizzes based on weekly HWs 20%
 (Best 7 out of 9 Quizzes)
 Submit HW solutions to your TA

Mid-term Examination (Feb 7, 1 page of formulas allowed) 30%

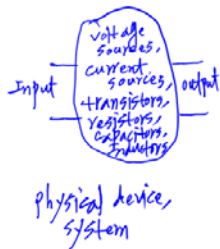Final Examination (March 20, 2 pages of formulas allowed) 50%



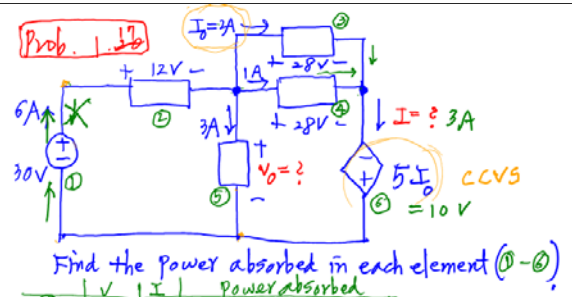
- 1) Formulate circuit equations using model equations for elements and circuit laws (KCL, KVL)
- 2) solve for outputs for given inputs




Find the power absorbed in each element (1-6)

Element	V	I	Power absorbed
1	30	-6	-180W
2	12	6	72W
3	28	2	56W
4	28	1	28W
5	18	3	54W
6	-10	3	-30W

-210W
+210W
0

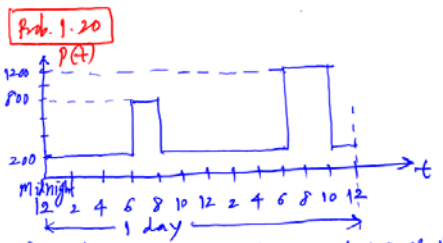

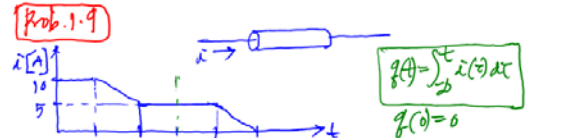- Total energy consumed in one day in KWh?
 $200 \times 6 + 800 \times 2 + 200 \times 10 + 1200 \times 4 + 400 \times 2 = 1200 + 1600 + 2000 + 4800 + 800 = 10 \text{ KWh}$
- Average power per our over 24 hour period?
 $P_{avg} = \frac{1}{24} \int_0^{24} P(t) dt = \frac{10 \text{ KWh}}{24 \text{ h}} \approx 0.416 \text{ kW}$



- Find the total charge that passes through the element:
- $t=1 \text{ s}$, i.e. $q(t=1)$
 $0 + \int_0^1 i(t) dt = 10 \cdot 1.5 = 10 \text{ Coulomb [C]}$
 - $t=3 \text{ s}$, i.e. $q(t=3)$
 $0 + \int_0^3 i(t) dt = 10 + 7.5 + 5 = 22.5 \text{ C}$
 - $t=5 \text{ s}$, i.e. $q(t=5)$
 $0 + \int_0^5 i(t) dt = 22.5 + 7.5 = 30 \text{ C}$

Prob. 1.14

For $t \geq 0$, $v(t) = 10 \cos 2t$ [V], $i(t) = 20(1 - e^{-0.5t})$ [mA]

a) Find the charge in the device at $t = 2.5$ (assume initial charge at $t = 0$ is zero)

$$q = \int_0^{2.5} i(t) dt = \int_0^{2.5} 20(1 - e^{-0.5t}) dt$$

$$= 20 \left[t - \frac{e^{-0.5t}}{-0.5} \right]_0^{2.5} = 20 \left[2.5 + \frac{e^{-1.25}}{0.5} - \frac{1}{0.5} \right]$$

$$= 20 \left[2 + (0.368 - 1) \times 2 \right] = 20(2 - 1.264) = 14.72$$

b) The power consumed by the device at $t = \pi/5$ ms

$$P(t) = v(t) i(t) = 10 \cos(2t) \times 20(1 - e^{-0.5t})$$

$$= 200 \times 0.792 = 158.4 \text{ mW} = 0.1584 \text{ W}$$

Example 1.10

What is the polarity?

Case A: $\ominus 3V$ (Case B: $\oplus 3V$)

is already presented using a loop analysis. Let's try to find V_x . [This is called Nodal Analysis]

Current $i_{2\Omega}$ [A] = $\frac{5 - V_x}{2}$ [V] [Ohm's Law]

$$i_{4\Omega} = \frac{3 - V_x}{4}$$

$$i_{8\Omega} = \frac{V_x}{8}$$

Also $i_{2\Omega} + i_{4\Omega} = i_{8\Omega}$ [Based on Kirchhoff's Current Law]

$$\frac{5 - V_x}{2} + \frac{3 - V_x}{4} = \frac{V_x}{8}$$

$$4(5 - V_x) + 2(3 - V_x) = V_x$$

$$20 + 6 - 4V_x - 2V_x = V_x$$

$$26 = 7V_x \Rightarrow V_x = \frac{26}{7} \text{ [V]}$$

$$i_{2\Omega} = \frac{5 - \frac{26}{7}}{2} = \frac{9}{14} \text{ [A]}$$

$$i_{4\Omega} = \frac{3 - \frac{26}{7}}{4} = -\frac{5}{28} \text{ [A]}$$

means in opposite direction

$$i_{8\Omega} = \frac{\frac{26}{7}}{8} = \frac{13}{28} \text{ [A]}$$

$i_{8\Omega} = i_{2\Omega} + i_{4\Omega}$ (KCL ✓)

Also, power absorbed in 2Ω , 4Ω , 8Ω resistors are:

2Ω case $\rightarrow \frac{9}{14} \text{ A}$

$$P_{2\Omega} = \left[\left(5 - \frac{26}{7} \right) \right] \left[\frac{9}{14} \right]$$

$$= \frac{9}{7} \text{ [V]} \times \frac{9}{14} \text{ [A]} = \frac{81}{98} \text{ [W]}$$

4Ω case $\rightarrow \frac{26}{7} \text{ V}$

$$P_{4\Omega} = \left(\frac{26}{7} - 3 \right) \left[\frac{5}{28} \right] = \frac{2}{7} \times \frac{5}{28} = \frac{10}{196} \text{ [W]}$$

8Ω case $\rightarrow \frac{26}{7} \text{ V}$

$$P_{8\Omega} = \frac{26}{7} \left[\frac{13}{28} \right] = \frac{169}{98} \text{ [W]}$$

Total consumption

$$P_{\text{total}} = \frac{81}{98} + \frac{10}{196} + \frac{169}{98} = \frac{162 + 10 + 338}{196} = \frac{510}{196} = \frac{255}{98} \text{ [W]}$$

conservation (not zero)

Power generated by two voltage sources:

$$P_{5V} = -5 \text{ [V]} \times \frac{9}{14} = -\frac{45}{14} \text{ [W]}$$

negative sign since this is supplied

$$P_{3V} = +3 \text{ [V]} \times \frac{5}{28} = +\frac{15}{28} \text{ [W]}$$

$$\text{Total } P_{5V} + P_{3V} = -\frac{45}{14} + \frac{15}{28} = -\frac{25}{28} \text{ [W]}$$

