

EE101 Lecture #3 Jan 12, 2018

websites <https://courses.soe.ucsc.edu/courses/ee101/winter18/01>

TAs Emily Enlow [eenlow@ucsc.edu](mailto:eenlow@ucsc.edu)  
 Ibrahim Ghossein [ghossein@ucsc.edu](mailto:ghossein@ucsc.edu)  
 Tae Sung Kim [tksim@ucsc.edu](mailto:tksim@ucsc.edu)  
 Tuwin Lam [tuwin@ucsc.edu](mailto:tuwin@ucsc.edu)

Text C.K. Alexander & M.W.O. Sadiku Fundamentals of Electric Circuits

<connect>  
<http://connect.mheducation.com/class/5-Kang-winter2018-mw/5240>

Tutors

Hartley Berman [haberman@ucsc.edu](mailto:haberman@ucsc.edu)  
 LSS

Jeff Chen [jchen120@ucsc.edu](mailto:jchen120@ucsc.edu)

Christopher Magat [cbmagat@ucsc.edu](mailto:cbmagat@ucsc.edu)





Shravya Palavarthi [spalavar@ucsc.edu](mailto:spalavar@ucsc.edu)

Dan Li [dli24@ucsc.edu](mailto:dli24@ucsc.edu)

Graders

Kelly Tu

[kjtu@ucsc.edu](mailto:kjtu@ucsc.edu)

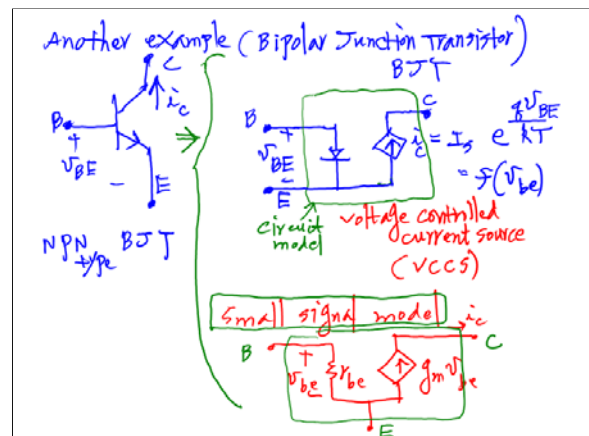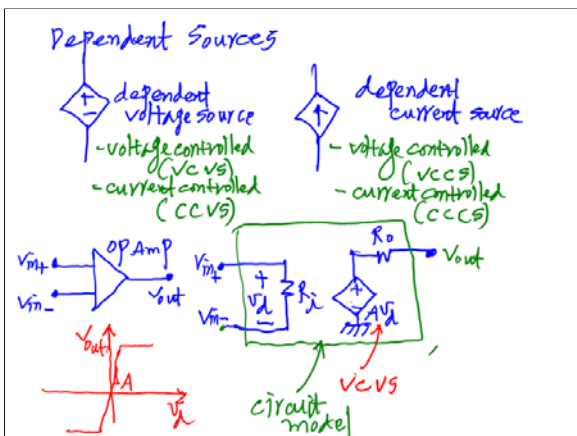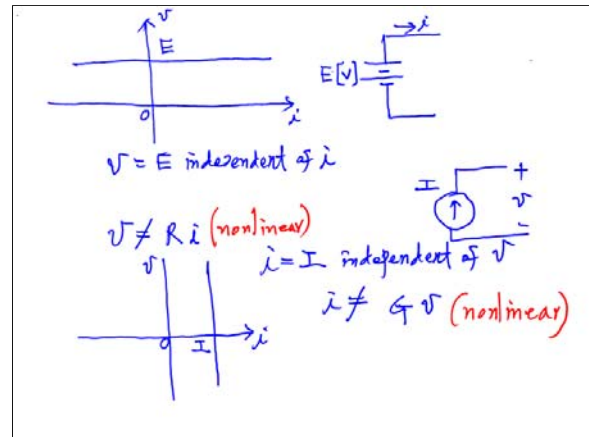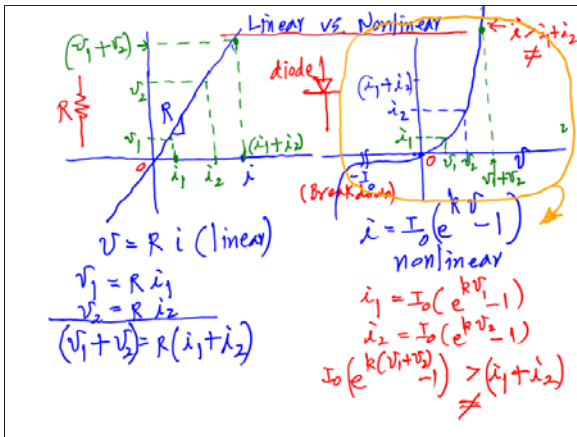

$$q = C v$$

$$q_1 + q_2 = C v_1 + C v_2 = C(v_1 + v_2)$$

$$g = L i$$

$$g_1 + g_2 = L i_1 + L i_2 = L(i_1 + i_2)$$

In general

$$y = f(x) \quad f \text{ linear function}$$

$$y_1 = f(x_1), y_2 = f(x_2)$$

For  $x = a x_1 + b x_2$

$$y = f(a x_1 + b x_2)$$

$$\neq a f(x_1) + b f(x_2) = a y_1 + b y_2$$

( $\rightarrow$  linear)

Complex number

$$z = x + j y$$

$$z = z_m \angle \phi_z$$

$$= \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x} = \phi_z$$

$$= z_m \cos \phi_z + j z_m \sin \phi_z$$

$$z = z_m e^{j \phi_z}$$

$$z_1 = x_1 + j y_1 = z_{1m} \angle \phi_{z1}$$

$$z_2 = x_2 + j y_2 = z_{2m} \angle \phi_{z2}$$

$$z_z = z_1 + z_2 = (x_1 + x_2) + j (y_1 + y_2)$$

$$= \sqrt{(x_1+x_2)^2 + (y_1+y_2)^2} \angle \tan^{-1} \frac{y_1+y_2}{x_1+x_2} = z_{zm} \angle \phi_{zz}$$

$$v = V_m \cos(\omega t + \phi_v)$$

$$= \text{Re}[V_m e^{j(\omega t + \phi_v)}]$$

$$= \text{Re}[V_m (\cos(\omega t + \phi_v) + j \sin(\omega t + \phi_v))]$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$= \text{Re}[V_m e^{j\phi_v} e^{j\omega t}] = \text{Re}[V e^{j\omega t}]$$

$$V = V_m e^{j\phi_v} = V_m \angle \phi_v$$

phasor

Like wise

$$i = I_m \cos(\omega t + \phi_i)$$

$$= \text{Re}[I_m e^{j(\omega t + \phi_i)}]$$

$$= \text{Re}[I_m e^{j\phi_i} e^{j\omega t}]$$

$$= \text{Re}[I e^{j\omega t}]$$

$$I = I_m e^{j\phi_i} = I_m \angle \phi_i$$

phasor

$$V \cdot I = V_m e^{j\phi_v} \cdot I_m e^{j\phi_i} = V_m I_m e^{j(\phi_v + \phi_i)}$$

Linear elements  
 (e.g.) Linear Resistors (series connection)

In this case loop analysis is preferred =  
 only one unknown for given  $V, R_1, R_2, R_3$   
 ohm's law  
 $V = R_1 i + R_2 i + R_3 i = (R_1 + R_2 + R_3) i$   
 $i = V / (R_1 + R_2 + R_3)$

e.g. Linear Resistors (parallel connection)

In this case Nodal Analysis is better than Loop Analysis. ohm's law  
 $I = i_1 + i_2 + i_3 = \frac{V_{N1}}{R_1} + \frac{V_{N1}}{R_2} + \frac{V_{N1}}{R_3}$   
 $= V_{N1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$   
 $V_{N1} = I / \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$

In Ohm's Law  $V = R i$ ,  $R = \text{resistance} [\Omega]$   
 or  $i = \frac{V}{R} = \frac{1}{R} V$   
 $= G V$   
 $G$  is conductance  $[S]$  mho  
 so  $V_{N1} = I / \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$   
 $= I / (G_1 + G_2 + G_3)$   
 $i_1 = \frac{V_{N1}}{R_1} = G_1 V_{N1} = I \left[ \frac{G_1}{G_1 + G_2 + G_3} \right]$

small pipes  
 radius  $r_1, r_2, r_3$   
 (bigger pipe gets more water stream)  
 In this picture  $r_3 > r_2 > r_1$

Revisit of the Example

$i_1 = I \frac{G_1}{G_1 + G_2 + G_3} = \frac{1}{1+2+3} = 1 [A]$   
 $i_2 = I \frac{G_2}{G_1 + G_2 + G_3} = 6 \frac{2}{1+2+3} = 2 [A]$   
 $i_3 = I \frac{G_3}{G_1 + G_2 + G_3} = 6 \frac{3}{1+2+3} = 3 [A]$   
 $I = i_1 + i_2 + i_3$  (✓) (KCL)

Loop (Mesh) current  $i = ?$   
 By Ohm's Law  $i = \frac{V_s}{R_1 + R_2 + R_3} = \frac{120 \cos 120\pi t}{60} = 2 \cos 120\pi t [A]$

Average power in light bulb 1

$$\begin{aligned}
 P_1 &= \frac{1}{T} \int_0^T v_1(t) i_1(t) dt \\
 &= \frac{1}{T} \int_0^T R_1 i_1^2(t) dt \\
 v_1 &= R_1 i_1 = \frac{10}{T} \int_0^T [2 \cos 120\pi t] dt \\
 &= \frac{10 \times 4}{T} \int_0^T \cos^2 120\pi t dt \\
 \cos^2 \theta &= \frac{1}{2}(1 + \cos 2\theta) \\
 &= \frac{40}{T} \left[ \frac{1}{2}T + \frac{1}{2} \int_0^T \cos 240\pi t dt \right] \\
 &= 20 \text{ W}
 \end{aligned}$$

For Light Bulb 2 ( $R_2 = 20 \Omega$ )



$$\begin{aligned}
 P_2 &= \frac{20}{10} [20 \text{ W}] = 40 \text{ W} \\
 P_3 &= \frac{30}{10} [20 \text{ W}] = 60 \text{ W} \\
 \text{Total wattage } P_1 + P_2 + P_3 &= \boxed{120 \text{ W}}
 \end{aligned}$$

If bulbs are connected in parallel



Avg Power in bulb 1

$$\begin{aligned}
 P_1 &= \frac{1}{T} \int_0^T v_s(t) i_1(t) dt = \frac{1}{T} \int_0^T \frac{v_s^2(t)}{R_1} dt \\
 &= \frac{1}{10} \frac{1}{T} \int_0^T [120 \cos 120\pi t]^2 dt \\
 &= \frac{14400}{10T} \left[ \frac{1}{2} \int_0^T (1 + \cos 240\pi t) dt \right] \\
 &= \frac{144}{T} \left[ \frac{1}{2}T + \frac{1}{2} \int_0^T \cos 240\pi t dt \right] \\
 &= 72 \text{ W} \\
 P_2 &= 72 \text{ W} \left( \frac{10}{20} \right) = 36 \text{ W} \quad (P(t) = \frac{v_s^2(t)}{R}) \\
 P_3 &= 72 \text{ W} \left( \frac{10}{30} \right) = 24 \text{ W} \\
 P_1 + P_2 + P_3 &= 72 + 36 + 24 = \boxed{132 \text{ W}}
 \end{aligned}$$

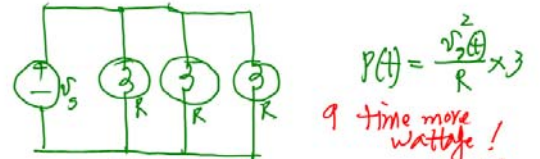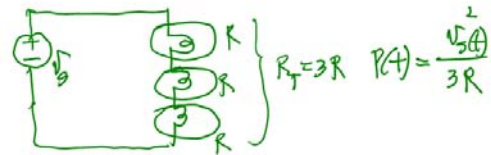

(Light Bulb at home are connected this way)  
 But if too many in parallel then overload (shut off)