
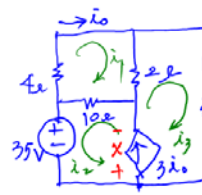


Midterm date change

From Feb 7 (W) to Feb 12 (M)
(new date)

1 Page of formulas/tables allowed.

Quiz #1 Average 7.9/10.0
~ 1.49

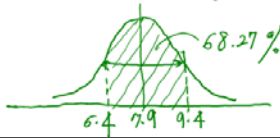

Problem: Find i_0

$$\begin{aligned} \text{Loop 1: } 4i_1 + 2(i_1 - i_2) + 10(i_1 + i_2) &= 0 & (1) \\ \text{Loop 2: } 35 + 10(i_1 + i_2) + X &= 0 & (2) \\ \text{Loop 3: } 2(i_2 - i_1) + 8i_2 + X &= 0 & (3) \end{aligned}$$

$i_0 = i_1$

Let's try to remove X

$$(2) - (3) \rightarrow 35 + 10(i_1 + i_2) + X - 2(i_2 - i_1) - 8i_2 - X = 0$$

$$35 + 12i_1 + 10i_2 - 10i_2 = 0 \quad (4)$$

Also from c.c.c., $i_2 + i_3 = 3i_0 \Rightarrow 3i_1$ (5)

From (5) & (4), $35 + 12i_1 + 10(3i_1) - 10(3i_1 - i_2) = 0$
or $35 - 18i_1 + 20i_2 = 0$ (6)

From (5) & (1) \rightarrow

$$4i_1 + 2(i_1 - (3i_1 - i_2)) + 10(i_1 + i_2) = 0$$

or $10i_1 + 12i_2 = 0$ (7)

In summary $\begin{cases} -18i_1 + 20i_2 = -35 & (6) \\ 10i_1 + 12i_2 = 0 & (7) \end{cases}$

From (7) $i_2 = -\frac{10}{12}i_1 = -\frac{5}{6}i_1$ (8)


From (6) & 8

$$-18i_1 + 20(-\frac{5}{6}i_1) = -35$$

$$(-18 - \frac{50}{3})i_1 = -35$$

$$i_1 = i_0 = \frac{35}{18 + \frac{50}{3}} = \frac{105}{104}$$


Equivalent Resistance

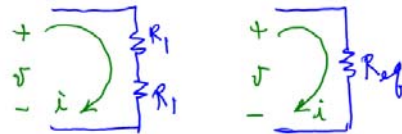

$$V = R_1 i + R_2 i \quad V = R_{eq} i$$


$$= (R_1 + R_2) i$$

$R_{eq} = R_1 + R_2$ (serial connection)

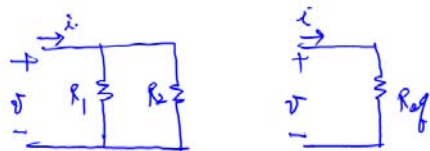

$$i = \frac{V}{R_1} + \frac{V}{R_2}$$

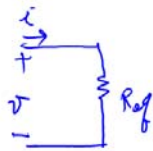
$$= V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$









$$i = \frac{V}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

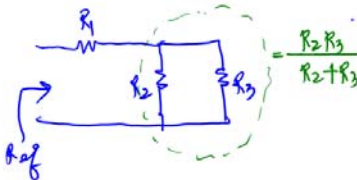$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$ (parallel connection)


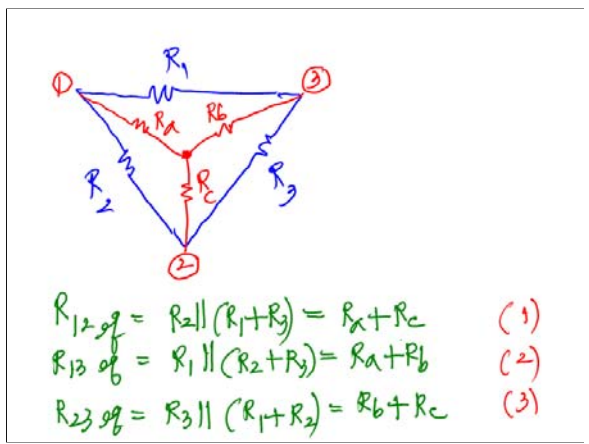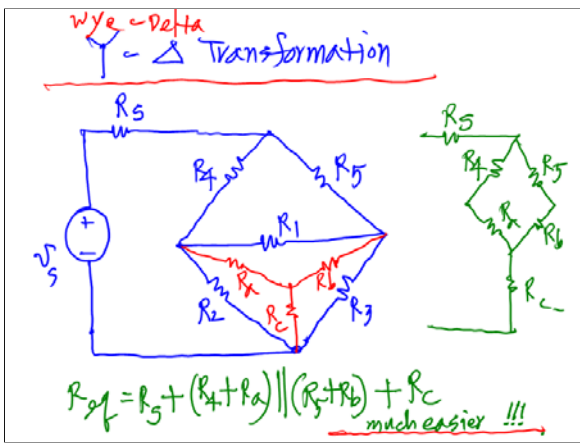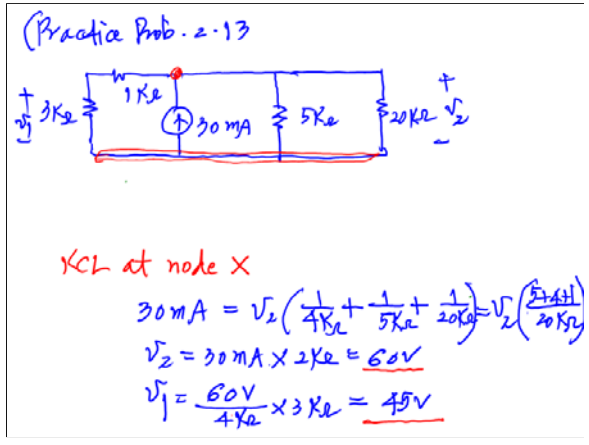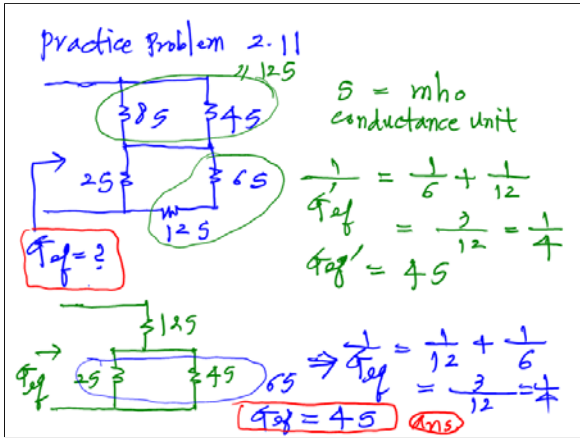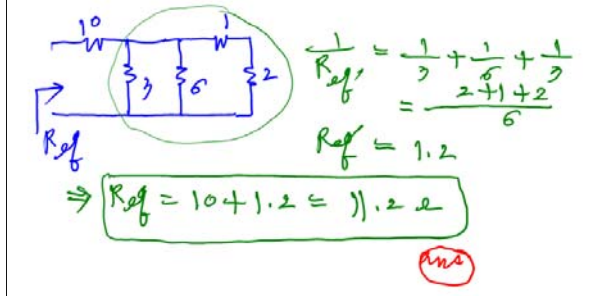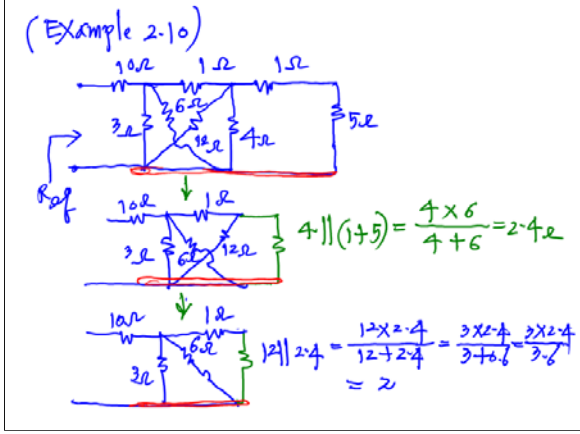
$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$



$$(2) - (1) \Rightarrow R_b - R_c = R_1 \parallel (R_2 + R_3) - R_2 \parallel (R_1 + R_3)$$


$$(3) \quad R_b + R_c = R_3 \parallel (R_1 + R_2) \quad (4)$$

$$(3) + (4) \Rightarrow 2R_b = R_1 \parallel (R_2 + R_3) - R_2 \parallel (R_1 + R_3) + R_3 \parallel (R_1 + R_2)$$

$$R_b = \frac{1}{2} \frac{R_1(R_2 + R_3) - R_2(R_1 + R_3) + R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$= \frac{1}{2} \frac{R_1 R_2 + R_1 R_3 - R_2 R_1 - R_2 R_3 + R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3}$$
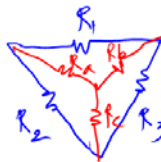
$$= \frac{R_1 R_2}{R_1 + R_2 + R_3} = R_{by}$$



$$R_{by} = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_{cy} = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_{bx} = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$


$$R_{cy} R_{by} + R_{by} R_{cy} + R_{cy} R_{bx} = \frac{R_1 R_2 R_1 R_2 + R_1 R_2 R_3 R_2 + R_2 R_3 R_1 R_3}{R_1 + R_2 + R_3}$$

$$= \frac{R_1 R_2 R_3 (R_1 + R_2 + R_3)}{R_1 + R_2 + R_3} = R_1 R_2 R_3$$

$$R_{1x} = \frac{R_1 R_2 R_3}{R_{cy}}$$

$$R_{2x} = \frac{R_{cy} R_{by} + R_{by} R_{cy} + R_{cy} R_{bx}}{R_{by}}$$
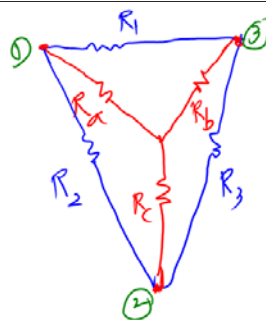
$$R_{3x} = \frac{R_{cy} R_{by} + R_{by} R_{cy} + R_{cy} R_{bx}}{R_{cy}}$$




Wye to Delta
Y to Δ

$$R_{1x} = \frac{R_2 R_3 + R_2 R_1 + R_3 R_1}{R_1}$$

$$R_{2x} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_{3x} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

(Prob 3.43)

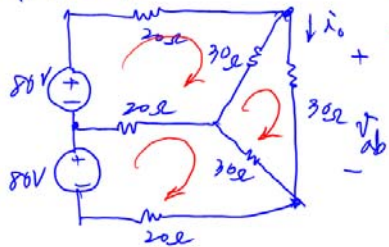

Find v_{ab} & i_0
use Mesh Analysis

example of Δ-Y transformation

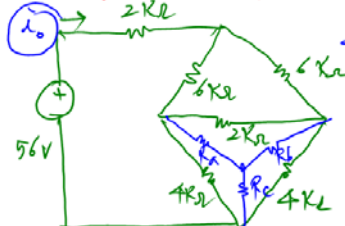

Find i_0

$$i_0 = \frac{56V}{7K} = 8[A]$$

$$R_x = \frac{2K \cdot 4K}{2K + 4K + 4K} = 0.8K\Omega$$

$$R_b = \frac{2K \cdot 4K}{2K + 4K + 4K} = 0.8K\Omega$$

$$R_c = \frac{4K \cdot 4K}{2K + 4K + 4K} = 1.6K\Omega$$

