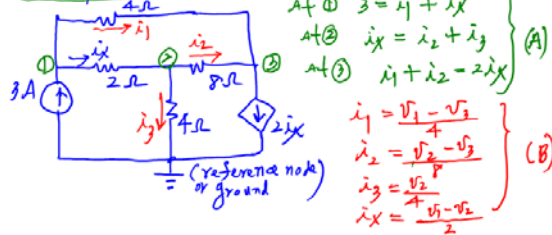


EE101 Lecture #7 Jan 24, 2018  
Further Discussion on Circuit Analysis  
(Nodal Analysis - KCL  
Loop/Mesh Analysis - KVL)

Example 3.2



From (A) & (B)

$$\frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2} = 3 \Rightarrow 3v_1 - 2v_2 - v_3 = 12 \quad (1)$$

$$\frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{2} + \frac{v_2}{4} \Rightarrow 4v_1 - 7v_2 + v_3 = 0 \quad (2)$$

$$\frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{4} = v_1 - v_2 \Rightarrow -2v_1 + 3v_2 - v_3 = 0 \quad (3)$$

In Matrix Form,


$$\begin{bmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ -2 & 3 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

$\tilde{v} = \tilde{b}$

$v_k = \frac{\Delta_k}{\Delta}$   
 $\Delta = |A|$   
 $\Delta_k = |A_k|$   
where  $A_k = A$  with  $k$ th column replaced with  $b$


$$v_2 = \frac{\begin{vmatrix} 3 & -1 & -1 \\ 4 & 1 & 1 \\ -2 & -1 & -1 \end{vmatrix}}{\begin{vmatrix} 3 & -2 & -1 \\ 4 & -7 & 1 \\ -2 & 3 & -1 \end{vmatrix}} = \frac{0 + 0 - 24 - 0 - 0 - (-10) = 24}{21 + (-12) + 4 - (-14) - 9 - 8 = 10} = 2.4 \text{ [V]}$$

Superposition

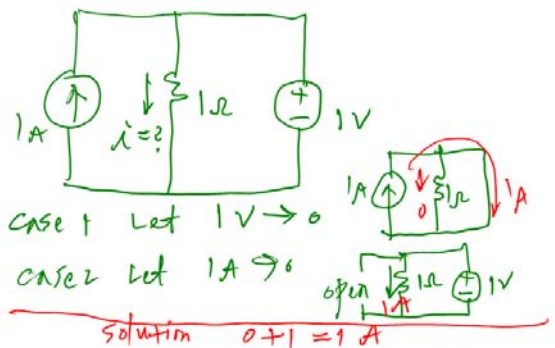


Nodal Analysis with a Supernode

A supernode is formed by enclosing an independent or a dependent voltage source between 2 non-reference nodes and any elements connected in parallel with it.

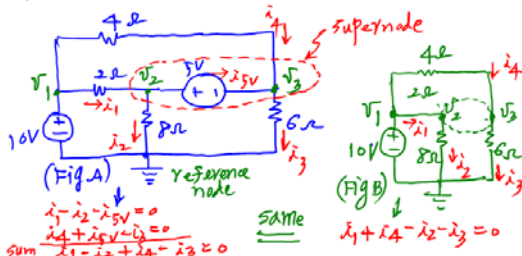


Example 3.4

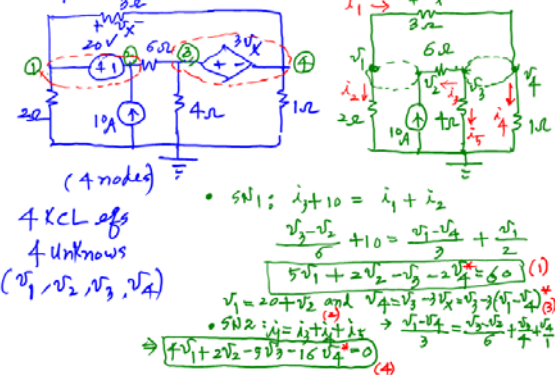

$$\underbrace{\begin{bmatrix} 5 & 2 & -1 & -2 \\ 4 & 2 & -5 & -16 \\ 1 & -1 & 0 & 0 \\ -3 & 0 & 1 & 2 \end{bmatrix}}_{\sim A} \underbrace{\begin{bmatrix} \sqrt{1} \\ \sqrt{2} \\ \sqrt{3} \\ \sqrt{4} \end{bmatrix}}_{\sim \vec{v}} = \underbrace{\begin{bmatrix} 60 \\ 0 \\ 20 \\ 0 \end{bmatrix}}_{\sim \vec{b}}$$

Revisit of a previous Prob. solved

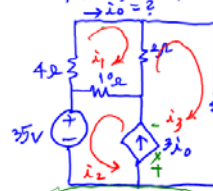

we said the voltage across

CCCS WAS  $X^0$  and removed


<sup>2</sup> by subtracting one eq. from the other.

$$\text{loop 1: } 4\lambda_1 + 2(\lambda_1 - \lambda_2) + 10(\lambda_1 + \lambda_2) = 0 \quad (1)$$

$$100p_2 \quad 35 + 10(\lambda_1 + \lambda_2) + x = 0 \quad (2)$$

$$2(\lambda_3 - \lambda_1) + 8\lambda_3 + x = 0 \quad (3)$$
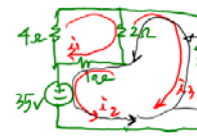
$$-(2) \Rightarrow 15 + 10(\lambda_1 + \lambda_2) - 2(\lambda_3 - \lambda_1) - 8\lambda_3 = 0$$



— This is the loop eq. for (5)

a combined loop

obtained by removing the

(dependent) current source

ined loop branch


$$\underbrace{\begin{bmatrix} 16 & 10 & -2 \\ 12 & 10 & -10 \\ -3 & 1 & 1 \end{bmatrix}}_{\tilde{A}} \underbrace{\begin{bmatrix} \hat{x}_1 \\ \hat{x}_2 \\ \hat{x}_3 \end{bmatrix}}_{\tilde{x}} = \underbrace{\begin{bmatrix} 0 \\ -35 \\ 0 \end{bmatrix}}_{\tilde{b}}$$

$$I_1 = I_o = \frac{|A_1|}{|A|} = \frac{420}{416} = \frac{105}{104} [A]$$

$$|A| = \begin{vmatrix} 16 & 10 & -2 \\ 12 & 10 & -10 \\ -3 & 1 & 1 \end{vmatrix} = 416$$

$$|A_1| = \begin{vmatrix} 0 & 10 & -2 \\ -35 & 10 & -10 \\ 0 & 1 & 1 \end{vmatrix} = 420$$

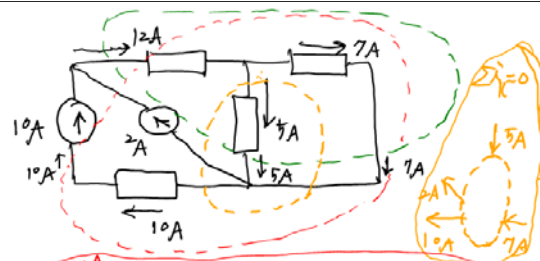same as in the previous solution (lect 6)



$$\sum \dot{V}_i = 0$$

7

↓ 5A

10

2. 木

7A

3

$$= |2 - 5 - 4|$$

$$= 0 \quad \gamma /$$

!

$$\sum_{\text{cutsets } K} \lambda_K = 12 - 2 - 10 = 0$$

$\sum_{\text{cutset } B} \dot{I}_K = 12 - 5 = 7$