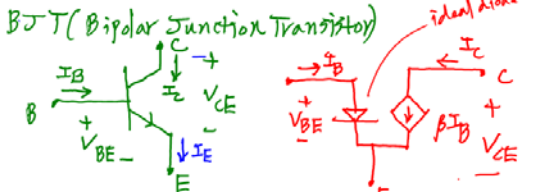


EE101 Lecture #8 Jan 26, 2018  
 Q23 on Jan 27 (M); Q22 returned today.  
 Move on Circuit Analysis  
 (Nodal Analysis - KCL  
 Loop/Mesh Analysis - KVL)



DC equivalent model  
 $I_E = I_B + I_C$   
 $I_B = \frac{I_C}{\beta} + I_C = \left(\frac{\beta+1}{\beta}\right) I_C$   
 $I_C = \frac{\beta}{\beta+1} I_E = \alpha I_E$   
 $\beta = \frac{I_C}{I_B}$


Practice Problem 3.12



For  $\beta = 100$   
 $V_{BE} = 0.7V$   
 Find  $V_o, V_{CE}$


Mesh:  $5V = 10k I_B + 0.7 + 0.2k (101) I_B$   
 $I_B = \frac{5-0.7}{30.2k}$   
 $V_o = 0.2k (101) \cdot \frac{4.3}{30.2k} = \frac{20.2}{30.2} \times 4.3 = 2.876V$

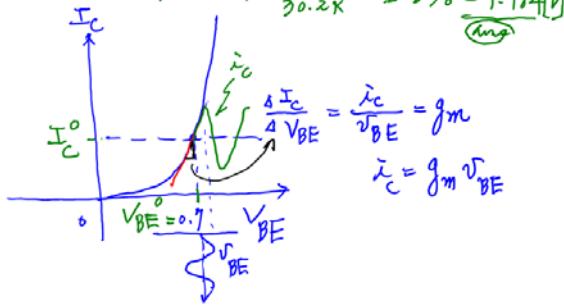$V_{CE} = 12 - 0.15k I_C - V_o$   
 $= 12 - 0.15k (100 I_B) - 2.876$   
 $= 12 - 50k \cdot \frac{4.3}{30.2k} - 2.876 = 1.984V$







At around the bias point  $V_{BE}$ ,  
 $f(V_{BE}^0 + v_{BE}) = I_C^0 + i_c$   
 $f(V_{BE}^0) + f'(V_{BE}^0) v_{BE} + \frac{f''(V_{BE}^0)}{2!} v_{BE}^2 + \dots$   
 $I_C^0 = I_C^0 + i_c$   
 Thus  $i_c = \frac{f'(V_{BE}^0)}{\text{slope at } V_{BE}^0} v_{BE} = g_m v_{BE} = i_c$

Small signal model

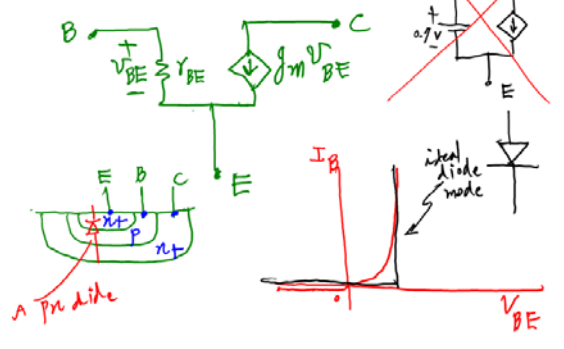

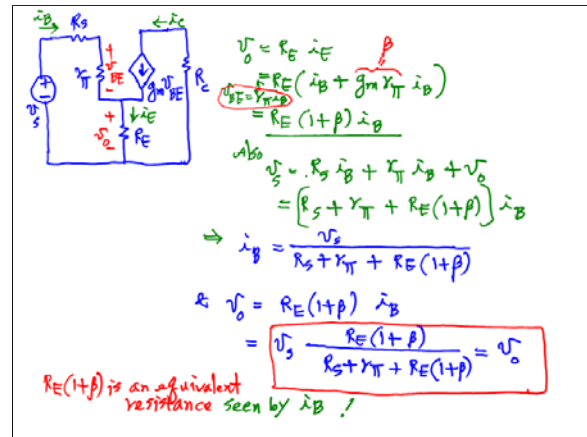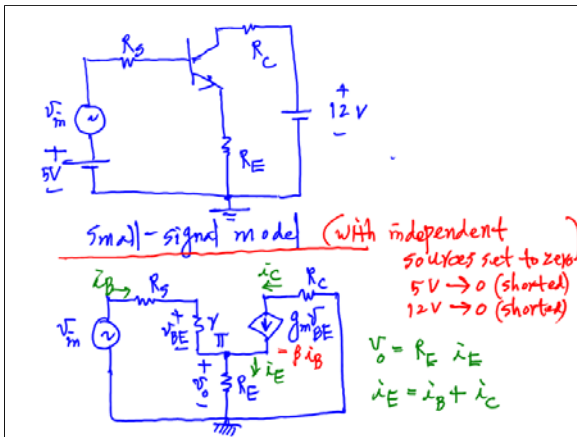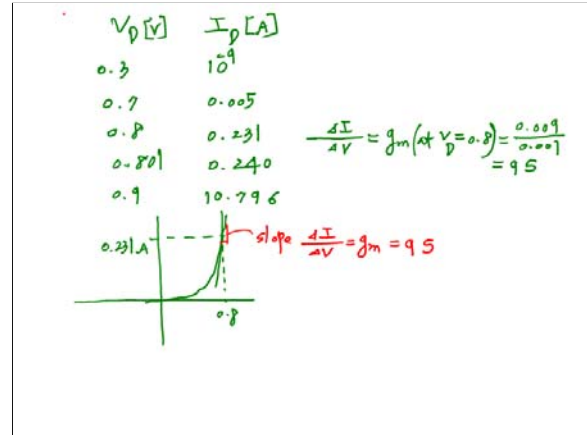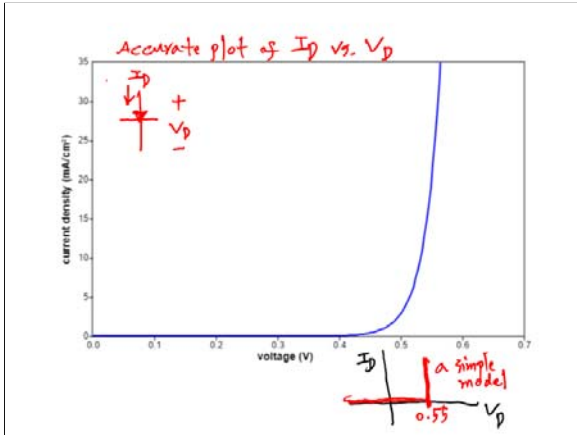diode equation  
 $I_D = I_0 \left( e^{\frac{V_D}{nV_T}} - 1 \right)$   
 $I_0 = \text{saturation current} = 10^{-14} [A]$   
 $V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} J/K (300 K)}{1.6 \times 10^{-19} \text{ Coulomb}}$   
 $= 0.026 [V]$



$$i_B = \frac{v_{in}}{R_S [1 + R_E(1 + g_m r_{\pi})]}$$


$$\Rightarrow v_o = R_E (1 + g_m r_{\pi}) \frac{v_{in}}{R_S [1 + \frac{R_E}{R_S}(1 + g_m r_{\pi})]}$$

$$= v_{in} \frac{R_E (1 + g_m r_{\pi})}{R_S + R_E (1 + g_m r_{\pi})}$$


$$= v_{in} \frac{1}{[1 + \frac{R_E}{R_S(1 + g_m r_{\pi})}]}$$

$R_S = 10 \text{ K}$ ,  $R_E = 0.2 \text{ K}$ ,  $g_m r_{\pi} = \beta = 100$

$$v_o = v_{in} \frac{1}{[1 + \frac{10 \text{ K}}{0.2 \text{ K} (1 + 100)}]} = \frac{v_{in}}{1.5}$$

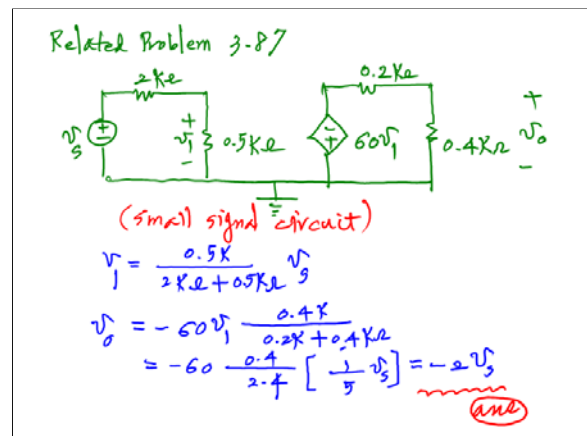

Prob. 3.90

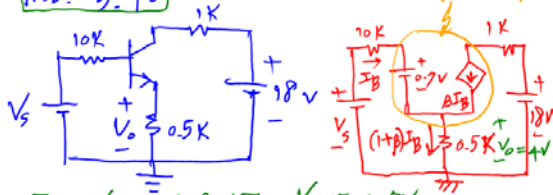

For  $V_o = 4V$ ,  $\beta = 150$ ,  $V_{BE} = 0.7V$   
Find  $V_s$


Solution  $V_s = 10K I_B + 0.7 + 4V$

$I_E = \frac{4}{0.5K} = 8mA = (1+\beta)I_B$

$I_B = \frac{8mA}{151}$

$\Rightarrow V_s = 10K(\frac{8mA}{151}) + 4.7 = \frac{80}{151} + 4.7 = 5.23$  (Ans)

Prob 3.91

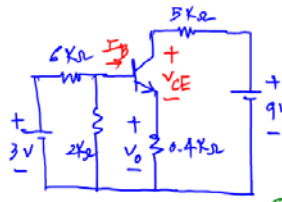

For  $\beta = 200$ ,  $V_{BE} = 0.7V$   
Find  $I_B$  and  $V_{CE}$ ,  $V_o$

solution

$\frac{V_o}{0.4K} = I_B(1+200)$

current through 2k resistor

$I_{2K} = \frac{0.7 + V_o}{2K}$

current through 6k is

$I_{6K} = I_B + I_{2K}$

KVL:  $3V = 6K \cdot I_{6K} + 0.7 + V_o$   
where  $I_{6K} = \frac{V_o}{0.4K(201)} + \frac{0.7 + V_o}{2K}$  solve for  $V_o = 4mV$