


Midterm date change

From Feb 7(W) to ~~Feb 12(M)~~
Today we start Circuit theorems & Quiz 3
(Thevenin's Norton's)

So far we have learned

- Ohm's Law $V = R i$ $i = \frac{1}{R} V = gV$
- KCL (nodal analysis, supernode)
- KVL (Mesh/Loop analysis, supermesh)
- How to Find Ref.
- $\Delta-Y$, $Y-\Delta$ transformation
- BJT circuit (Biasing point, small-signal model)


Motivation Example

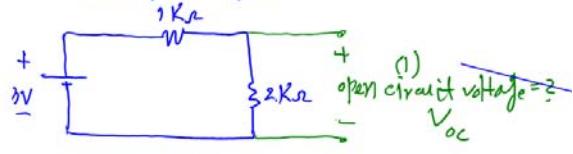


$$3V \xrightarrow{\frac{2k\Omega}{1k\Omega+2k\Omega}} 2V$$

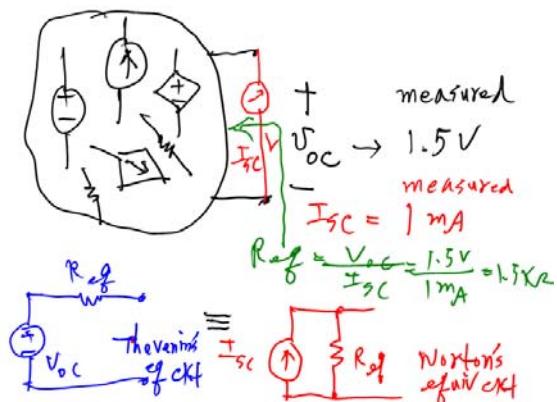(2) equivalent circuit looking into
(set all independent sources = 0)

$$\xrightarrow{\frac{1k\Omega}{1k\Omega+2k\Omega} \leftarrow R_{eq} = \frac{2k\Omega \times 1k\Omega}{2k\Omega + 1k\Omega} = \frac{2}{3}k\Omega}$$




Thevenin's equivalent circuit

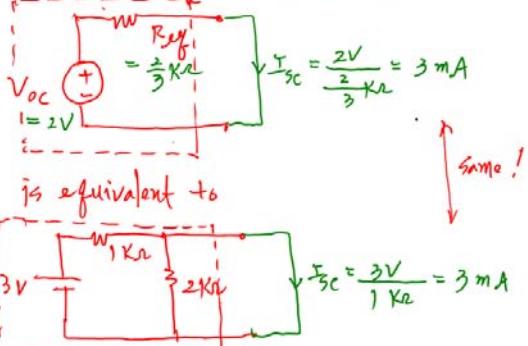

What if we put any resistor to the port?

$$\begin{aligned} &\text{Top Port: } I_{RL} = \frac{2V}{\frac{2}{3}k\Omega + R_L} \\ &\text{Bottom Port: } I_{RL} = \frac{2k\Omega}{R_L + 2k\Omega} I \\ &I = \frac{3}{1k\Omega + \frac{2k\Omega \cdot R_L}{2k\Omega + R_L}} \\ &I_{RL} = \frac{3(2k\Omega + R_L)}{1k\Omega(2k\Omega + R_L) + 2k\Omega R_L} = \frac{3}{1k\Omega + 2k\Omega} = \frac{3}{3k\Omega} = \frac{1}{k\Omega} \end{aligned}$$


Source Transformation

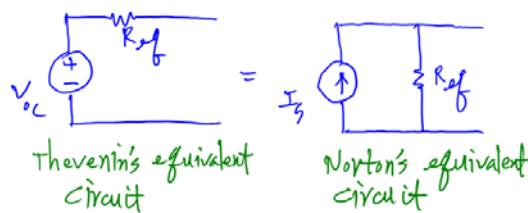

short circuit current

$$\begin{aligned} &V_{oc} = I_{sc} R_{ref} \\ &R_{ref} = R_{eq} \text{ (set input current = 0)} \end{aligned}$$

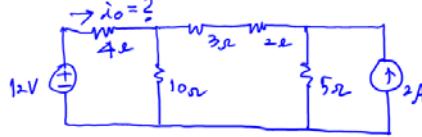Application (Prob. #16) \rightarrow A source removed for simplicity



Let us try to apply the Thévenin's theorem. we find V_{OC} & R_{Ref} w/o 4Ω.

$$V_A = 12V$$

$$V_B = 2A \left(\frac{10+3+2}{15+5} \parallel 5 \right)$$

$$= 2A \cdot \frac{10+3+2}{15+5} \cdot \frac{10}{15+5}$$

$$\text{Thus } V_{OC} = V_A - V_B = 12 - 5 = 7V$$

Next $R_{Ref} = ?$

$$12V \quad \begin{array}{c} 3\Omega \\ \parallel \\ 16\Omega \end{array} \quad \begin{array}{c} 2\Omega \\ \parallel \\ 5\Omega \end{array} \quad 2A$$


$$R_{Ref} = \frac{3+2+2}{10+5} \parallel 5\Omega = 5\Omega$$

$$\text{Thévenin's eq. of. ckt}$$

$$V_{OC} = 7V$$

$$I_o = \frac{7}{5+4} = \frac{7}{9} A \text{ (ans)}$$

Norton's theorem says

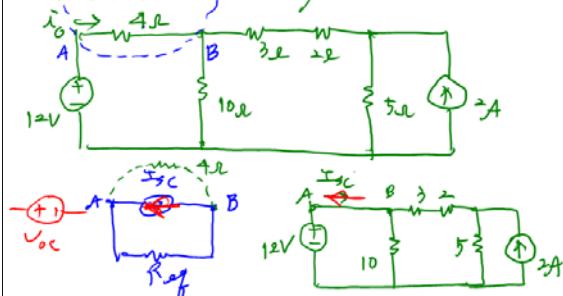

We can find I_{SC} by using the superposition principle, i.e. $I_{SC} = I_{SC_1}(\text{for } 12V \text{ only}) + I_{SC_2}(\text{for } 2A \text{ only})$

$$I_{SC_1} \quad \begin{array}{c} 2\Omega \\ \parallel \\ 5\Omega \end{array} \quad 2A \rightarrow 0$$

$$12V \quad \Rightarrow \quad I_{SC_1} = \frac{12V}{5\Omega} = 2.4A$$

$$I_{SC_2} \quad \begin{array}{c} 3\Omega \\ \parallel \\ 10\Omega \end{array} \quad 10\Omega \quad 2A$$


$$12V \quad \Rightarrow \quad I_{SC_2} = 1A$$

By Superposition

$$I_{SC} = I_{SC_1} + I_{SC_2} = 2.4[A] + (+1[A])$$

$$= 3.4[A]$$

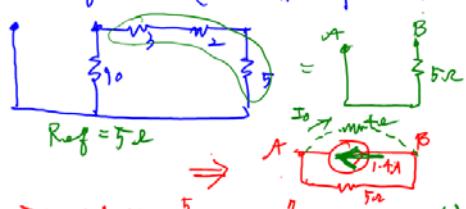Next $R_{Ref} = ?$ (Set all indep. sources = 0)



$$I_o = 1.4 \times \frac{5}{5+4} = \frac{1}{9} A \text{ (same!)}$$

Alternative solution

$$12V \quad \begin{array}{c} 3\Omega \\ \parallel \\ 10\Omega \end{array} \quad \begin{array}{c} 2\Omega \\ \parallel \\ 5\Omega \end{array} \quad 2A$$

$$12V \quad \begin{array}{c} 3\Omega \\ \parallel \\ 10\Omega \end{array} \quad 10V$$

$$5(12-x) = 2x + x - 10$$

$$12 - 5x = \frac{vx}{10} + \frac{v-x-10}{10}$$

$$I_o = (12 - \frac{8x}{9}) / 4 = \frac{12-8x}{9} / 4 = \frac{12}{9} - \frac{2x}{9}$$

$$V_x = \frac{80}{9}$$

$$I_o = \frac{12}{9} - \frac{2x}{9} = \frac{12}{9} - \frac{2x}{9} = \frac{12}{9} - \frac{2x}{9}$$