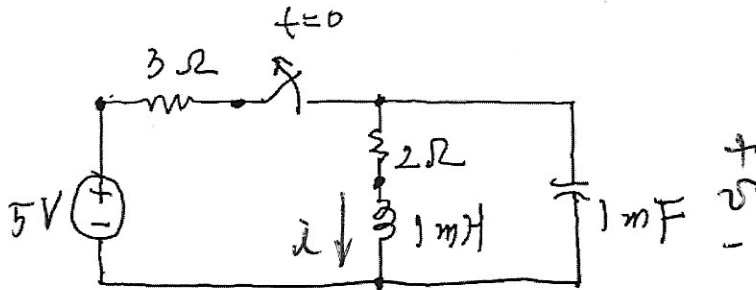


# Solution

EE101 Quiz 9Encore, March 16, 2018

Name \_\_\_\_\_ Student ID \_\_\_\_\_

For a second-order circuit shown below,



- (a) (4 points) Determine the voltage across 1 mF capacitor and the current through 1 mH inductor just before the switch is opened ( $t = 0^-$ ).

$$V(0^-) = \frac{2}{2} \text{ [V]}$$

$$I(0^-) = 1 \text{ [A]}$$

- (b) (2 points) For  $t > 0$ , the second-order circuit is (checked the right case)

Overdamped \_\_\_\_\_

Critically damped

Underdamped \_\_\_\_\_

$$\alpha = \frac{R}{2L} = \frac{2}{2 \times 10^{-3}} = 10^3$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \cdot 10^{-3}}} = 10^3$$

$$\alpha = \omega_0$$

- (c) (4 points) Find the expression for  $V(t)$  for  $t > 0$ . You need to identify the coefficients in the expression by using initial condition.

$$v(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$

$$v(0) = A_1 = 2$$

$$v'(0) = -\alpha A_1 + A_2 = -2000 + A_2 = -1000 \Rightarrow A_2 = 1000$$

$$C \frac{dv'(0)}{dt} = -i(0) \quad \frac{dv'(0)}{dt} = -\frac{1}{10^{-3}} = -10^3$$

$$v(t) = (2 + 1000t) e^{-1000t}$$

$$v(0) = 2 \quad \checkmark$$

$$v'(0) = -2000 + 1000 = -1000 \quad \checkmark$$