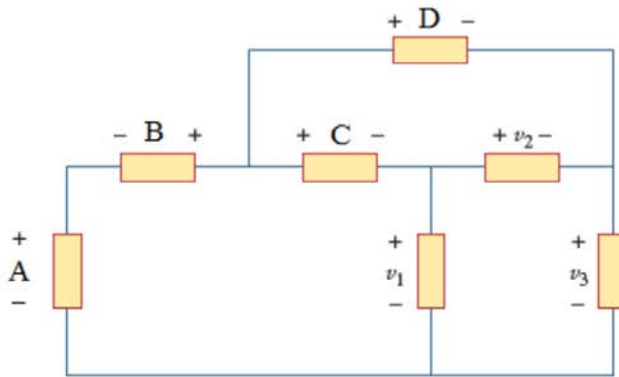


EE101_Quiz 2 January 22, 2018 Solution

NAME _____ ID _____

In the circuit below, voltages are specified to be
 (6 points) $A = 75\text{ V}$, $B = 25\text{ V}$, $C = 30\text{ V}$, $D = 40\text{ V}$.



The unknown voltages v_1 , v_2 , and v_3 are V, V, and V, respectively.

(ans) $v_1 = 25 + 75 - 30 = 70\text{V}$, $v_2 = 40 - 30 = 10\text{V}$, $v_3 = v_1 - v_2 = 70 - 10 = 60\text{V}$

(4 points) If the voltage D is across a $20\ \Omega$ resistor and v_2 is across a $10\ \Omega$ resistor, what is the power consumed in the element with v_3 across it.

$P = \underline{\hspace{2cm}} 180 \underline{\hspace{2cm}} \text{ W}$

$P = v_3 \times i_3 = 60\text{V} \times i_3$

Where $i_3 = i_D + i_{v_2} = 40/20 + 10/10 = 3\text{A}$

Thus $P = 60\text{V} \times 3\text{A} = 180\text{ W}$ (ans)