


solution

EE101 Quiz 9, March 12, 2018

Name _____ Student ID _____

2nd Qz 9
on Friday
March 16 in
the beginning
of the class.

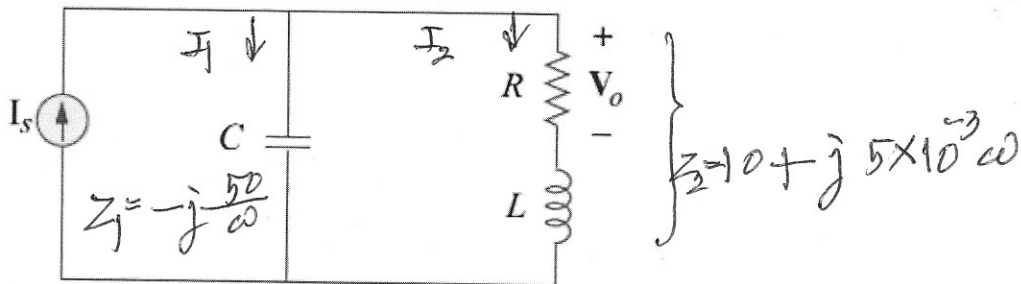For a second-order circuit below with $C = 0.02\text{F}$, $L = 5\text{mH}$ and $R = 10\ \Omega$,



- (a) (6 points) Find the transfer function $H(j\omega) = V_o(j\omega)/I_s(j\omega)$, which is also called a transfer impedance. (Hint: Express $V_o(j\omega)$ in terms of $I_s(j\omega)$ first, then find $H(j\omega)$.)

$$H(j\omega) = \frac{R \times I_2}{I_s} = \frac{R \cdot I_2}{I_1 + I_2} = \frac{10(-j\frac{50}{\omega})}{-j\frac{50}{\omega} + 10 + j(5 \times 10^{-3})\omega} = \frac{10(-j50)}{-j50 + 10\omega + j(5 \times 10^{-3})\omega^2}$$

$$= \frac{10(-j50)}{10\omega + j(5 \times 10^{-3}\omega^2 - 50)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 10^{-3} \times 2 \times 10^{-2}}} = \frac{1}{\sqrt{1 \times 10^{-4}}} = 10^2$$

- (b) (4 points) Find the magnitude of the transfer function $H(j\omega)$ at $\omega = 2\omega_0$, where $\omega_0^2 = 1/(LC)$

$$\omega = 2\omega_0 = 200$$

$$|H(j\omega)|_{\omega=200} = \left| \frac{-j50 \times 10}{10(200) + j(5 \times 10^{-3} \times 4 \times 10^4 - 50)} \right|$$

$$= \left| \frac{-j50 \times 10}{2000 + j150} \right| = \frac{50 \times 10}{100 \sqrt{(200)^2 + (1.5)^2}}$$

$$= \frac{5}{20} = 0.25$$