

- EE101 Lecture 19 Feb 26, 2018
- Quiz 5 Average 8.0,  $\sigma = 1.52$
- Quiz 7 Today
- HW 8 (additional first order ckt problems)


First, a method for analog computing  
 solving an ordinary differential equation

$$\frac{dx}{dt} + a_1 x + a_2 = f(t)$$

$x(0) = x_0$

Solve for  $x(t)$  for given  $x_0, f(t)$

Consider the following OP Amp circuit.

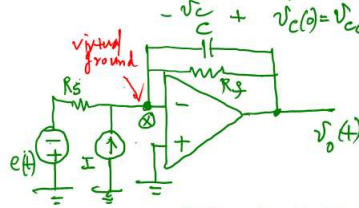

KCL at node X


$$C \frac{dv_o}{dt} + \frac{v_o}{R_f} + I = \frac{e(t)}{R_s}$$

$$\frac{dv_o}{dt} + \frac{v_o}{R_f C} + \frac{I}{C} = \frac{e(t)}{C R_s}$$

$$\frac{dx}{dt} + a_1 x + a_2 = f(t)$$

$x_0 = v_{co}$   
 $x(t) = v_o(t)$   
 $a_1 = \frac{1}{R_f C}$   
 $a_2 = \frac{I}{C}$   
 $f(t) = \frac{e(t)}{C R_s}$

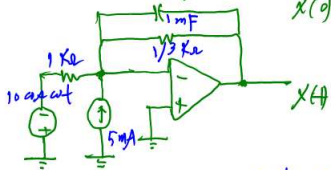Example  $\frac{dx}{dt} + 3x + 5 = 10 \text{ constant}$   
 $x(0) = 3 \text{ V}$




$$a_1 = \frac{1}{R_f C}$$

$$a_2 = \frac{I}{C}$$


$$f(t) = \frac{e(t)}{C R_s}$$

Let  $R_f = \frac{1}{3} \text{ k}\Omega, C = 1 \text{ }\mu\text{F}$ , then  $a_1 = 3$   
 $I = a_2 C = 5 \times 10^{-3} = 5 \text{ mA}$   
 $e(t) = f(t) C R_s$   
 $= 10 \text{ constant } (10^3)(10^{-6})$   
 $R_s = 1 \text{ k}$   
 $= 10 \text{ constant}$


A generic RC, RL circuit

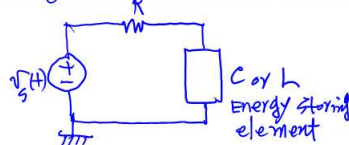


(case 1) capacitor

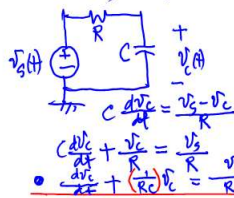

(case 2) Inductor

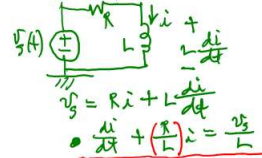

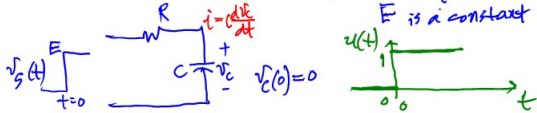A case with  $v_s(t) = E u(t)$ ,  $u(t) = \begin{cases} 1 & t > 0 \\ 0 & t \leq 0 \end{cases}$   
 $E$  is a constant



For  $t > 0$ ,  $RC \frac{dv_c}{dt} + v_c = E$

$$\Rightarrow RC \frac{dv_c}{dt} + (v_c - E) = 0$$

$$\Rightarrow \frac{dv_c}{dt} + \frac{1}{RC}(v_c - E) = 0$$

$$\frac{dv_c}{v_c - E} + \frac{1}{RC} dt = 0 \Rightarrow \frac{d(v_c - E)}{v_c - E} = -\frac{1}{RC} dt$$

Integrating both sides

$$\ln(v_c - E) \Big|_{v_{co}-E}^{v_c-E} = -\frac{t}{RC}$$

$$\Rightarrow \ln \frac{v_c - E}{v_{co} - E} = -\frac{t}{RC}$$

$$v_c(t) - E = (v_{co} - E) e^{-\frac{t}{RC}}$$

$$\frac{v_c - E}{v_{co} - E} = e^{-\frac{t}{RC}}$$

$$= \begin{cases} 1 & t = 0 \\ 0 & t \rightarrow \infty \end{cases}$$

$v_c(t) = E + (v_{co} - E) e^{-\frac{t}{RC}}$  (1)  
 $RC = \tau$  (time constant)  $v_c(\infty) = E$

$e^{-\frac{t}{\tau}}$	$\frac{t}{\tau}$
0.36788	1
0.00674	5

If  $E=0, v_{co} \neq 0$ , then from (1)  
 $v_c(t) = v_{co} e^{-t/RC}$  (2)

$v_s(t) = R i + L \frac{di}{dt}$   
 For  $t > 0$   
 $L \frac{di}{dt} + R i = E$   
 $L \frac{di}{dt} + R i - E = 0$   
 $(\frac{t}{R} - E) di + dt = 0$   
 $\frac{1}{R} \ln(\frac{R i - E}{R i_0 - E}) + \frac{t}{R} = 0$   
 $\ln \frac{R i - E}{R i_0 - E} + \frac{t}{R} = 0$   
 $\Rightarrow R i(t) - E = (R i_0 - E) e^{-\frac{t}{R}}$   
 $i(t) = \frac{E}{R} + (i_0 - \frac{E}{R}) e^{-\frac{t}{R}}$  (3)

Example  
  
 For  $t \leq 0$ ,  $i(t) = 1A$ ,  $i(0) = 1A$   
 For  $t > 0$ ,  
 $200i + 1 \frac{di}{dt} = 100$   
 $i(t) = \frac{E}{R} + (i_0 - \frac{E}{R}) e^{-\frac{t}{RC}}$   
 $= \frac{100}{200} + (1 - \frac{100}{200}) e^{-\frac{t}{200}}$   
 $= 0.5 + 0.5 e^{-\frac{t}{200}}$   
 $i(0) = 0.5 + 0.5 = 1$   
 $i(\infty) = 0.5$

(Example)  
  
 For  $t \leq 0$   
 $v_{OC} = 10 \frac{2}{3+2} = 4V$   
 $R_{eq} = 3 \parallel 2 = \frac{3 \times 2}{3+2} = 1.2\Omega$   
 From (2) for  $v_C$ ,  
 $v(t) = v_{C0} e^{-\frac{t}{RC}}$   
 $= 4 e^{-\frac{t}{(1.2 \times 7F)}}$

Thevenin's of ckt  
  
 $v_C(t) = E + (v_{C0} - E) e^{-\frac{t}{RC}}$   
 $= 4 + (4 - 4) e^{-\frac{t}{RC}}$   
 $= 4$  ? double check

(Example)  
  
 $V_s = 12V$   
 $R = 4\Omega$   
 $L = 6mH$   
 $t_{switch to open} = 1 \mu sec$   
 For  $t \leq 0$ ,  $i = \frac{12V}{4\Omega} = 3A$   
 the voltage across the spark is  
 $L \frac{di}{dt} = L \frac{\Delta i}{\Delta t} = 6 \times 10^{-3} \rightarrow \frac{(3-0)A}{1 \times 10^{-6}s}$   
 $= 18KV$

(Prob 7.54) 5th edition  
  
 For  $t \leq 0$   
 $i = 1A$   
 For  $t > 0$   
 $2A$  source,  $4\Omega$  resistor,  $3.5H$  inductor,  $3\Omega$  resistor,  $3.5H$  inductor,  $6V$  source,  $3.5H$  inductor.

Prob 7.1 (5th ed)

