

(Example)

$V_S = 12V$

$R = 4\Omega$

$L = 6mH$

spark Plug

$t_{\text{switch to open}} = 1 \mu\text{sec}$

For  $t \leq 0$ ,  $i = \frac{12V}{4\Omega} = 3A$

the voltage across the spark is

$$L \frac{di}{dt} = L \frac{\Delta i}{\Delta t} = 6 \times 10^{-3} \rightarrow \frac{(3-0)A}{1 \times 10^{-6}s}$$

$$= 18KV$$

(Prob 7.54) 5th edition

From (a)

$$i(t) = \frac{E}{R} + (i_0 - \frac{E}{R})e^{-\frac{t}{\tau}}$$

$$= \frac{6}{7} + (1 - \frac{6}{7})e^{-\frac{t}{3.5}}$$

$$= \frac{6}{7} + \frac{1}{7}e^{-\frac{t}{3.5}}$$

For  $t \leq 0$

For  $t > 0$

Prob 7.51 (5th ed)

$v(0) = 0, v_s = 3V$

$$v(t) = 6(1 - e^{-\frac{t}{20k \parallel 10k \times 10\mu F}})$$

$$= 6(1 - e^{-5t})$$

Detailed Analysis

KCL at (b)

$$\frac{V_o - V_o}{R_2} + \frac{V_o - V_o}{R_2} = I_o \quad (1)$$

$$e = V_o \frac{R_1 \parallel R_2}{R_2 + R_1 \parallel R_2} = \alpha V_o \quad (2)$$

$$(2) \rightarrow (1) \rightarrow \left[ \frac{\alpha K - 1}{V_o} + \frac{\alpha - 1}{R_2} \right] V_o = I_o$$

$$R_{eq} = \frac{V_o}{I_o} = \frac{R_2}{\alpha - 1} + \frac{\alpha - 1}{\alpha - 1} = \frac{R_2}{\alpha - 1} + 1$$

For  $\alpha K \gg 1, \gamma_o \ll R_2$

$$R_{eq} = \frac{R_2 \gamma_o}{(\alpha K - 1) R_2 + (\alpha - 1) \gamma_o}$$

$$\approx \frac{R_2 \gamma_o}{\alpha K R_2} = \frac{\gamma_o}{\alpha K}$$

For example if  $R_1 = R_2 = 10K$

$\gamma_o = 100\Omega, \gamma_i = 10M\Omega, K = 10^5$

then  $\alpha = \frac{R_1 \parallel R_2}{R_2 + R_1 \parallel R_2} = \frac{10K \parallel 10K}{10K + 10K \parallel 10K} = \frac{1}{2}$

and  $R_{eq} = \frac{\gamma_o}{\alpha K} = \frac{100\Omega}{\frac{1}{2} \times 10^5} = 50 \times 10^{-6} \Omega$

$$v_c(t) = 6(1 - e^{-\frac{t}{20k(10\mu F)}})$$

$$= 6(1 - e^{-5t})$$

Review of Midterm problems +

[1] (a) Find  $i_0$

KCL at  $V_1$  node

$$\frac{10 - V_1}{20} + \frac{V_2 - V_1}{10} = \frac{V_1}{10}$$

KCL at  $V_2$  node (1)

$$\frac{V_1 - V_2}{10} + \frac{10 - V_2}{10} + 2 \frac{V_1}{10} = 0$$

(2)

$$20 \times (1) \rightarrow 10 - V_1 + 2V_2 - 2V_1 = 2V_1$$

$$10 \times (2) \rightarrow 10 - 5V_1 + 2V_2 = 0 \Rightarrow 2V_2 = -10 + 5V_1$$

$$3V_1 - 2V_2 + 10 = 0 \Rightarrow 3V_1 - 2(-10 + 5V_1) + 10 = 0$$

$$3V_1 - (-10 + 5V_1) + 10 = 0 \Rightarrow 8V_1 + 20 = 0 \Rightarrow V_1 = -2.5V$$

$$i_0 = \frac{V_1}{10} = \frac{-2.5}{10} = -0.25A$$

(b) find power consumed by the dependent source & (c) by 20 ohm resistor

(b):  $2i_0 = 2(-0.25) = -0.5A$

$$V_2 = -5 + 2.5V_1 = -5 + 2.5(-2.5) = -11.25V$$

$$P = (-0.5)(-11.25) = 5.625W$$

(c)  $P_{20\Omega} = \frac{(10 - (-2.5))^2}{20} = \frac{12.5^2}{20} = \frac{(2.5)^2}{8} = 7.8125W$

[2] Use superposition principle, find the voltage  $V_{6k\Omega}$  & power

For  $I = 0$

$$V_{6k\Omega} = 3 \frac{6}{3+6} = 2V$$

For  $V = 0$

$$V_{6k\Omega} = 2mA \frac{3 \times 6}{3+6} = 4V$$

$$\Rightarrow V_{6k\Omega} = 2 + 4 = 6V, P = \frac{(6)^2}{6k\Omega} = 6mW$$

[3]  $R_{load}$  for max power transfer = ?

$R = \frac{10 \times 10 + 10 \times 10 + 10 \times 10}{10} = \frac{300}{10} = 30\Omega$

$R_{eq} = 15\Omega$

$$\Rightarrow R_{load} = R_{eq} = 15\Omega$$

[4]

Let's apply a test voltage of 5V

$$R_{eq} = \frac{5V}{0.25mA} = 20k\Omega$$

$V_x = V_{oc}$


$$\frac{5 - V_{oc}}{20k\Omega} = \frac{0.5V_{oc}}{10k\Omega}$$

$$5 - V_{oc} = V_{oc}$$

$$V_{oc} = 2.5V$$

Thevenin's equiv. ckt

[5].

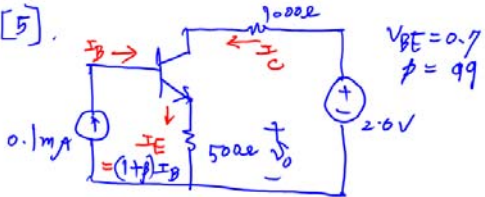

$$I_B = 0.1 \text{ mA} \quad (1 + \beta)I_B = (1 + 99)0.1 \text{ mA} = 10 \text{ mA}$$

$$V_o = 500 \Omega \times 10 \text{ mA} = \underline{5 \text{ V}}$$

$$V_{CE} = 20 - \beta I_B (1 \text{ k}\Omega) - 5 \text{ V}$$

$$= 20 - 5 - 99 \text{ mA} \times 1 \text{ k}\Omega = \underline{6.1 \text{ V}}$$