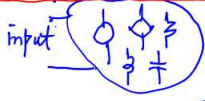


EE101 Lecture #22 May 5, 2018


Quiz 8 today Quiz 7 average 6.5 and 1.15
 Chap 8 second-order circuits




circuit contains both capacitor and inductor elements.

Circuit equations become 2nd-order differential eq.
 $a \frac{d^2x}{dt^2} + b \frac{dx}{dt} + c x = f(t)$
 where x = either voltage across a capacitor or a current through an inductor
 a, b, c depends on R, L, C & dep. sources


Example

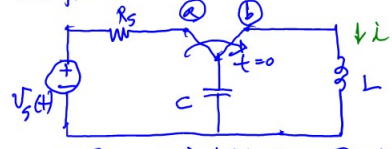

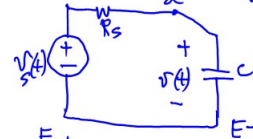Before switching from (a) to (b), $i = 0$



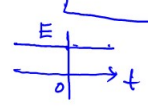
KCL at (a)
 $\frac{E - v}{R_s} = C \frac{dv}{dt}$



$E - v = R_s C \frac{dv}{dt}$
 $E - v = R_s C \left(-\frac{d(E-v)}{dt} \right)$
 $\frac{d(E-v)}{(E-v)} = -\frac{1}{R_s C} dt$

$\frac{d(E-v)}{(E-v)} = -\frac{1}{R_s C} dt$
 Integrating both sides, $\int \frac{dx}{x} = \ln x$
 $\ln(E-v) = -\frac{1}{R_s C} (t - t_{20})$
 and $\ln \frac{E-v(t)}{E-v(t_{20})} = -\frac{1}{R_s C} (t - t_{20})$
 $\Rightarrow E - v(t) = (E - v(t_{20})) e^{-\frac{1}{R_s C} (t - t_{20})}$
 $v(t) = E - (E - v(t_{20})) e^{-\frac{1}{R_s C} (t - t_{20})}$
 At $t=0$ (just before switching from (a) to (b)), $\frac{dv}{dt} = 0$
 $v(0) = E - (E - v(t_{20})) e^{-\frac{1}{R_s C} (\infty)} = E$

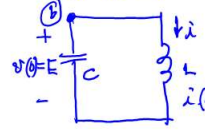For $t > 0$, we have a parallel LC circuit (oscillator)



KCL at (b)
 $C \frac{dv}{dt} + i = 0$ (1)
 $L \frac{di}{dt} = v$ (2)
 $i(0) = 0$

$\frac{d}{dt} (1) \rightarrow C \frac{d^2v}{dt^2} + \frac{di}{dt} = 0$ (3)
 (2) at (3) $\rightarrow C \frac{d^2v}{dt^2} + \frac{v}{L} = 0$

$\frac{d^2v}{dt^2} + \frac{1}{LC} v = 0$

Initial conditions: $v(0) = v(t_{20}) = E$
 $\frac{di}{dt}(0) = \frac{di}{dt}(t_{20}) = -\frac{E}{L}$
 $i(0) = i(t_{20}) = 0 = -C \frac{dv}{dt}(t_{20}) = -C \frac{dv}{dt}(0)$
 $\frac{dv}{dt}(0) = \frac{E}{L}$

To derive a characteristic equation of the circuit, put $v(t) = e^{st}$, then

$\frac{d^2v}{dt^2} + \frac{1}{LC} v = 0 \rightarrow s^2 e^{st} + \frac{1}{LC} e^{st} = 0$
 $\rightarrow \boxed{s^2 + \frac{1}{LC} = 0}$ $s^2 = -\frac{1}{LC}$
 $s_1, s_2 = \pm \sqrt{-\frac{1}{LC}} = \pm j \frac{1}{\sqrt{LC}}$
 $\frac{1}{\sqrt{LC}} = \omega_0$

$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
 $= A_1 e^{+j\omega_0 t} + A_2 e^{-j\omega_0 t}$
 $v(0) = A_1 + A_2 = E$
 $v'(0) = 0 = +j\omega_0 A_1 - j\omega_0 A_2 = 0$
 $\Rightarrow A_1 = A_2 = \frac{E}{2}$

$\Rightarrow v(t) = \frac{E}{2} \left[e^{j\omega_0 t} + e^{-j\omega_0 t} \right]$
 $= E \left(\frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} \right) = E \cos \omega_0 t$


Laplace Transform method (Ref Table 15.1 textbook)

$$s^2 V(s) - sV(0+) - V'(0+) + \frac{1}{LC} V(s) = 0$$

$$(s^2 + \frac{1}{LC}) V(s) = sV(0+) + V'(0+)$$

$$= sE + 0$$

$$V(s) = \frac{s}{s^2 + \frac{1}{LC}} E = \frac{s}{s^2 + \omega_0^2} E$$

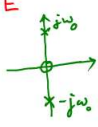$\downarrow \mathcal{L}^{-1}$ $(\omega_0 = \frac{1}{\sqrt{LC}})$ 

$$v(t) = E \cos \omega_0 t$$

$$v(0) = E \quad (v)$$

$$v'(0) = -\omega_0 E \sin \omega_0 t \Big|_{t=0} = 0 \quad (v')$$

Solution of $\frac{d^2 v}{dt^2} + \frac{1}{LC} v = 0$

When $v(t) = A \cos(\omega t + \theta)$

$$\frac{dv}{dt} = -\omega A \sin(\omega t + \theta)$$

$$\frac{d^2 v}{dt^2} = -\omega^2 A \cos(\omega t + \theta)$$

$$\rightarrow -\omega^2 A \cos(\omega t + \theta) + \frac{1}{LC} A \cos(\omega t + \theta) = 0$$

$$\rightarrow \omega^2 = \frac{1}{LC} \Rightarrow \omega = \pm \frac{1}{\sqrt{LC}}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$v(t) = A \cos(\frac{1}{\sqrt{LC}} t + \theta)$$

$$v(0) = E = A \cos \theta \rightarrow \text{for any } \theta \Rightarrow \theta = 0, A = E$$

$\rightarrow v(t) = E \cos \omega_0 t$

Series RLC circuit

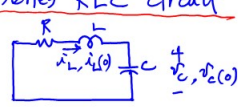

$$v_C(0) = \frac{1}{C} \int_0^0 i_L(\tau) d\tau \quad (1)$$

$$i_L(t) = i_L(t) \quad (2)$$

$$i_L(t)|_{t=0} = i_L(0)$$

KVL, $R i_L + L \frac{di_L}{dt} + \frac{1}{C} \int_0^t i_L(\tau) d\tau \quad (3)$

Taking $\frac{d}{dt}$ on both sides,

$$L \frac{d^2 i_L}{dt^2} + R \frac{di_L}{dt} + \frac{1}{C} i_L(t) = 0 \quad (4)$$

At $t=0$, from (3) $R i_L(0) + L \frac{di_L(0)}{dt} + v_C(0) = 0$

$$\frac{di_L(0)}{dt} = -\frac{1}{L} (R i_L(0) + v_C(0)) \quad (5)$$

For $i_L(t) = A e^{st}$,

$$(4) \rightarrow L s^2 A e^{st} + R s A e^{st} + \frac{1}{C} A e^{st} = 0$$

$$\Rightarrow (L s^2 + R s + \frac{1}{C}) = 0 \text{ or } s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Characteristic Equation

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s^2 + 2(\frac{R}{2L}) s + [\frac{1}{LC} - (\frac{R}{2L})^2] + (\frac{R}{2L})^2 = 0$$

$$(s + \frac{R}{2L})^2 - [\frac{R}{2L}]^2 + \frac{1}{LC} = 0$$

$$(s + \frac{R}{2L} + \sqrt{[\frac{R}{2L}]^2 - \frac{1}{LC}})(s + \frac{R}{2L} - \sqrt{[\frac{R}{2L}]^2 - \frac{1}{LC}}) = 0$$


$$\Rightarrow s_{1,2} = -\frac{R}{2L} \pm \sqrt{[\frac{R}{2L}]^2 - \frac{1}{LC}}$$

Let $\frac{R}{2L} = \alpha$, $\frac{1}{LC} = \omega_0^2$, then

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

- 1) If $\alpha > \omega_0$ ($\frac{R}{2L} > \frac{1}{\sqrt{LC}}$) then $s_{1,2}$ both are negative real (over damped)
- 2) If $\alpha = \omega_0$ $s_{1,2} = -\alpha$ (critically damped)
- 3) If $\alpha < \omega_0$ $s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$ (under damped)

1) For $\alpha > \omega_0$ over damped

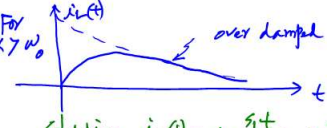

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$\alpha = \frac{R}{2L}$$

Solution $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$i_L(0) = A_1 + A_2$$

$$i_L'(0) = A_1 s_1 + A_2 s_2$$

3) For $\alpha < \omega_0$ under damped

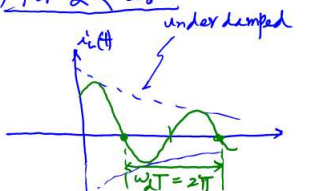


$$s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$$i_L(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$\sqrt{\omega_0^2 - \alpha^2} = \omega_d$$

$$= e^{-\alpha t} [A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}]$$


$$= e^{-\alpha t} [A_1 \cos \omega_d t + j A_1 \sin \omega_d t + A_2 \cos \omega_d t - j A_2 \sin \omega_d t]$$
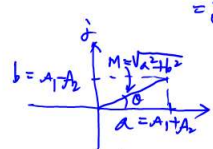
$$= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$


$$= e^{-\alpha t} [M \cos(\omega_d t + \theta) + j M \sin \omega_d t]$$

$$= e^{-\alpha t} M \cos(\omega_d t + \theta) = i_L(t)$$

Use $i_L(0) = A_1 + A_2$
 $i_L'(0) = A_1 s_1 + A_2 s_2$ solve for A_1, A_2

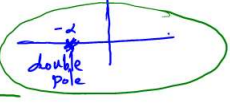3) For $\alpha = \omega_0$
 $s_1, s_2 = -\alpha$ 

$i_L(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$

$i_L(0) = A_2 = 5$
 $i_L'(0) = A_1 + (-\alpha)A_2 = 0$
 $\Rightarrow A_1 - 5\alpha = 0 \Rightarrow A_1 = 5\alpha = 5$

An Alternative Approach (using Laplace Transform)

$L[s i_L(s) - i_L(0)] + \frac{1}{s} I(0) = 0$
 where $i_L(0) = 5$
 $(Ls^2 + Rs + \frac{1}{C}) i_L(s) = L i_L(0) + \frac{1}{s} I(0)$
 $i_L(s) = \frac{Ls i_L(0) + \frac{1}{s} I(0)}{Ls^2 + Rs + \frac{1}{C}} = \frac{5s + \frac{5}{10}}{s^2 + 5s + 1}$

Partial Fraction Decomposition:
 $\frac{5s + 0.5}{(s + \alpha)^2} = \frac{K_1}{s + \alpha} + \frac{K_2}{(s + \alpha)^2}$
 $a = i_L(0) = 5, b = i_L'(0) + \alpha i_L(0) = -10/10 = -1$

$I_L(s) = \frac{K_1}{(s+\alpha)^2} + \frac{K_2}{s+\alpha}$
 $\downarrow e^{-\alpha t}$
 $i_L(t) = K_1 t e^{-\alpha t} + K_2 e^{-\alpha t}$ Eq (**)

$i_L(0) = K_2 = 5$
 $i_L'(0) = K_1 + (-\alpha)K_2 = 0$
 $\Rightarrow K_1 - 5\alpha = 0 \Rightarrow K_1 = 5\alpha = 5$


thus $K_1 = i_L'(0) + K_2 \alpha = \frac{d}{dt} i_L(0) + i_L(0) \alpha$

$i_L(t) = [i_L'(0) + i_L(0) \alpha] t e^{-\alpha t} + i_L(0) e^{-\alpha t}$

(Example) $R = 40 \Omega, L = 20 \text{ mH}, C = \frac{1}{20} \text{ F}, i_L(0) = 5$
 then $\frac{R}{2L} = \frac{1}{C} = \alpha = 1$
 $i_L'(0) = 0$
 then $i_L(t) = 5(1+t)e^{-t} = 5(t+1)e^{-t}$


$\frac{20 \text{ V}}{10 \text{ F}} \rightarrow i_L(0) = 5$

$20 i_L + 10 \frac{di_L}{dt} + \frac{1}{10} i_L = 0$
 $20 \frac{di_L}{dt} + 10 \frac{d^2 i_L}{dt^2} + i_L = 0$

for $i_L(t) = e^{st}$, characteristic eq.
 $20s^2 + 10s + 1 = 0$
 $\Rightarrow s^2 + 2s + 1 = (s+1)^2 = 0$ 


$i_L(t) = A_1 t e^{-t} + A_2 e^{-t}$
 $i_L(0) = A_2 = 5$
 $i_L'(0) = A_1 + (-1)A_2 = 0 \Rightarrow A_1 = A_2 = 5$
 $i_L(t) = 5t e^{-t} + 5e^{-t} = 5(t+1)e^{-t}$ **Ans**

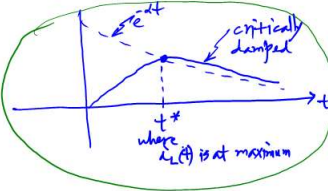$I_L(s) = \frac{K_1}{(s+\alpha)^2} + \frac{K_2}{s+\alpha} \xrightarrow{e^{-\alpha t}} i_L(t) = K_1 t e^{-\alpha t} + K_2 e^{-\alpha t}$



$i_L(0) = K_2$
 Also i_L^{max} occurs when $\frac{di_L(t)}{dt} = 0$
 $\Rightarrow K_1 - K_1 \alpha t - K_2 \alpha = 0$
 thus $t^* = \frac{K_1 - K_2 \alpha}{K_1 \alpha} = \frac{1}{\alpha} - \frac{K_2}{K_1}$
 where $K_1 = i_L'(0) + i_L(0) \alpha$

Example

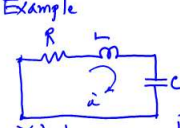

$R = 40 \Omega, L = 4 \text{ H}, C = \frac{1}{4} \text{ F}$

$R_1 + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$
 $R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$
 $(Ls^2 + Rs + \frac{1}{C}) I(s) = 0$
 $I(s) = \frac{F(s)}{Ls^2 + Rs + \frac{1}{C}}$

1) Calculate the characteristic roots of the circuit. $s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + 10s + 25 = (s+5)^2 = 0$
 2) Is it over damped, underdamped or critically damped? $\alpha = 5, \omega_0 = 5$
 $\alpha = \omega_0 \Rightarrow$ critically damped.

$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$
 $= -5 \pm \sqrt{25 - 25} = -5 \pm 0 = -5$

$\frac{R}{2L} = \frac{40}{8} = 5 = \alpha$
 $\frac{1}{LC} = \frac{1}{4 \times \frac{1}{4}} = 1 = \omega_0^2$
 $\alpha^2 - \omega_0^2 = 25 - 25 = 0 > 0$ (over damped)


$i(t) = A_1 e^{-0.9t} + A_2 e^{-9.1t}$
 $i(0) = A_1 + A_2$
 $i'(0) = -0.9A_1 - 9.1A_2 = -10$

$A_1 + A_2 = 1$ (1)
 $-0.9A_1 - 9.1A_2 = -10$ (2)
 $\times 2 \rightarrow -1.8A_1 - 18.2A_2 = -20$ (3)

(1) + (3) $\Rightarrow 0 - 18A_2 = -19 \Rightarrow A_2 = \frac{19}{18}$
 $A_1 = 1 - \frac{19}{18} = \frac{1}{18}$
 $-1.8 \left(\frac{1}{18}\right) - 19 \left(\frac{19}{18}\right) = \frac{1 - 361}{18} = -20 \checkmark$

$i(t) = \frac{1}{18} e^{-0.9t} + \frac{19}{18} e^{-9.1t}$ **Ans**

Parallel RLC circuit

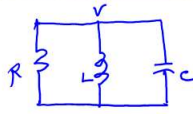

In series RLC circuit the loop current is common to all elements. (same)

In parallel RLC circuit, the node voltage is common. (same)

$$KCL \Rightarrow \frac{V}{R} + \frac{1}{L} \int V(t) dt + C \frac{dV}{dt} = 0$$

$$\text{Taking } \frac{d}{dt} \rightarrow \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2 V}{dt^2} = 0$$

$$\text{dividing by } C \rightarrow \frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

$$\text{for } V = e^{st}, \left[s^2 + \frac{1}{RC} s + \frac{1}{LC} \right] e^{st} = 0$$

$$\text{Thus } \boxed{s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0} \leftrightarrow \boxed{s^2 + \frac{R}{L} s + \frac{1}{LC} = 0} \text{ series ext}$$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$\text{Let } \alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{Then } s^2 + 2\alpha s + \omega_0^2 = 0$$

$$(s + \alpha)^2 - (\alpha^2 - \omega_0^2) = 0$$

$$(s + \alpha + \sqrt{\alpha^2 - \omega_0^2})(s + \alpha - \sqrt{\alpha^2 - \omega_0^2}) = 0 \quad \boxed{s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}}$$

1) If $\alpha > \omega_0$, then s_1, s_2 are both negative, real.



Overdamped

2) If $\alpha = \omega_0$, then $s_1, s_2 = -\alpha$ (double root)




Critically damped

3) If $\alpha < \omega_0$, then $s_1, s_2 = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$



underdamped

Dual circuit

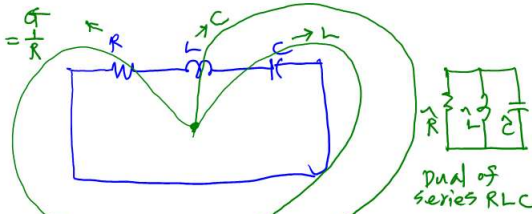


Dual of series RLC

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$\Rightarrow \boxed{\hat{L} = L, \hat{R} = \frac{1}{R}, \hat{C} = C}$$

Example

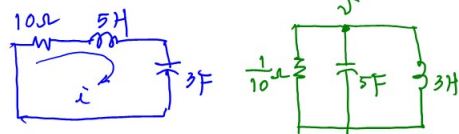

$$10i + 5 \frac{di}{dt} + \frac{1}{3} \int i(t) dt = 0$$

$$\frac{v}{(1/10)} + 5 \frac{dv}{dt} + \frac{1}{3} \int v(t) dt = 0$$

$$\boxed{5 \frac{d^2 i}{dt^2} + 10 \frac{di}{dt} + \frac{1}{3} i = 0}$$

$$10v + 5 \frac{dv}{dt} + \frac{1}{3} \int v(t) dt = 0$$

$$5s^2 + 10s + \frac{1}{3} = 0$$

$$\boxed{5 \frac{d^2 v}{dt^2} + 10 \frac{dv}{dt} + \frac{1}{3} v(t) = 0}$$

$$\leftrightarrow \text{same! } 5s^2 + 10s + \frac{1}{3} = 0$$

TABLE 8.1

Dual pairs.

Resistance R	Conductance G
Inductance L	Capacitance C
Voltage v	Current i
Voltage source	Current source
Node	Mesh
Series path	Parallel path
Open circuit	Short circuit
KVL	KCL
Thevenin	Norton

Two circuits that are described by equations of the same form, but in which the variables are interchanged, are said to be dual to each other.

Two circuits are said to be duals of one another if they are described by the same characterizing equations with dual quantities interchanged.