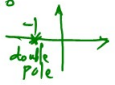
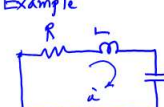



EE101 Lecture # 23 May 7, 2018

- Problem Solving session on March 17, Sat.
The time and place to be announced
- Course review on March 16 (F)
- Final Exam (12 problems) $\frac{3 \text{ hrs} = 180 \text{ min}}{12} = 15 \text{ min}$ Prob.
You are allowed to use 2 pages of formulas and tables only, not concepts, Prob. soln
Coverage: chapters 1-8, 13 (transformer, coupled inductors)
14 (14.2 ~ 14.4 Bode plots)

$\frac{20e^{-t} \cos 10t}{s^2 + 10s + 100} + \frac{1}{s} \cdot 5 = 0$
 $\Rightarrow \frac{20s}{s^2 + 10s + 100} + \frac{1}{s} \cdot 5 = 0$
 $\Rightarrow 20s + 10s^2 + 100 = 0$
 $\Rightarrow s^2 + 2s + 1 = (s+1)^2 = 0$ 
 $i_L(t) = A_1 t e^{-t} + A_2 e^{-t}$
 $\bullet i_L(0) = A_2 = 5$
 $\bullet i_L'(0) = A_1 e^{-t} + A_1(-1)e^{-t} - A_2 e^{-t} \Big|_{t=0} = 0$
 $= A_1 - A_2 = 0 \Rightarrow A_1 = A_2 = 5$
 $i_L(t) = 5t e^{-t} + 5e^{-t} = 5(t+1)e^{-t}$ **Ans**

Example

 $R = 40 \Omega$
 $L = 4 \text{ H}$
 $C = \frac{1}{4} \text{ F}$
 $i(0) = 1$
 $i'(0) = -10$
 1) Calculate the characteristic roots of the circuit. $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$
 $s^2 + 10s + 25 = 0$
 2) Is it over damped, underdamped or critically damped?
 $\alpha = \frac{R}{2L} = 5$
 $\omega_0 = \frac{1}{\sqrt{LC}} = 5$
 $\alpha^2 - \omega_0^2 = 25 - 25 = 0$ (critically damped)
 $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm 0 = -5$
 $i(t) = A_1 e^{-5t} + A_2 t e^{-5t}$
 $i(0) = A_1 = 1$
 $i'(0) = -5A_1 + A_2 = -10 \Rightarrow A_2 = -5$
 $i(t) = (1 - 5t)e^{-5t}$

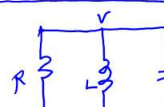$A_1 + A_2 = 1$ (1)
 $-0.5A_1 - 9.5A_2 = -10$ (2)
 $\rightarrow -A_1 - 19A_2 = -20$ (2')
 $(1) + (2') \rightarrow 0 - 18A_2 = -19 \Rightarrow A_2 = \frac{19}{18}$
 $A_1 = 1 - \frac{19}{18} = -\frac{1}{18}$
 $i(t) = -\frac{1}{18} e^{-0.5t} + \frac{19}{18} e^{-9.5t}$ **Ans**
 $i(0) = -\frac{1}{18} + \frac{19}{18} = 1$ ✓
 $i'(0) = +\frac{0.5}{18} - \frac{19 \times 9.5}{18} = \frac{0.5 - 180.5}{18} = -10$ ✓
 Both check out, thus the ans above is correct.

Parallel RLC circuit

 In series RLC circuit the loop current is common to all elements. (same)
 In parallel RLC circuit, the node voltage is common. (same)
 $KCL \Rightarrow \frac{v}{R} + \frac{1}{L} \int v dt + C \frac{dv}{dt} = 0$
 Taking $\frac{d}{dt} \rightarrow \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v + C \frac{d^2 v}{dt^2} = 0$
 dividing by C $\rightarrow \frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$
 for $v = e^{st}$, $[s^2 + \frac{1}{RC}s + \frac{1}{LC}] e^{st} = 0$
 Thus $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \Leftrightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$
 Let $\alpha = \frac{1}{2RC}$, $\omega_0 = \frac{1}{\sqrt{LC}}$
 Then $s^2 + 2\alpha s + \omega_0^2 = 0$
 $(s + \alpha)^2 - (\alpha^2 - \omega_0^2) = 0$
 $(s + \alpha + \sqrt{\alpha^2 - \omega_0^2})(s + \alpha - \sqrt{\alpha^2 - \omega_0^2}) = 0$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
 1) If $\alpha > \omega_0$, then s_1, s_2 are both negative, real. **Overdamped**
 $\leftarrow \begin{array}{c} * \\ * \end{array}$
 2) If $\alpha = \omega_0$, then $s_1, s_2 = -\alpha$ (double root) **critically damped**
 $\leftarrow *$
 3) If $\alpha < \omega_0$, then $s_1, s_2 = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$
 $\leftarrow \begin{array}{c} * + j\omega_d \\ * - j\omega_d \end{array}$ **underdamped**

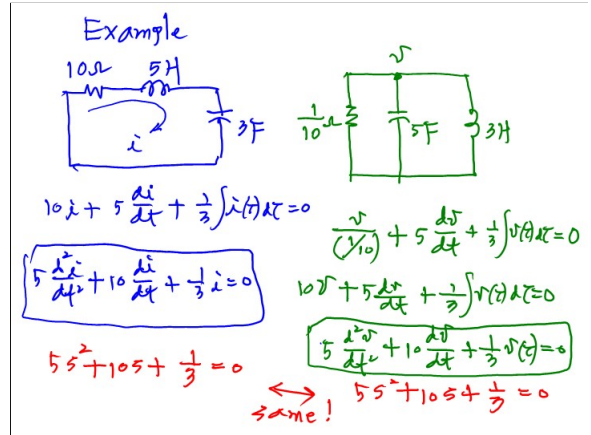
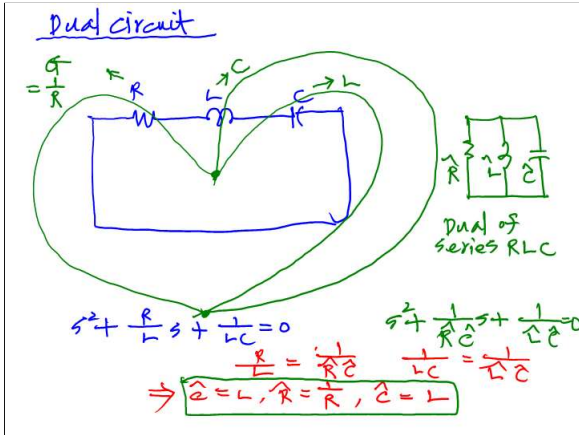



TABLE 8.1

Dual pairs.

Resistance R	Conductance G
Inductance L	Capacitance C
Voltage v	Current i
Voltage source	Current source
Node	Mesh
Series path	Parallel path
Open circuit	Short circuit
KVL	KCL
Thevenin	Norton

Two circuits that are described by equations of the same form, but in which the variables are interchanged, are said to be dual to each other.

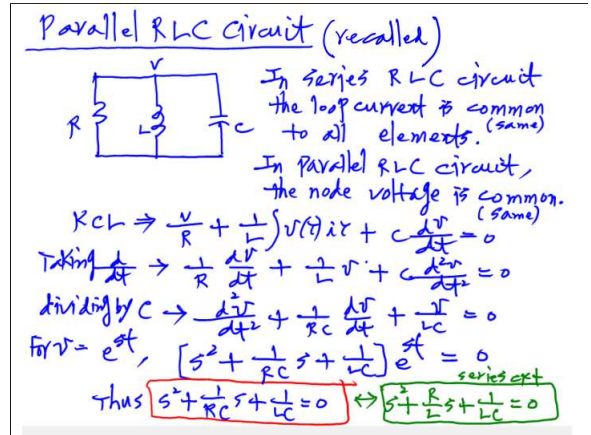Two circuits are said to be **duals** of one another if they are described by the same characterizing equations with dual quantities interchanged.



Give the characteristic eq. of the Parallel RLC circuit as $s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$

($s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$ for the series RLC)

$$(s + \frac{1}{2RC})^2 - ((\frac{1}{2RC})^2 - \frac{1}{LC}) = 0$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{(\frac{1}{2RC})^2 - \frac{1}{LC}}$$

Let $\frac{1}{2RC} = \alpha$

Case 1) $\alpha > \omega_0$, s_1, s_2 are neg. real

$$\Rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case 2) $\alpha = \omega_0$, $s_1 = s_2 =$ (double)

$$v(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$

Case 3) $\alpha < \omega_0$

$$s_{1,2} = -\alpha \pm j \sqrt{\omega_0^2 - \alpha^2} = -\alpha \pm j\omega_d$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

$$v(t) = e^{-\alpha t} M \cos(\omega_d t - \theta)$$

$$v(0) = M \cos(-\theta) = M \cos \theta \quad (A)$$

$$v'(0) = -\alpha e^{-\alpha t} M \cos(\omega_d t - \theta) + e^{-\alpha t} M (-\omega_d \sin(\omega_d t - \theta)) \Big|_{t=0}$$

$$= -\alpha M \cos \theta + \omega_d M \sin \theta \quad (B)$$

$$\frac{v'(0)}{v(0)} = -\alpha + \omega_d \tan \theta \Rightarrow \theta, \text{ next use (A) to find } M$$

Example

$\omega_0^2 = \frac{1}{LC} = \frac{1}{1 \times 10 \times 10^{-3}} = 100, \omega_0 = 10$
 $\alpha = \frac{1}{2RC} = \frac{1}{2(6.25)10 \times 10^{-3}} = \frac{1000}{125} = 8$
 $\alpha < \omega_0$ (Case 3)!

$i(0) = 0$
 $v(0) = 5$

$v(t) = e^{-\alpha t} M \cos(\omega_d t - \theta)$
 where $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{100 - 8^2} = 6$
 $v(t) = e^{-8t} M \cos(6t - \theta)$

next identify M, θ from initial conditions

$v(0) = M \cos \theta = 5$
 $C \frac{dv(t)}{dt} \Big|_{t=0} = -\left(\frac{v(t)}{C} + i(t)\right) \Big|_{t=0}$
 $v'(0) = -\frac{1}{C} \left(\frac{v(0)}{6.25} + 0\right) = -\frac{1}{10 \times 10^{-3}} \left(\frac{5}{6.25}\right) = -80$
 $v'(t) = -\alpha e^{-\alpha t} M \cos(\omega_d t - \theta) + e^{-\alpha t} M \sin(\omega_d t - \theta)$

$\Rightarrow v'(0) = -\alpha M \cos \theta + \alpha M \sin \theta$
 $\frac{v'(0)}{5} = -\alpha + \alpha \tan \theta$
 $\frac{-80}{5} = -8 + 8 \tan \theta$
 $-8 = 8 + 8 \tan \theta \Rightarrow \tan \theta = -1 \Rightarrow \theta = -45^\circ$

thus, $M \cos \theta = 5, M = \frac{5}{\cos(-45^\circ)} = \frac{5}{\frac{\sqrt{2}}{2}} = \frac{5\sqrt{2}}{1}$

$v(t) = \frac{5}{\sqrt{2}} e^{-8t} \cos(6t + 45^\circ)$

Step (input) Response of RLC Circuits.

$E = L \frac{di}{dt} + R i + C \frac{dv}{dt} + v$
 $= LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v$

$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{E}{LC}$

In DC steady state $v_{ss} = E$ & $v(t) = v_t + v_{ss}$

Series RLC

$v(t) = v_t + v_{ss} = E$
 v_t natural response due to initial condition
 i) $\omega_0 > \alpha$
 ii) $\omega_0 = \alpha$
 iii) $\omega_0 < \alpha$

Parallel RLC

$i(t) = i_t(t) + i_{ss} = I_s$
 $i_t(t)$ natural response due to initial condition
 i) $\omega_0 > \alpha$
 ii) $\omega_0 = \alpha$
 iii) $\omega_0 < \alpha$

Pendulum

$v_s(t) = LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v$
 $v = v_t + v_{ss}$
 when $v_s(t) = 0, R = 0$

$LC \frac{d^2v}{dt^2} + v = 0$

$Ml \frac{d^2\theta}{dt^2} + Mgsin\theta = 0$
 For small $\theta, \sin \theta \approx \theta$
 $\frac{d^2\theta}{dt^2} + \left(\frac{g}{L}\right)\theta = 0$

Example

$i(0^-) = 4A = i(0^+)$
 $v(0) = 30 \frac{20}{20+20} = 15V = v(0^+)$

For $t > 0$ $i(0) = 4A$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 8 \times 10^{-6}}} = \frac{1}{\frac{4}{10}} = 2.5$
 $\alpha = \frac{R}{2L} = \frac{10}{40} = 0.25$
 $\omega_0 > \alpha$
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 2.4895$

$i_t(t) = M e^{-\alpha t} \cos(\omega_d t - \theta)$

$$\tilde{x}_4(t) = e^{-\alpha t} m \cos(\omega_d t - \theta) \quad \omega_d = 2.4875$$

$$= 4.16 e^{-0.5t} \cos(\omega_d t - 15.5^\circ)$$

$$\tilde{x}_4(0) = m \cos(-\theta) = m \cos \theta = 4 \quad \left[\begin{array}{l} M = \frac{4}{0.962} \\ = 4.16 \end{array} \right]$$

$$\tilde{x}_4'(t) = \left. \frac{d}{dt} e^{-\alpha t} m \cos(\omega_d t - \theta) + e^{-\alpha t} m (-\omega_d \sin(\omega_d t - \theta)) \right|_{t=0}$$

$$= -\alpha \frac{m \cos \theta}{\uparrow = 4} + \omega_d m \sin \theta = \dot{x}_4(0)$$

$$\downarrow \dot{x}_4(0) = v(0) = 15 \quad \dot{x}_4(0) = \frac{15}{20} = 0.75$$

$$\frac{\dot{x}_4(0)}{\uparrow} = -\alpha + \omega_d \tan \theta = -0.5 + 2.4875 \tan \theta$$

$$\tan \theta = \left(\frac{0.75}{4} + 0.5 \right) / 2.4875 = 0.276$$

$$\theta = 0.27 \text{ rad} \quad \cos \theta = 0.962$$