

EE101 Lecture # 24 May 9, 2018


- Quiz 9 on Monday, March 12 on RLC Circuits.
- Course review on F, March 16
- Final Exam on T, March 20 4-7 p.m.

Final Exam (12 problems)

You are allowed to use 2 pages of formulas and tables only, not concepts, prob. soln

Coverage: chapters 1-8, 13 (transformer, coupled inductors)
14 (14.2 ~ 14.4 Bode plots)

Step (input) Response of RLC Circuits.

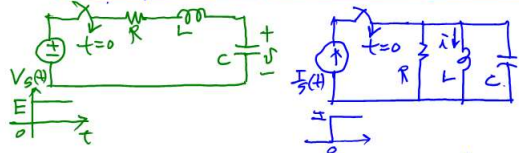

For $t > 0$

$$E = L \frac{d}{dt} \left(C \frac{dV}{dt} \right) + R \left(C \frac{dV}{dt} \right) + V$$

$$= LC \frac{d^2 V}{dt^2} + RC \frac{dV}{dt} + V$$

$$\frac{d^2 V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = \frac{E}{LC}$$

In DC steady state $V_{ss} = E$ & $V(t) = V_t + V_{ss}$

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + i = \frac{I_s}{LC}$$

Series RLC

$$v(t) = v_t + v_{ss} = E$$

v_t natural response due to initial condition


- $\omega_0 > \alpha$
- $\omega_0 = \alpha$
- $\omega_0 < \alpha$

Parallel RLC

$$i(t) = i_t + i_{ss} = I$$

i_t natural response due to initial condition

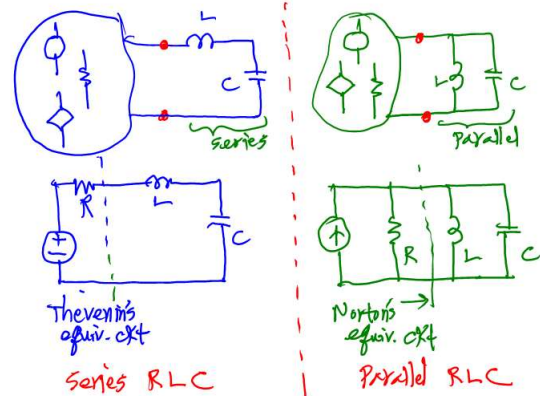- $\omega_0 > \alpha$
- $\omega_0 = \alpha$
- $\omega_0 < \alpha$



Example

$i(0^-) = 4A = i(0^+)$
 $v(0^-) = 30 \frac{20}{20+20} = 15V = v(0^+)$
 For $t > 0$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 20 \times 10^{-6}}} = \frac{1}{4} = 2.5$
 $\alpha = \frac{R}{2L} = \frac{10}{40} = 0.25$
 $\omega_0 > \alpha$
 $\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 2.4875$

$$i_t(t) = M e^{-\alpha t} \cos(\omega_d t - \theta)$$

$$i_t(t) = e^{-\alpha t} m \cos(\omega_d t - \theta) \quad \omega_d = 2.4875$$

$$= 4.16 e^{-0.25t} \cos(\omega_d t - 15.5^\circ)$$

$$i_t(0) = m \cos(-\theta) = m \cos \theta = 4 \quad \left[M = \frac{4}{0.962} = 4.16 \right]$$

$$i_t'(t) = -\alpha e^{-\alpha t} m \cos(\omega_d t - \theta) + e^{-\alpha t} m (-\omega_d \sin(\omega_d t - \theta)) \Big|_{t=0}$$

$$= -\alpha M \cos \theta + \omega_d M \sin \theta = i_t'(0)$$

$$-i_t'(0) = v(0) = 15 \quad i_t'(0) = \frac{15}{20} = 0.75$$

$$\frac{i_t'(0)}{4} = -\alpha + \omega_d \tan \theta = -0.25 + 2.4875 \tan \theta$$

$$\tan \theta = \frac{(0.75/4) + 0.25}{2.4875} = 0.276$$

$\theta = 0.27 \text{ rad} \quad \cos \theta = 0.962$

Example

For $t < 2$

Thevenin's equivalent

$$\alpha = \frac{R}{2L} = \frac{30}{2 \times 3} = 5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \left(\frac{1}{27}\right)}} = 3$$

$\alpha > \beta$, thus overdamped +

$$s_1, s_2 = -5 \pm \sqrt{5^2 - 3^2}$$

$$v(t) = 6 + A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t} = 6 + A_1 e^{-t} + A_2 e^{-9t}$$

$$v(0) = 6 + A_1 + A_2 = 0, \quad v'(0) = -A_1 - 9A_2 = 0$$

$$v(t) = 6 + A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$$

$$\frac{dv(t)}{dt} = 0 + A_1(-\alpha_1) e^{-\alpha_1 t} + A_2(-\alpha_2) e^{-\alpha_2 t} \Big|_{t=0}$$

$$= 0 - A_1(1)(1) + A_2(-9)(1)$$

$$= -A_1 - 9A_2 = v'(0)$$

capacitor current

$$v'(0) = i(0) = 0$$

$$A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$$

$$s^2 + 2\alpha s + \omega_0^2 - \alpha^2 = 0 \quad (s + \alpha) - (\alpha^2 - \omega_0^2) = 0$$

$$(s + \alpha + \sqrt{\alpha^2 - \omega_0^2}) \times (s + \alpha - \sqrt{\alpha^2 - \omega_0^2}) = 0$$

$$-s_1 = \alpha_1 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} < 0$$

$$-s_2 = \alpha_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} < 0$$

From $-A_1 - 9A_2 = 0 \quad A_1 = -9A_2$

From $0 = 6 + A_1 + A_2 = 6 - 9A_2 + A_2$

$$A_2 = \frac{3}{4}$$

$$A_1 = -9 \left(\frac{3}{4}\right) = -\frac{27}{4}$$

$$v(t) = 6 - \frac{27}{4} e^{-t} + \frac{3}{4} e^{-9t}, \quad v(0) = 6$$

$$v(2) = 6 - \frac{27}{4} e^{-2} + \frac{3}{4} e^{-18} = 5.086, \quad \frac{dv}{dt} = \frac{27}{4} e^{-t} - \frac{27}{4} e^{-9t}$$

$t > 2$, same circuit but no indep. voltage source

$$v(t) \Big|_{t=2} = 5.086$$

$$\frac{dv}{dt} \Big|_{t=2} = \frac{27}{4} e^{-2} - \frac{27}{4} e^{-18} \approx \frac{27}{4} e^{-2}$$

$$v(t) = (A_1 e^{-(t-2)} + A_2 e^{-9(t-2)}) u(t-2)$$

$$v(t-2) \Big|_{t=2} = -A_1 - 9A_2 = \frac{27}{4} e^{-2}$$

5.086 = $A_1 + A_2$
solve for A_1, A_2

$$v(t) = \left[5.086 e^{-(t-2)} - 0.249 e^{-9(t-2)} \right] u(t-2)$$

$$v(t) = \left[-6.75 e^{-t} + 0.75 e^{-9t} \right] u(t)$$

In the circuit given below, $R = 30 \Omega$, $V = 30V$, and $L = 1/6 H$.

Calculate $i_L(0^+)$, $v_C(0^+)$, and $v_R(0^+)$.

At $t = 0^-$,
 \downarrow shorted
 \uparrow opened

The value of $i_L(0^+)$ is A.

The value of $v_C(0^+)$ is V.

The value of $v_R(0^+)$ is V.

In the circuit given below, $R_1 = 4 \Omega$ and $R_2 = 7 \Omega$.

Find $dv(0^+)/dt$ and $di(0^+)/dt$.

The value of $dv(0^+)/dt$ is V/s.

The value of $di(0^+)/dt$ is A/s.

At $t=0 \rightarrow i(0) = \frac{4}{11}$

$v(t=0) = 4 \left(\frac{2}{4+2} \right) = \frac{8}{3} \text{ V}$
 $C \frac{dv(t)}{dt} \Big|_{t=0} = \frac{4}{11} + 4 - \frac{2i}{11} / 7$
 $= \frac{4+16-4}{11} = \frac{16}{11}$
 $\bullet \frac{dv(t)}{dt} = \frac{16}{11} / \frac{1}{7} = \frac{64}{11}$
 $4i(0) + L \frac{di(0)}{dt} = v(0) \bullet \frac{di(0)}{dt} = \frac{v(0) - 4i(0)}{0.25} = \frac{\frac{8}{3} - 4(\frac{4}{11})}{0.25} = \frac{12 \times 7}{11}$

The current in an RLC circuit is described by

$$\frac{d^2 i}{dt^2} + 10 \frac{di}{dt} + 25 i = 0 \Rightarrow s^2 + 10s + 25 = (s+5)^2 = 0$$

$s_{1,2} = -5$

If $i(0) = 10 \text{ A}$ and $d(i(t))/dt = 0$, then for $t > 0$, $i(t) = (A + Bt)e^{st} \text{ A}$,
 where $A = \underline{\hspace{2cm}}$, $B = \underline{\hspace{2cm}}$, and $s = \underline{\hspace{2cm}}$.

$i(0) = 10 = (A + Bt) e^{st} \Big|_{t=0} = A$
 $i'(0) = A s e^{st} + B e^{st} + B + s A e^{st} \Big|_{t=0} = 0$
 $10s + B = 0 \quad 10(-5) + B = 0 \Rightarrow B = 50$

In the circuit given below, $R = 20 \Omega$ and the switch moves (a make-before-break switch) from position A to B at $t = 0$. Find $v(t)$ for all $t \geq 0$.

The voltage equation is $v(t) = A e^{s_1 t} + B e^{s_2 t}$,
 where $A = \underline{\hspace{2cm}}$, $B = \underline{\hspace{2cm}}$, $s_1 = \underline{\hspace{2cm}}$ and $s_2 = \underline{\hspace{2cm}}$.

$i(0) = 0 \quad v(0) = 5A(4\Omega) = 20 \text{ V}$
 $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 \times 0.04}} = 10$
 $\alpha = \frac{R}{2L} = \frac{20}{2 \times 0.25} = 40$
 $\omega_0 = 10 < \alpha = 40$ (overdamped)

$\alpha > \omega_0$ overdamped.

$$v(t) = A e^{-\alpha_1 t} + B e^{-\alpha_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -40 \pm \sqrt{40^2 - 10^2} = -40 \pm \sqrt{1500}$$

$$s_1 = -40 + 10\sqrt{15}, \quad s_2 = -40 - 10\sqrt{15}$$

$v(0) = A + B = 20 \quad [A = 20 - B]$
 $v'(0) = -\alpha_1 A - \alpha_2 B = 0$
 $s_{1,2} A + s_{2,1} B = 0 \Rightarrow (-40 + 10\sqrt{15})A + (-40 - 10\sqrt{15})B = 0$
 $20\sqrt{15} B = (-4) + 10\sqrt{15} \Rightarrow B = \frac{-4 + 10\sqrt{15}}{\sqrt{15}}$

Assuming $R = 12 \text{ k}\Omega$, design a parallel RLC circuit that has the characteristic equation $s^2 + 100s + 10^6 = 0$.

The value of L is $\underline{\hspace{2cm}}$ H.
 The value of C is $\underline{\hspace{2cm}}$ nF.

$s^2 + 100s + 10^6 = (s+50)^2 + 10^6 - (50)^2$
 $\omega_0^2 = \frac{1}{LC} = 10^6 \quad \bullet \quad C = \frac{1}{L \omega_0^2} = \frac{1}{1.2 \times 10^3 \times 10^6} = \frac{1}{1.2 \times 10^9}$
 $\frac{R}{2L} = 50 = \frac{12 \times 10^3}{2L} \Rightarrow L = \frac{12 \times 10^3}{100} = 1.2 \times 10^2 \text{ H}$

In the circuit given below, $i = 15[1 - u(t)] \text{ A}$. Calculate $i(t)$ for $t > 0$.

$i(0) = 15 \text{ A}$
 $i'(0) = 0$
 $i_{5\Omega}(0) = 15 \times \frac{10}{10+15} = 6 \text{ A}$
 $v_{5\Omega}(0) = 5 \times 6 = 30 \text{ V}$

The current equation is $i(t) = [A e^{s_1 t} + B e^{s_2 t}] \text{ A}$,
 where $A = \underline{\hspace{2cm}}$, $B = \underline{\hspace{2cm}}$, $s_1 = \underline{\hspace{2cm}}$ and $s_2 = \underline{\hspace{2cm}}$.

$A + B = i(0) = 15$
 $s_1 A + s_2 B = i'(0) = -40$
 $t > 0 \rightarrow \frac{1}{3} \frac{dv}{dt} = 15 \times \frac{10}{10+15} - \frac{v}{3} \Rightarrow \frac{dv}{dt} + \frac{v}{3} = 30$
 $\frac{dv}{dt} + 4 \frac{v}{3} = 30 \Rightarrow v(t) = (30 - 60e^{-4t/3}) \times \frac{1}{3} = -40e^{-4t/3} + 10$