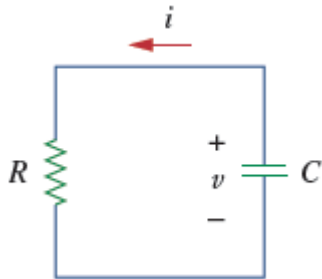


In the given circuit,  
 $v(t) = 58 e^{-240t} \text{ V}, t > 0$

$i(t) = 9 e^{-240t} \text{ mA}, t > 0$



### References

Section Break

Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.

1.

Award: 10.00 points

Calculate the time constant  $\tau$ .

The time constant  $\tau$  is  ms.

**Hints**

[Hint #1](#)

### References


Worksheet

Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.
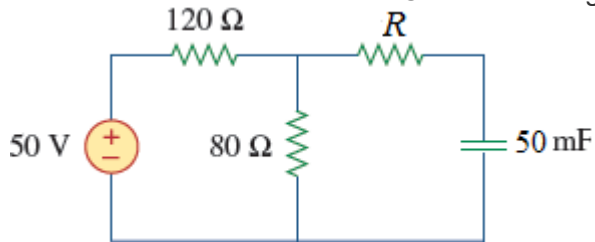
## 2. Award: 10.00 points

Find the time constant for the RC circuit in the given figure. Assume  $R = 12 \Omega$ .



The time constant for the RC circuit in the given figure is  s.

### Hints

[Hint #1](#)

### References


**Worksheet**

Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.
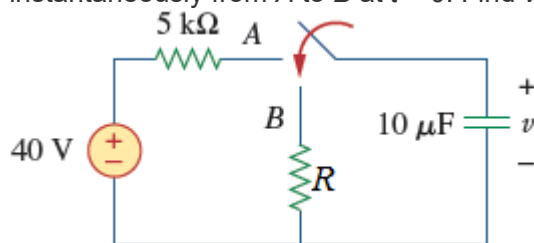
## 3. Award: 10.00 points

The switch in the given figure has been in position A for a long time. Assume the switch moves instantaneously from A to B at  $t = 0$ . Find  $v$  for  $t > 0$ . Assume  $R = 3 \text{ k}\Omega$ .



The voltage  $v(t) = v(0) e^{-t/\tau}$ , where  $v(0) =$   V and  $\tau =$   s.

**Hints**[Hint #1](#)**References****Worksheet**


Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

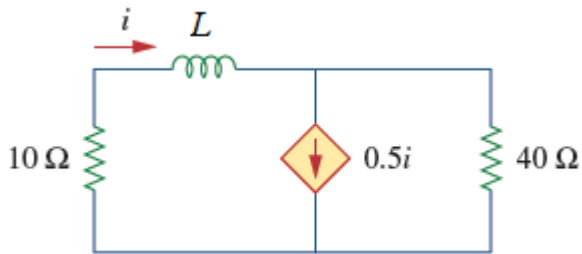**4.**

Award: 10.00 points

In the given circuit, find the unknown quantities of  $i(t)$  for  $t > 0$  if  $i(0) = 8$  A. Assume  $L = 7$  H.



The current  $i(t) = 8e^{-t/\tau}$  A, where  $\tau =$   s.

**Hints**[Hint #1](#)**References****Worksheet**


Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

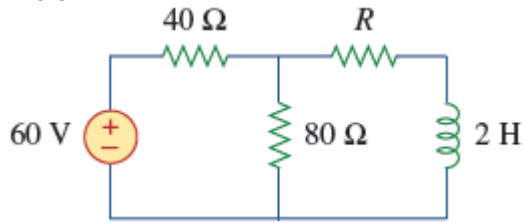**5.**

Award: 10.00 points

In the given circuit, find the value of  $R$  for which the steady-state energy stored in the inductor will be 1.6 J.



The value of  $R$  is   $\Omega$ .

### Hints

[Hint #1](#)

[Hint #2](#)

[Hint #3](#)

### References

**Worksheet**


Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

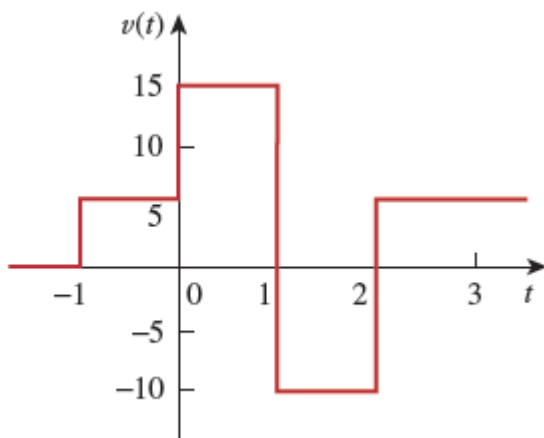6.

Award: 10.00 points

Express  $v(t)$  in the given figure in terms of step functions.



$v(t) = (5u(t-1) + 10u(t) - 25u(t+2) + 15u(t+2)) \text{ V}$

- $v(t) = (5u(t+1) + 10(t-1) - 25u(t) + 15u(t-2))$  V
- $v(t) = (5u(t-2) + 10u(t-1) - 25u(t) + 15u(t+1))$  V
- $v(t) = (5u(t+1) + 10u(t) - 25u(t-1) + 15u(t-2))$  V

## Hints

[Hint #1](#)

## References

Multiple Choice

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

7.

Award: 10.00 points

The voltage across a 10-mH inductor is  $40\delta(t-2)$  mV. Find the inductor current, assuming that the inductor is initially uncharged.

The inductor current is  $i(t) = \boxed{\phantom{000}} u(t-2)$  A.

## Hints

[Hint #1](#)

## References

Worksheet

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

8.

Award: 10.00 points

Find the solution of the differential equation  $\frac{dv}{dt} + 4v = 0$ ,  $v(0) = -1$  V.

The solution of the given differential equation is  $-(e^{-\text{[ ]}t}) V$ .

### Hints

[Hint #1](#)

### References

**Worksheet**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

9.

Award: 10.00 points

Identify the solution of the following differential equation, subject to the stated initial condition.

$$2\frac{dv}{dt} - v = 3u(t), \quad v(0) = -6$$

- $v(t) = 3(1 - e^{t/2})u(t) V, \quad t > 0$
- $v(t) = -3(1 + e^{t/2})u(t) V, \quad t > 0$
- $v(t) = 3(1 - e^{t/2}) V, \quad t < 0$
- $v(t) = -3(1 + e^{t/2}) V, \quad t < 0$

### Hints

[Hint #1](#)

[Hint #2](#)

### References

**Multiple Choice**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

A circuit is described by

$$1 \frac{dv}{dt} + v = 10.$$

### References

**Section Break**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

# 10.

Award: 10.00 points

If  $v(0) = 4$ , find  $v(t)$  for  $t \geq 0$ .

The voltage  $v(t) =$    $+ ($    $) (e^{-$    $t}) \times u(t) \text{ V.}$

### Hints

[Hint #1](#)

[Hint #2](#)

### References

**Worksheet**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.