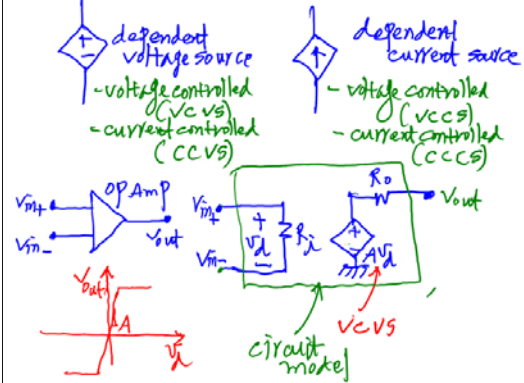


EE101 Lecture #4 Jan 17, 2018
 Quiz #1 today 3:30-3:45 p.m.


Text adopted (official) register by Friday

<connect>
<http://connect.mheducation.com/class/5-Kang-winter2018-mw/5240>


Dependent Sources



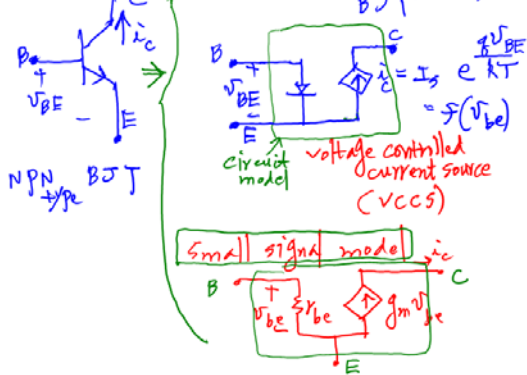Another example (Bipolar Junction Transistor)



Series connection

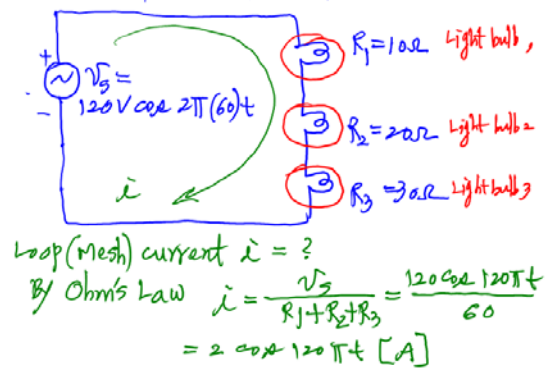


Average power in Light Bulb 1

$$\begin{aligned}
 P_1 &= \frac{1}{T} \int_0^T v_1(t) i(t) dt \\
 &= \frac{1}{T} \int_0^T R_1 i^2(t) dt \\
 v_1 &= R_1 i = \frac{10}{T} \int_0^T [2 \cos 120\pi t]^2 dt \\
 &= \frac{10}{T} \int_0^T \cos^2 120\pi t dt \\
 \cos^2 \theta &= \frac{1}{2}(1 + \cos 2\theta) \\
 &= \frac{10}{T} \left[\frac{1}{2} T + \frac{1}{2} \int_0^T \cos 240\pi t dt \right] \\
 &= 20 \text{ W}
 \end{aligned}$$

For Light Bulb 2 ($R_2 = 20\Omega$)

$$\begin{aligned}
 P_2 &= \frac{20}{10} [20\text{W}] = 40\text{W} \\
 P_3 &= \frac{30}{10} [20\text{W}] = 60\text{W} \\
 \text{Total wattage } P_1 + P_2 + P_3 &= \boxed{120\text{W}}
 \end{aligned}$$

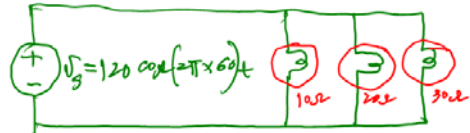\Rightarrow bulbs are connected in parallel



avg power in bulb 1

$$P_1 = \frac{1}{T} \int_0^T v_s(t) i_1(t) dt = \frac{1}{T} \int_0^T \frac{v_s^2(t)}{R_1} dt$$

$$= \frac{1}{10 \text{ T}} \int_0^T [120 \cos 120\pi t]^2 dt$$

$$= \frac{14400}{10 \text{ T}} \int_0^T \left[\frac{1}{2} + \cos 240\pi t \right] dt$$


$$= \frac{144}{T} \left[\frac{1}{2} T + \underbrace{\int_0^T \cos 240\pi t dt}_{=0} \right]$$

$$= 72 \text{ W}$$

$$P_2 = 72 \text{ W} \left(\frac{10}{20} \right) = 36 \text{ W} \quad (P(t) = \frac{v_s^2(t)}{R})$$

$$P_3 = 72 \text{ W} \left(\frac{10}{30} \right) = 24 \text{ W}$$

$$P_1 + P_2 + P_3 = 72 + 36 + 24 = \boxed{132 \text{ W}}$$

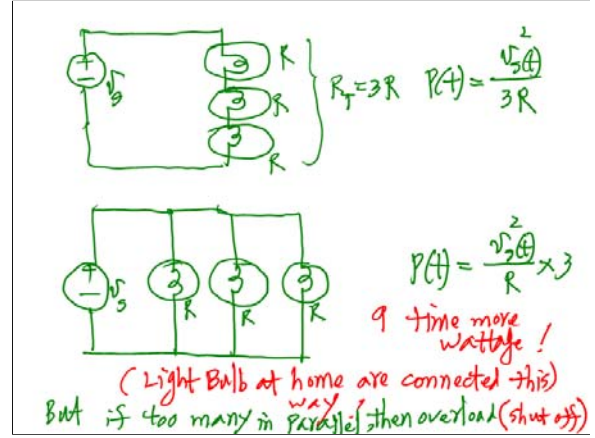

chapter 2
Resistance


$$R[\Omega] = \rho \frac{l}{A}$$

resistivity [$\Omega \cdot m$]

length [m]

cross-sectional area [m^2]

Material	$\rho [\Omega \cdot m]$	Type
Copper	1.72×10^{-8}	conductor
silicon	6.4×10^2	semiconductor
Glass	10^{12}	insulator

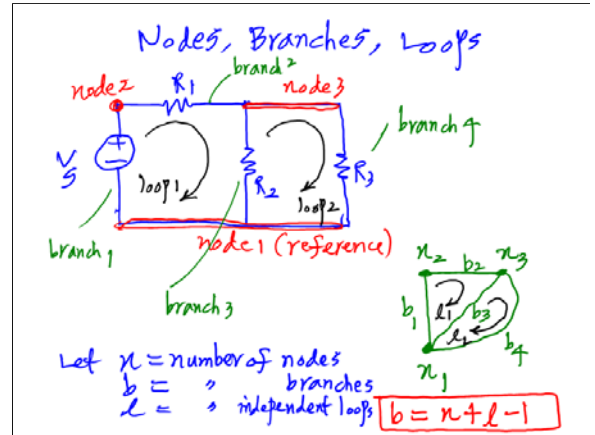


$b = n + l - 1$

Example 1

$n = 3$
 $b = 4$
 $l = 2$
 $4 = 3 + 2 - 1$ (✓)

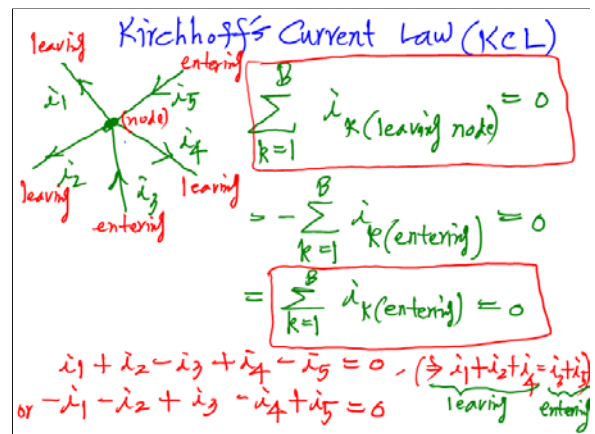Example 2


$n = 4$
 $b = 6$
 $l = 3$
 $6 = 4 + 3 - 1$ (✓)




Another way of stating KCL is

$$\sum i_k(\text{leaving}) = \sum i_k(\text{entering})$$

Example

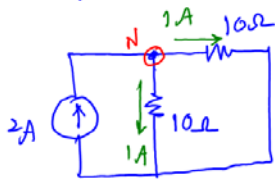


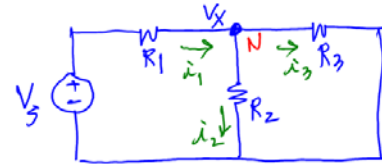At N, by KCL
 $-2 + 1 + 1 = 0$
 or $+2 - 1 - 1 = 0$
 or $2 = 1 + 1$ (✓)




Applying KCL at node N,
 current entering node N, $i_1 = \frac{V_s - V_x}{R_1}$
 currents leaving node N,
 $i_2 = \frac{V_x}{R_2}$, $i_3 = \frac{V_x}{R_3}$
 $\rightarrow \frac{V_s - V_x}{R_1} = \frac{V_x}{R_2} + \frac{V_x}{R_3}$ $V_x = \text{unknown}$
 solve for V_x , then i_1, i_2, i_3 ☐

Example Practice Prob. 2.7

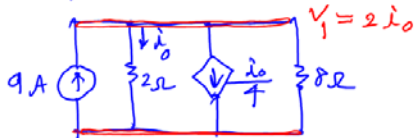

KCL $9 = i_0 + \frac{V_1}{2} + \frac{V_1}{8} = 2i_0$
 $= i_0(1 + \frac{1}{4} + \frac{1}{8})$
 $i_0 = \frac{9}{1.5} = 6 \text{ [A]}$
 $V_1 = 2i_0 = 2 \text{ [}\Omega\text{]} 6 \text{ [A]} = 12 \text{ [V]}$

(Prob 2.32)

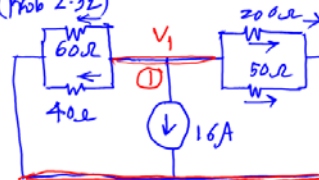

KCL at node ①
 KCL $\sum i_k(\text{leaving}) = 0$
 $16 + \left(\frac{V_1}{200} + \frac{V_1}{50}\right) + \left(\frac{V_1}{60} + \frac{V_1}{40}\right) = 0$
 $16 + V_1 \left(\frac{1}{200} + \frac{1}{50} + \frac{1}{60} + \frac{1}{40}\right) = 0$
 $V_1 = -16 / \left(\frac{1}{200} + \frac{1}{50} + \frac{1}{60} + \frac{1}{40}\right) = -240 \text{ [V]}$

$$\left. \begin{aligned} i_{200\Omega} &= -\frac{240}{200} = -1.2 \text{ A} \\ i_{50\Omega} &= -\frac{240}{50} = -4.8 \text{ A} \\ i_{60\Omega} &= -\frac{240}{60} = -4 \text{ A} \\ i_{40\Omega} &= -\frac{240}{40} = -6 \text{ A} \end{aligned} \right\} \sum i_k = -16 \text{ A}$$



Kirchhoff's Voltage Law (KVL)

$$\sum_k^{B(\text{in loop})} v_k(\text{voltage drop}) = 0$$

$$= \sum_k (-v_k(\text{voltage drop})) = 0$$

$$= \sum_k^{B(\text{in loop})} v_k(\text{voltage rise}) = 0$$

