

EE 101 Winter 2018

Midterm Exam (February 12)


Name : *Solution*

Student Id:

*Presented here are one of many
different ways to solve these problems.*

Problem	Maximum points	score
1	20	
2	20	
3	20	
4	20	
5	20	

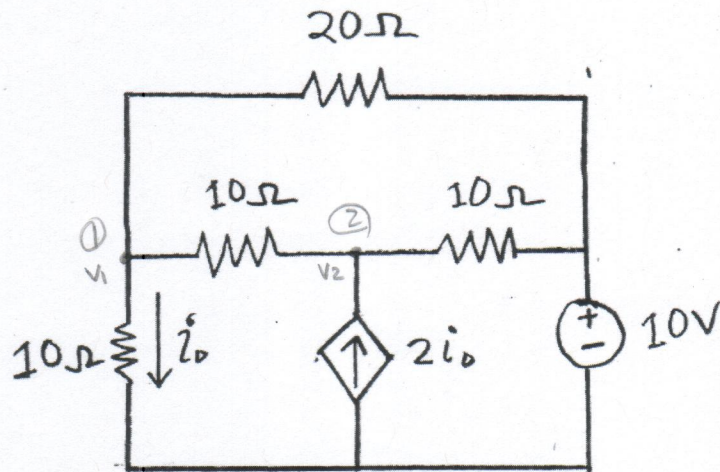1. (12+4+4 points) Using nodal analysis, (a) calculate the value of i_o in the following circuit. Calculate the power generated/consumed by (b) the current dependent current source ($2i_o$) and (c) 20Ω resistance.



$$\text{KCL at } \textcircled{1} : \frac{v_1 - 10}{20} + \frac{v_1}{10} + \frac{v_1 - v_2}{10} = 0$$

$$\textcircled{2} : \frac{v_1 - v_2}{10} + 2i_o + \frac{10 - v_2}{10} = 0, \quad i_o = \frac{v_1}{10}$$

$$v_1 - 10 + 2v_1 + 2v_1 - 2v_2 = 0$$

$$5v_1 - 2v_2 = 10$$

$$v_1 - v_2 + 2v_1 + 10 - v_2 = 0$$

$$3v_1 - 2v_2 = -10$$

$$2v_1 = 20, \quad v_1 = 10$$


$$a) i_o = \frac{v_1}{10} = \frac{10}{10} = \underline{\underline{1 \text{ A}}}$$

$$v_2 = 20$$


$$b) P_{2i_o} = v_2 \cdot 2i_o = 20 \times -(2 \times 1) = \underline{\underline{-40 \text{ W}}} \text{ (provide power)}$$

$$c) P_{20\Omega} = (v_1 - 10) \cdot i_{20\Omega} = \underline{\underline{0 \text{ W}}} \text{ (no power consumed)}$$

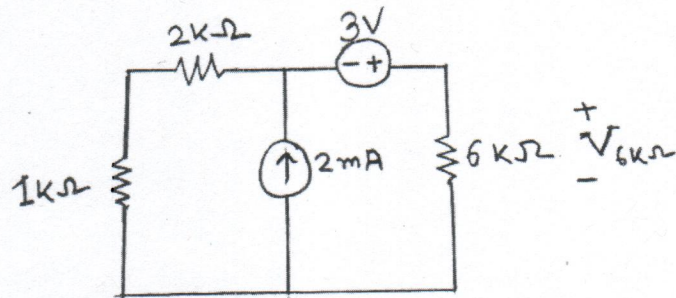2. (15+5 points) Using superposition theorem, calculate the voltage and the power of $6k\Omega$ resistor in the following circuit.




With $2mA$ Source only.

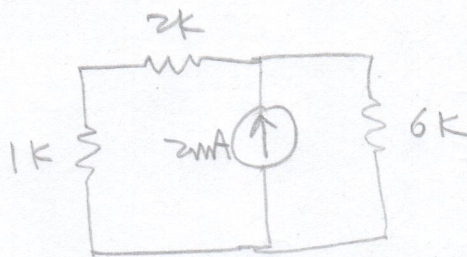

$$i_{6k} = 2m \cdot \frac{(2k+1k)}{6k+(2k+1k)} = \frac{2}{3} mA$$


$$V_{6k} = \frac{2}{3} m \cdot 6k = \frac{12}{3} = 4V$$

With $3V$ Source only.

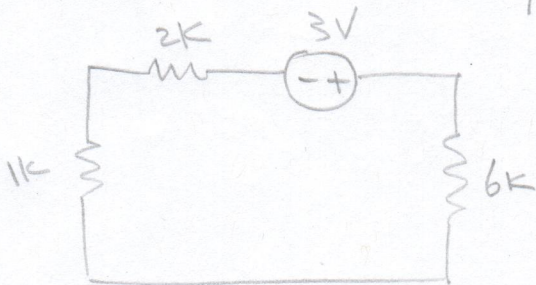

$$i_{6k} = \frac{3}{(6+1+2)k} = \frac{1}{3} mA$$
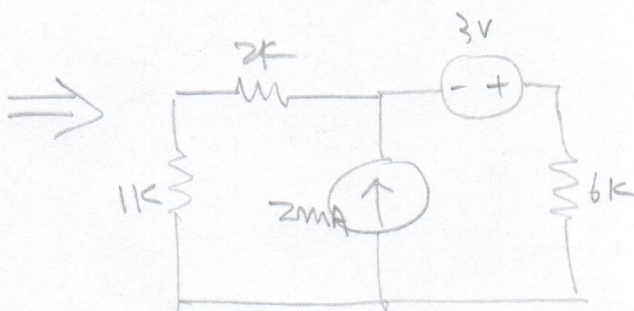
$$V_{6k} = 3 \cdot \frac{6k}{(6+2+1)k} = 2V$$




$$i_{6k} = \frac{2}{3} m + \frac{1}{3} m = 1 mA$$

$$V_{6k} = 4 + 2 = \underline{\underline{6V}}$$



$$P_{6k} = V_{6k} \cdot i_{6k} = 6 \cdot 1m = \underline{\underline{6mW}}$$

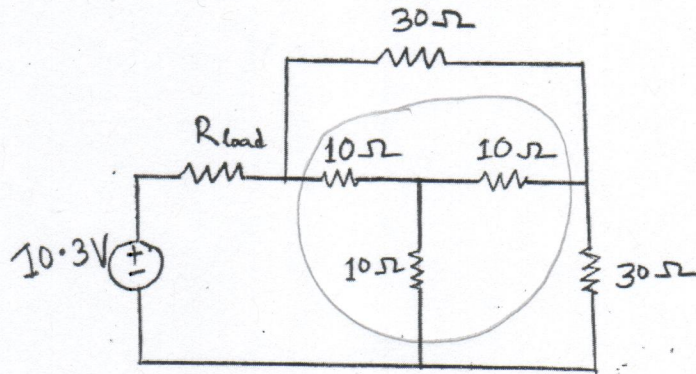3. (20 points) For the following circuit determine the value of R_{load} that would result in maximum power being transferred to R_{load} . (Hint: Δ -Y conversion would help you simplify the network.)





using Δ -Y conversion with Y network in the circuit drawn

($R_{\Delta} = 3 R_Y$)

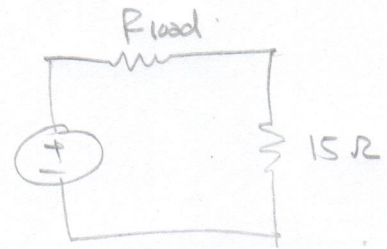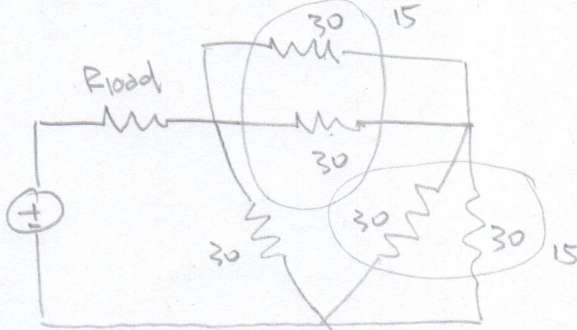


For maximum power transfer

$R_{load} = 15 \Omega$

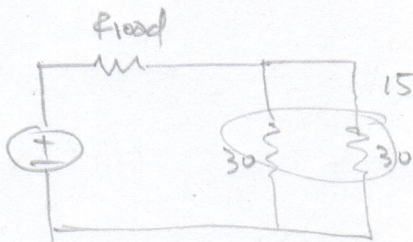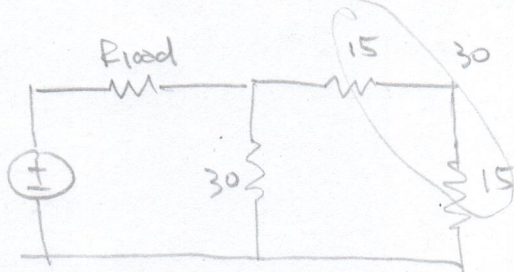

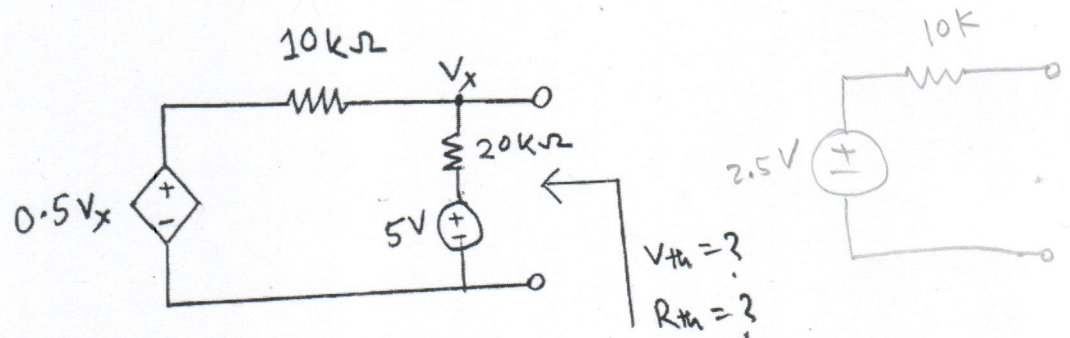4. (10+10 points) Determine the Thevenin equivalent for the following circuit:




$$V_{th} = V_{oc} = V_x$$

KCL at X,
$$\frac{5 - V_x}{20K} + \frac{0.5V_x - V_x}{10K} = 0$$

$$5 - V_x + V_x - 2V_x = 0$$

$$\underline{\underline{V_x = \frac{5}{2} V}}$$

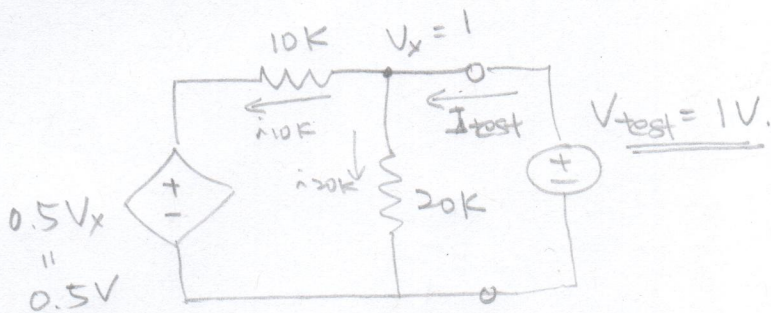
To find R_{th} , turn off the independent source and apply test source to the port. then $R_{th} = \frac{V_{test}}{I_{test}}$.



$$\begin{aligned} I_{test} &= i_{20K} + i_{10K} \\ &= \frac{V_x}{20K} + \frac{V_x - 0.5V_x}{10K} \\ &= \frac{1}{20K} + \frac{1}{20K} \quad (V_x = V_{test} = 1V) \\ &= \frac{1}{10K} \end{aligned}$$

$$\underline{\underline{R_{th} = \frac{1}{\left(\frac{1}{10K}\right)} = 10K \Omega}}$$

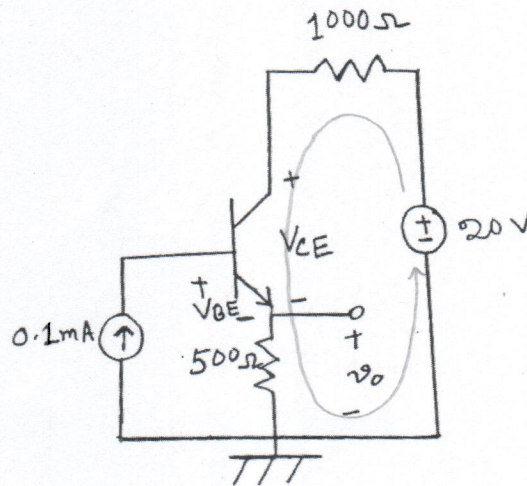5. (10+10 points) Consider the following transistor circuit with $V_{BE}=0.7V$ and $\beta=99$. Determine the V_0 and V_{CE} .



$$I_B = 0.1 \text{ mA}$$

$$I_C = \beta I_B = 99 \times 0.1 = 9.9 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 100 \times 0.1 = 10 \text{ mA}$$

$$V_0 = I_E \cdot 500 = 10 \text{ mA} \cdot 500 = \underline{5 \text{ V}}$$

KVL along the loop in the figure

$$-20 + I_E \cdot 1000 + V_{CE} + V_0 = 0$$

$$V_{CE} = 20 - 9.9 \text{ mA} \times 1000 - 5$$

$$= 20 - 9.9 - 5$$

$$= \underline{5.1 \text{ V}}$$