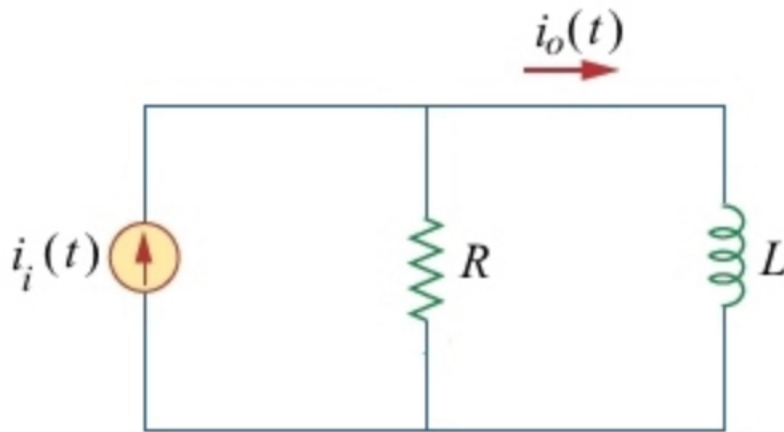


1.

value:
10.00 points

Identify the transfer function I_o/I_i of the RL circuit shown below. Express the transfer function using $\omega_o = R/L$.



→ $H(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_o}}$

$H(\omega) = \frac{1}{j + \frac{\omega_o}{\omega}}$

$H(\omega) = \frac{1}{1 + j\frac{\omega_o}{\omega}}$

$H(\omega) = \frac{j\omega}{1 + \frac{\omega}{\omega_o}}$

$$H(\omega) = \frac{I_o}{I_i} = \frac{\left(\frac{Rj\omega L}{R + j\omega L}\right)}{j\omega L} = \frac{1}{\left(1 + \frac{j\omega L}{R}\right)} \quad \text{--(1)}$$


Given $\omega_o = R/L$.

Eq.(1) becomes

$$H(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_o}}$$

$$H = |H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_o}\right)^2}} \text{ and } \theta = \angle H(\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_o}\right)$$

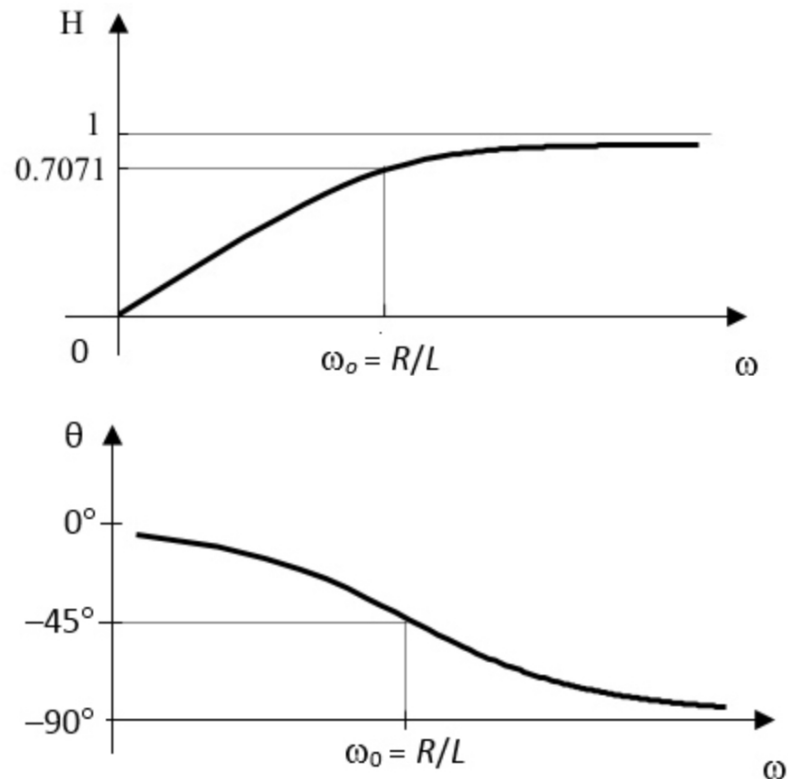
This is a highpass filter. The sketches of H and θ are shown below.



The transfer function I_o/I_i of the RL circuit is given by


$$H(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_o}}$$

2.

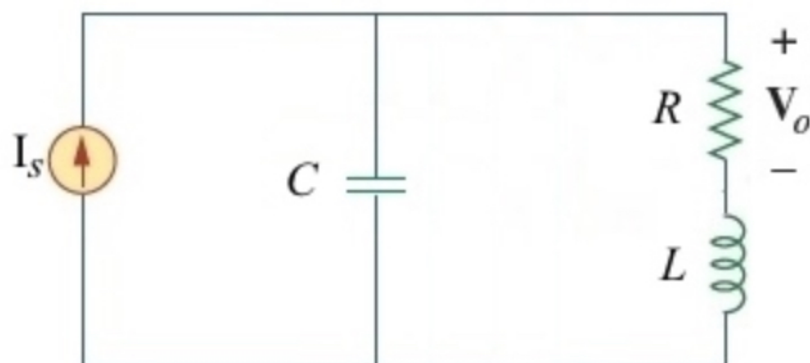value:
10.00 pointsFor the circuit shown below, find $H(s) = V_o/I_s$.

- $H(s) = \frac{Ls}{(LCs^2 + 1)}$
- $H(s) = \frac{Ls}{(LCs^2 + RCs + 1)}$
- $H(s) = \frac{(Rs + L)}{(RCs^2 + LCs + 1)}$
- $H(s) = \frac{R}{(LCs^2 + RCs + 1)}$

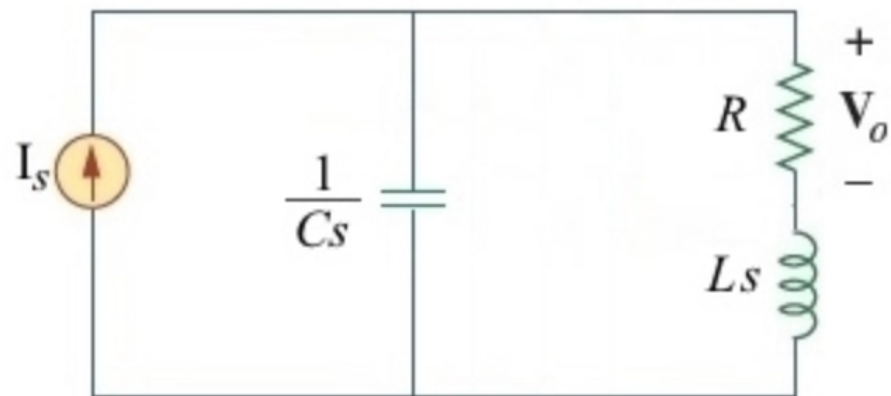Let the capacitor be represented by $1/(Cs)$ and the inductor by Ls . Then, convert the circuit into the s -domain.



By current division, we can represent I_o as

$$I_o = \left(\frac{1}{Cs}\right) \left(\frac{I_s}{\left(\frac{1}{Cs}\right) + R + Ls} \right)$$

which leads to $V_o = (R)I_o$.

$$I_o = \frac{I_s}{(1 + RCs + LCs^2)} \quad \text{or} \quad V_o = \frac{(R)I_s}{(LCs^2 + RCs + 1)}$$

Therefore, $H(s)$ can be written as

$$H(s) = \frac{V_o}{I_s} = \frac{R}{(LCs^2 + RCs + 1)}$$

The transfer function $H(s)$ is given by

$$H(s) = \frac{R}{(LCs^2 + RCs + 1)}$$

3.

value:
10.00 points

A ladder network has a voltage gain of

$$H(\omega) = \frac{30}{(1 + j\omega)(10 + j\omega)}$$

Identify the gain H_{dB} .

- $H_{dB} = 20\log_{10}|3| - 20\log_{10}|1 + j\omega| - 20\log_{10}|10 + j\omega|$
- $H_{dB} = 20\log_{10}|3| - 20\log_{10}|1 + j\omega| - 20\log_{10}|1 + j\omega/10|$
- $H_{dB} = 20\log_{10}|3| - 40\log_{10}|1 + j\omega|$
- $H_{dB} = 20\log_{10}|3| - 20\log_{10}|1 + j\omega| + 20\log_{10}|1 + j\omega/10|$

The given $H(\omega)$ can be rewritten as follows:

$$H(\omega) = \frac{3}{(1 + j\omega)(1 + j\omega/10)}$$

Therefore, $H_{dB} = 20\log_{10}|3| - 20\log_{10}|1 + j\omega| - 20\log_{10}|1 + j\omega/10|$.

The value of gain H_{dB} is given below.

$$H_{dB} = 20\log_{10}|3| - 20\log_{10}|1 + j\omega| - 20\log_{10}|1 + j\omega/10|.$$

4.

value:
10.00 points

A ladder network has a voltage gain of

$$H(\omega) = \frac{30}{(1 + j\omega)(10 + j\omega)}$$

Identify the phase ϕ .

- $\phi = -\tan^{-1}(\omega) - \tan^{-1}(\omega/10)$
- $\phi = \tan^{-1}(\omega) - \tan^{-1}(\omega/10)$
- $\phi = \tan^{-1}(\omega) + \tan^{-1}(10\omega)$
- $\phi = -\tan^{-1}(\omega) - \tan^{-1}(10\omega)$

The phase can be written as

$$\begin{aligned}\angle H(\omega) &= \angle 30 - \angle (1 + j\omega) - \angle (1 + j\omega / 10) \\ &= 0 - \angle (1 + j\omega) - \angle (1 + j\omega / 10)\end{aligned}$$

Therefore, $\phi = -\tan^{-1}(\omega) - \tan^{-1}(\omega/10)$.

The value of phase ϕ is given below.

$$\phi = -\tan^{-1}(\omega) - \tan^{-1}(\omega/10)$$

5.

value:
10.00 points

Given

$$H(\omega) = \frac{175(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

Identify the gain H_{dB} .

- $H_{dB} = 20\log_{10}|7| + 20\log_{10}|1 + j\omega| - 20\log_{10}|j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$
- $H_{dB} = 20\log_{10}|1 + j\omega| - 20\log_{10}|j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$
- $H_{dB} = 20\log_{10}|7| - 20\log_{10}|j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$
- $H_{dB} = 20\log_{10}|7| + 20\log_{10}|1 + j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$

 $H(\omega)$ can be rewritten as


$$H(\omega) = \frac{175}{25} \frac{(1 + j\omega)}{j\omega \left(1 + \frac{10}{25}j\omega + \left(\frac{j\omega}{5}\right)^2 \right)}$$

Therefore, H_{dB} is calculated as follows:

$$H_{dB} = 20\log_{10}|7| + 20\log_{10}|1 + j\omega| - 20\log_{10}|j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$$

$$H_{dB} = 20\log_{10}|7| + 20\log_{10}|1 + j\omega| - 20\log_{10}|j\omega| - 20\log_{10}|1 + 2j\omega/5 + (j\omega/5)^2|$$

6.

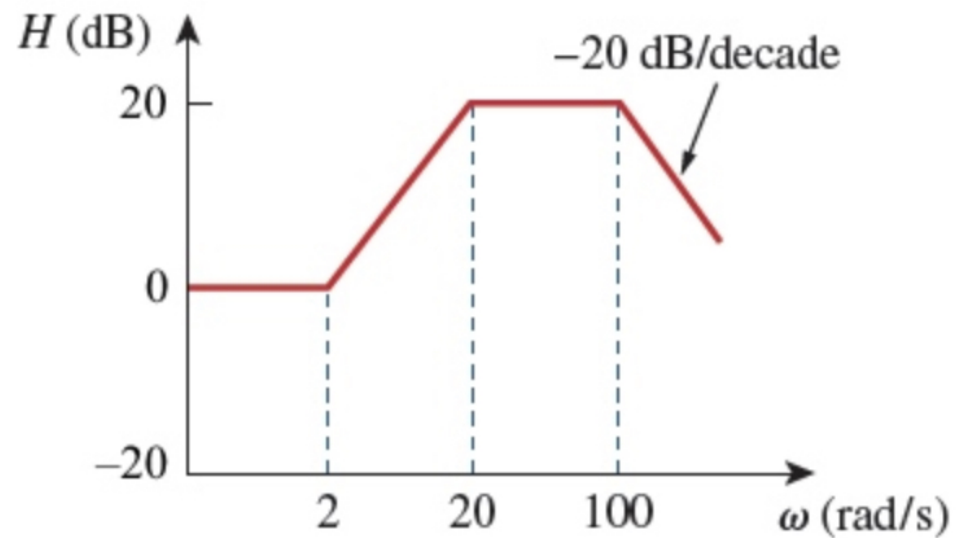value:
10.00 pointsFind the transfer function $H(\omega)$ with the Bode magnitude plot shown below.

- $H(\omega) = \frac{(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$
 $H(\omega) = \frac{100(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$
 $H(\omega) = \frac{100(2 + j\omega)}{(20 + j\omega)(10 + j\omega)}$
 $H(\omega) = \frac{1000(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$

$$0 = 20 \log_{10} k \quad \rightarrow \quad k = 1$$

$$\text{A zero of slope } +20 \text{ dB/dec at } \omega = 2 \quad \rightarrow \quad \mathbf{1 + j\omega / 2}$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 20 \quad \rightarrow \quad \frac{1}{1 + j\omega / 20}$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 100 \quad \rightarrow \quad \frac{1}{1 + j\omega / 100}$$

Hence,

$$\mathbf{H(\omega) = \frac{1(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)} = \frac{1000(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}}$$


The transfer function $H(\omega)$ is mentioned below.

$$\mathbf{H(\omega) = \frac{1000(2 + j\omega)}{(20 + j\omega)(100 + j\omega)}}$$

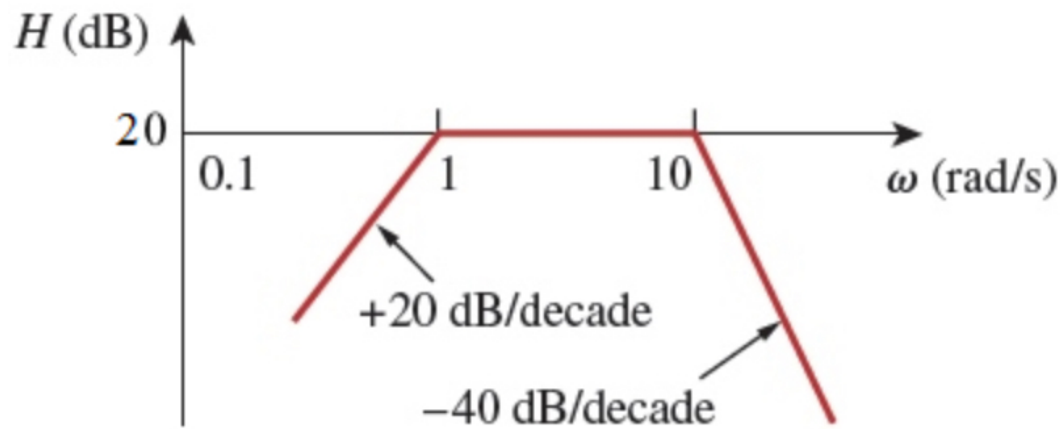7.

value:
10.00 points

The Bode magnitude plot of $H(\omega)$ is shown below. Identify $H(\omega)$.



→ $H(\omega) = \frac{1000j\omega}{(1 + j\omega)(10 + j\omega)^2}$

$H(\omega) = \frac{0.001j\omega}{(1 + j\omega)(10 + j\omega)^2}$

$H(\omega) = \frac{100j\omega}{(1 + j\omega)(10 + j\omega)}$

$H(\omega) = \frac{100j\omega}{(1 + j\omega)(10 + j\omega)^2}$

The initial slope indicates we have $j\omega$ in the numerator. Our approach to plotting requires the plot of $j\omega$ to cross 0dB at $\omega = 1$ rad/s. Since the plot crosses at 20dB, it indicates that the overall gain is 20dB or

$20 = 20\log_{10}|\text{gain}|$, where the gain has to be 10.

A zero of slope +20dB/dec at the origin $\rightarrow j\omega$

A pole of slope -20dB/dec at $\omega = 1$ $\rightarrow \frac{1}{1 + j\omega}$

A pole of slope -40dB/dec at $\omega = 10$ $\rightarrow \frac{1}{(1 + j\omega/10)^2}$

Hence,

$$\mathbf{H}(\omega) = \frac{10j\omega}{(1 + j\omega)(1 + j\omega/10)^2} = \frac{1000j\omega}{(1 + j\omega)(10 + j\omega)^2}$$


The transfer function $\mathbf{H}(\omega)$ is mentioned below.

$$\mathbf{H}(\omega) = \frac{1000j\omega}{(1 + j\omega)(10 + j\omega)^2}$$

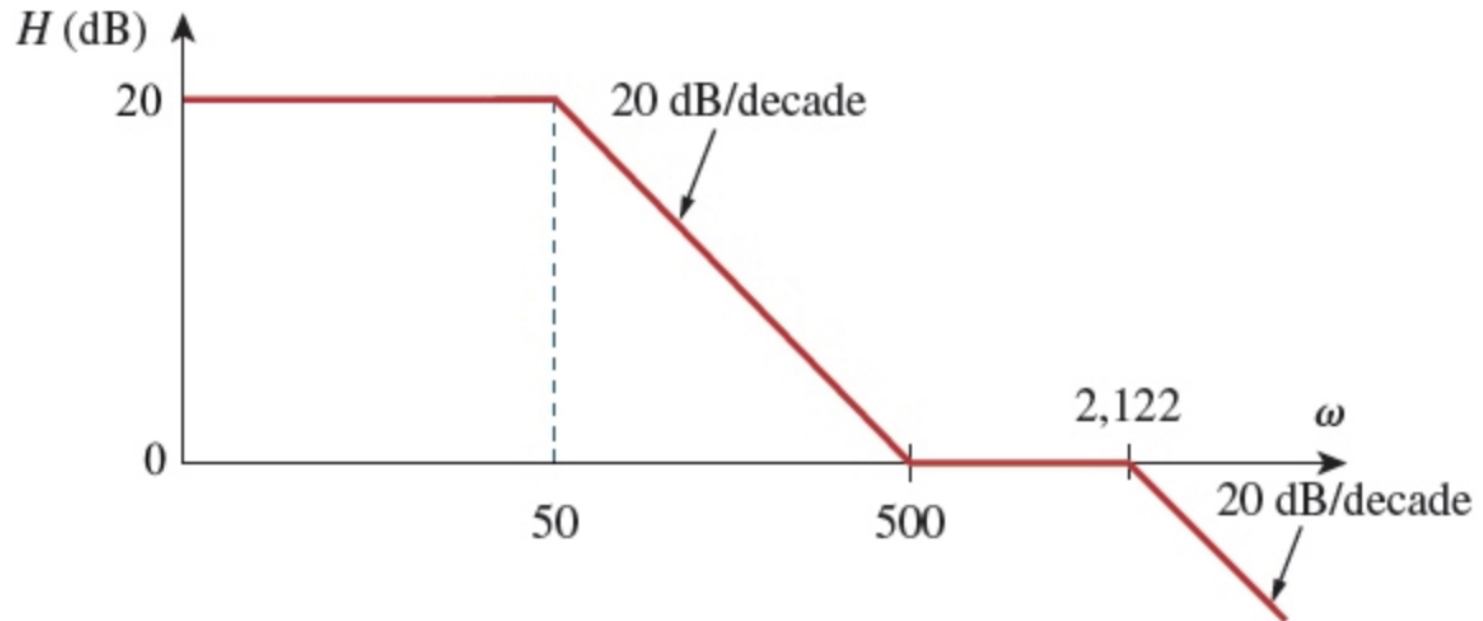8.

value:
10.00 points

The magnitude plot shown below represents the transfer function of the preamplifier. Find $H(s)$.



$H(s) = \frac{(s + 500)}{(s + 50)(s + 2122)}$

$H(s) = \frac{42.44(s + 500)}{(s + 50)(s + 2122)}$

$H(s) = \frac{2122(s + 500)}{(s + 50)(s + 2122)}$

$H(s) = \frac{4.244(s + 500)}{(s + 50)(s + 2122)}$

$$20 = 20 \log_{10} |\text{gain}| \quad \rightarrow \quad \text{gain} = 10$$

There is a pole at $\omega = 50$, which results in

$$\frac{1}{1 + j\omega/50}$$

There is a zero at $\omega = 500$, which results in

$$1 + j\omega/500$$

There is another pole at $\omega = 2122$, which results in

$$\frac{1}{1 + j\omega/2122}$$

Thus,

$$H(\omega) = \frac{10(1 + j\omega/500)}{(1 + j\omega/50)(1 + j\omega/2122)}$$

$$H(s) = \frac{2122(500 + s)}{(s + 50)(s + 2122)}$$

The transfer function $H(s)$ is mentioned below.

$$H(s) = \frac{2122(s + 500)}{(s + 50)(s + 2122)}$$

9.

value:
10.00 points

A series *RLC* network has $R = 4 \text{ k}\Omega$, $L = 80 \text{ mH}$, and $C = 1 \text{ }\mu\text{F}$.

Calculate the impedance at twice the resonant frequency.

The impedance at twice the resonant frequency is $4.000 \pm 2\%$ + j $0.424 \pm 2\%$ $\text{k}\Omega$

Explanation:

Calculate the value of ω_0 .

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(80 \times 10^{-3} \text{ H})(1 \times 10^{-6} \text{ F})}} = 3.536 \text{ krad/s}$$

The impedance at twice the resonant frequency is calculated as follows:

$$Z(2\omega_0) = R + j\left(2\omega_0 L - \frac{1}{2\omega_0 C}\right)$$

$$Z(2\omega_0) = 4000 \text{ }\Omega + j\left(2 \times (3.536 \times 10^3 \text{ rad/s}) \times (80 \times 10^{-3} \text{ H}) - \frac{1}{2 \times (3.536 \times 10^3 \text{ rad/s}) \times (1 \times 10^{-6} \text{ F})}\right) = (4 + j(0.424)) \text{ k}\Omega$$

The impedance at twice the resonant frequency is $Z(2\omega_0) = (4 + j(0.424)) \text{ k}\Omega$.

10.

value:
10.00 points

A series RLC network has $R = 4 \text{ k}\Omega$, $L = 80 \text{ mH}$, and $C = 1 \text{ }\mu\text{F}$.

Calculate the impedance at resonance.

The impedance at resonance is $\text{k}\Omega$.

Explanation:

At resonance, the impedance of the inductor is equal and opposite the impedance of the capacitor, and the impedances cancel.

Therefore, the impedance at resonance is calculated as

$$Z(\omega_0) = R = 4 \text{ k}\Omega$$

The impedance at resonance is $4 \text{ k}\Omega$.