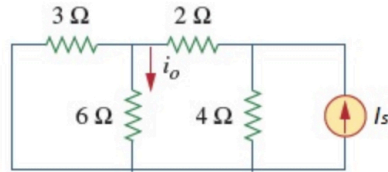


1.

value:  
10.00 points


Assume  $I_o = 1$  A and use linearity to determine  $I_o$  in the given circuit when  $I_s = 13$  A.



The current  $I_o$  is equal to  A.

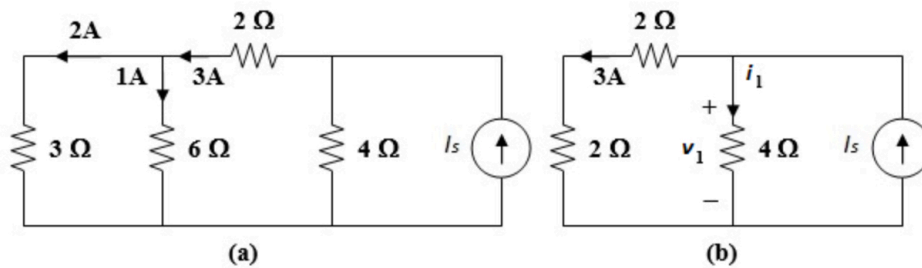**Explanation:**

If  $I_o = 1$  A, the voltage across the 6-Ω resistor is 6 V so that the current through the 3-Ω resistor is 2 A.



The equivalent resistance is given by  $3 \Omega \parallel 6 \Omega = 2 \Omega$ .

Let  $v_o$  be the voltage across the two 2 ohm resistors in series in figure (b)

Since  $v_o = 3 \times 4 = 12$  V,  $i_1 = v_o / 4 = 3$  A.

Hence,  $I_s = 3 + 3 = 6$  A.

When  $I_s = 6$  A,  $I_o = 1$  A.


Since  $I_s = 13$  A,  $I_o = 13 / 6$  A = 2.17 A.

The current  $I_o$  is equal to 2.17 A.

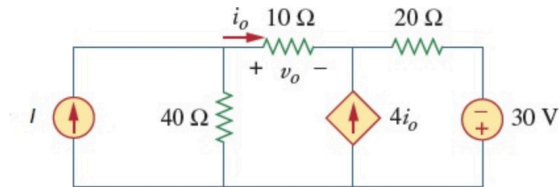2.

value:  
10.00 points

Use the superposition principle to determine the voltage across 10 Ω resistor due to 7-A current source and 30-V voltage source. Determine  $i_o$  and  $v_o$  in the given circuit where  $I = 7$  A.



The voltage across 10 Ω resistor solely due to 7-A current source is  $18.6598 \pm 2\%$  V.


The voltage across the 10 Ω resistor solely due to 30-V voltage source is  $2 \pm 2\%$  V.

The value of  $v_o$  is  $20.66 \pm 2\%$  V.

The value of  $i_o$  is  $2.07 \pm 2\%$  A.
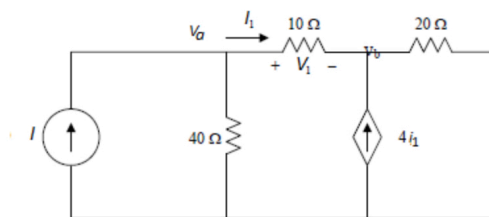
#### Explanation:

Let  $v_o = v_1 + v_2$ , where  $v_1$  and  $v_2$  are due to the 7-A and 30-V sources, respectively. To find  $v_1$ , consider the circuit below.



$$\text{At node a, } 7 = \frac{v_a}{40} + \frac{v_a - v_b}{10} \Rightarrow 280 = 5v_a - 4v_b \quad (1)$$

$$\text{At node b, } -i_1 - 4i_1 + \frac{(v_b - 0)}{20} = 0 \text{ or } v_b = 100i_1$$


$$\text{But } i_1 = (v_a - v_b) / 10, \text{ which leads to } 100(v_a - v_b)10 = v_b \text{ or } v_b = 0.9091 v_a \quad (2)$$

Substituting (2) in (1),

$$5v_a - 3.636v_b = 280 \text{ or } v_a = 205.28 \text{ V and } v_a = 186.62 \text{ V}$$

However,  $v_1 = v_a - v_b = 18.66$  V.

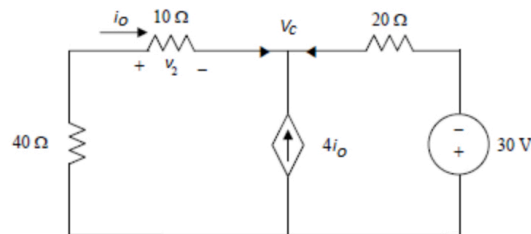To find  $v_2$ , consider the circuit below.



$$\frac{0-v_c}{50} + 4i_o + \frac{(-30-v_c)}{20} = 0$$

But  $i_o = (0 - v_c) / 50$

$$-\frac{5v_c}{50} - \frac{(30+v_c)}{20} = 0 \Rightarrow v_c = -10 \text{ V}$$

Therefore,  $i_2 = \frac{0-v_c}{50} = \frac{0+10}{50} = \frac{1}{5}$

$$v_2 = 10i_2 = 2 \text{ V}$$

Therefore,  $v_o = v_1 + v_2 = 18.66 + 2 = 20.66 \text{ V}$

and  $i_o = v_o / 10 = 2.07 \text{ A}$ .

The voltage across  $10 \Omega$  resistor solely due to 7-A current source is 18.6598 V.

The voltage across the  $10 \Omega$  resistor solely due to 30-V voltage source is 2 V.

The value of  $v_o$  is 20.66 V.


The value of  $i_o$  is 2.07 A.

3.

value:  
10.00 points

---

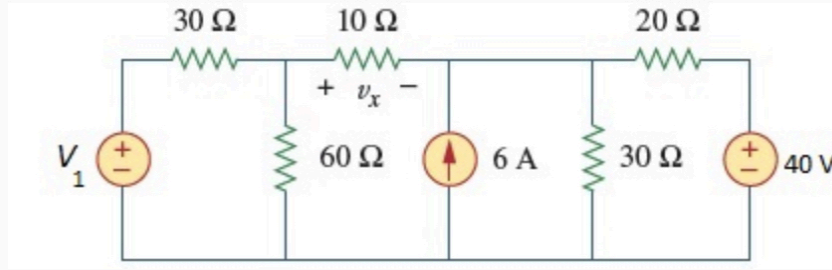Consider the circuit given below where  $V_1 = 84$  V.




Use superposition to obtain  $v_x$  in the given circuit.

The value of  $v_x$  in the given circuit is  $-9.524 \pm 2\%$  V.

Assume  $v_{x1}$ ,  $v_{x2}$ , and  $v_{x3}$  are due to 84-V, 6-A and 40-V sources.

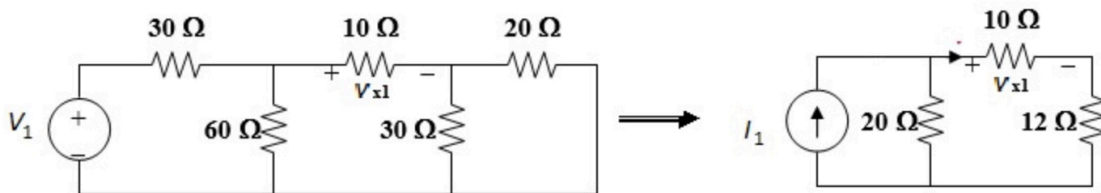**Explanation:**

Let  $v_x = v_{x1} + v_{x2} + v_{x3}$ , where  $v_{x1}$ ,  $v_{x2}$ , and  $v_{x3}$  are due to 84-V, 6-A, and 40-V sources. For  $v_{x1}$ , consider the circuit below.



In the given figure,  $I_1 = V_1 / 30 = 3$  A.

The equivalent resistance is calculated as follows:


$$20 \parallel 30 = 12 \Omega, 60 \parallel 30 = 20 \Omega$$

By using the current division principle,

$$i_o = (20 / (22 + 20)) \times 3 = 1.333 \text{ A}$$

Therefore,  $v_{x1} = 10i_o = 13.333$  V.

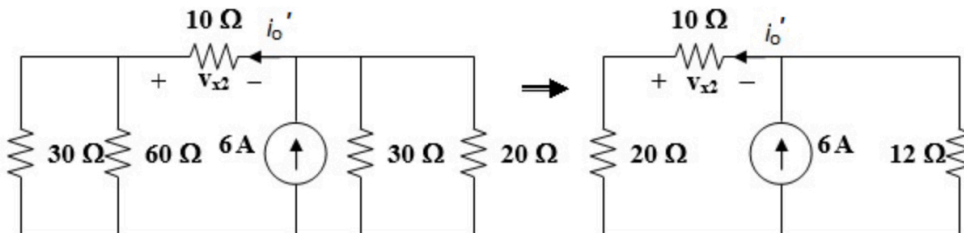For  $v_{x2}$ , consider the circuit below.




The current  $i_o'$  is calculated as follows:

$$i_o' = (12 / (12 + 30)) \times 6 = 72 / 42 \text{ A}$$

Therefore,  $v_{x2} = -10i_o' = -17.143$  V.

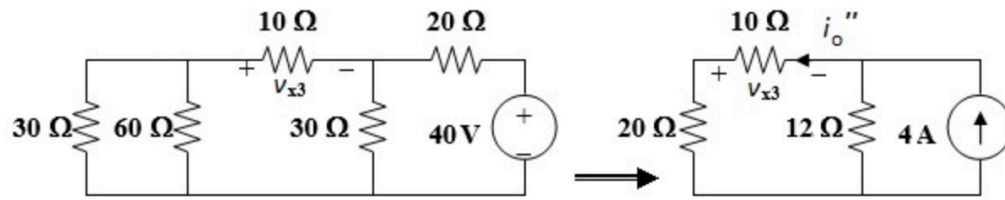For  $v_{x3}$ , consider the circuit below.



The current  $i_o''$  is calculated as follows:

$$i_o'' = (12 / (12 + 30)) \times 2 = 24 / 42 \text{ A}$$

Therefore,  $v_{x3} = -10i_o'' = -5.714 \text{ V}$ .


Hence,  $v_x = v_{x1} + v_{x2} + v_{x3} = 13.333 \text{ V} + (-17.143) \text{ V} + (-5.714) \text{ V} = -9.524 \text{ V}$ .

The value of  $v_x$  in the given circuit is  $-9.524 \text{ V}$ .

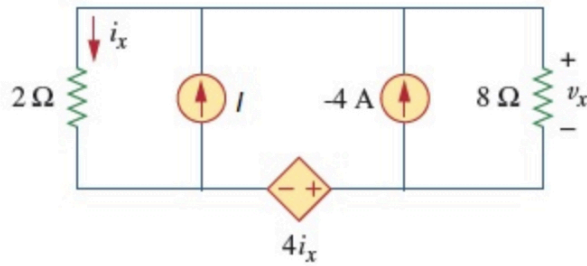5.

value:  
10.00 points

Use superposition to solve for  $v_x$  in the given circuit where  $I = 24$  A.




The value of  $v_x$  in the given circuit is  V.

Assume  $v_1$  and  $v_2$  are due to 4-A and 24-A sources.

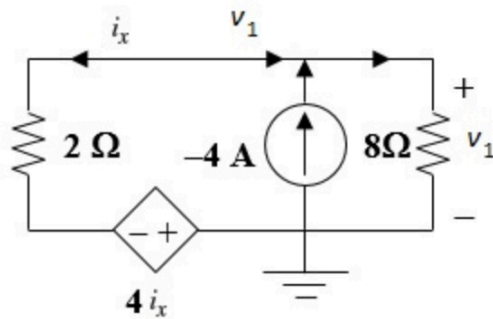**Explanation:**

Let  $v_x = v_1 + v_2$ , where  $v_1$  and  $v_2$  are due to 4-A and 24-A sources, respectively. To find  $v_1$ , consider the given circuit.



$$\frac{(v_1-0)}{8} - (-4) + \left[ \frac{(v_1-(-4i_x))}{2} \right] = 0 \text{ or } (0.125 + 0.5) v_1 = -4 - 2i_x$$


or

$$v_1 = -6.4 - 3.2i_x$$

But,  $i_x = (v_1 - (-4i_x)) / 2$  or  $i_x = 0.5 v_1$

Therefore,  $v_1 = -6.4 + 3.2(0.5v_1)$ , which leads to  $v_1 = 6.4 / 0.6 = 10.667$  V.

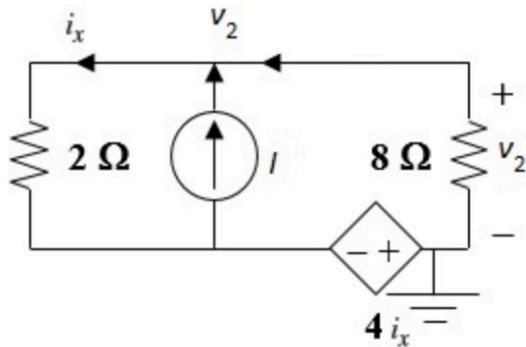To find  $v_2$ , consider the given circuit.



$$\frac{v_2}{8} - 24 + \frac{(v_2-(-4i_x))}{2} = 0 \text{ or } v_2 + 3.2i_x = \frac{24 \times 8}{5} = 38$$


But  $i_x = -0.5 v_2$ . Therefore,  $v_2 + 3.2(-0.5v_2) = 38$ , which leads to  $v_2 = -64.00$  V.  
Hence,  $v_x = v_1 + v_2 = 10.667 + (-64.00) = -53.33$  V.

The value of  $v_x$  in the given circuit is -53.33 V.

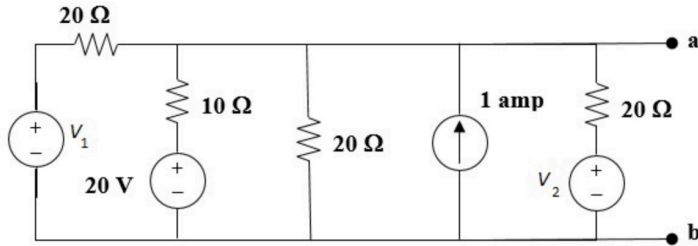6.

value:  
10.00 points

Consider the given figure where  $V_1 = 30\text{ V}$  and  $V_2 = 35\text{ V}$ . Use source transformations to reduce the circuit between terminals a and b to a voltage source in series with a single resistor.




The equivalent resistor is  $4 \pm 2\%$   $\Omega$ .

The equivalent voltage is  $25 \pm 2\%$  V.

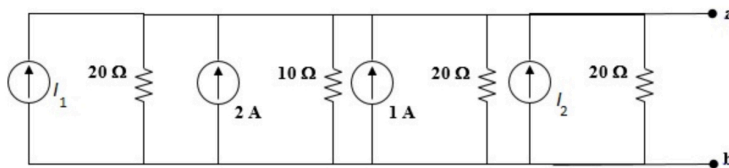**Explanation:**

This problem is most easily solved by converting all the voltage sources in series with resistors to current sources in parallel with resistors.



In the above figure,  $I_1 = 30 / 20 = 2\text{ A}$  and  $I_2 = 35 / 20 = 1.75\text{ A}$ .

Now all we need is to add the current sources together algebraically and place all the resistors in parallel and combine them. Finally, all we need to do is to change the current source and resistance back into a single voltage source in series with a resistor.

The total current =  $2 + 2 + 1 + 1.75 = 6.25\text{ A}$ .

The equivalent resistance is calculated as follows:

$$\frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{10} + \frac{1}{20} + \frac{1}{20} \Rightarrow R_{eq} = 4\ \Omega$$

Finally,  $V_{eq} = 6.25 \times 4 = 25\text{ V}$ .

The equivalent resistor is  $4\ \Omega$ .


The equivalent voltage is  $25\text{ V}$ .



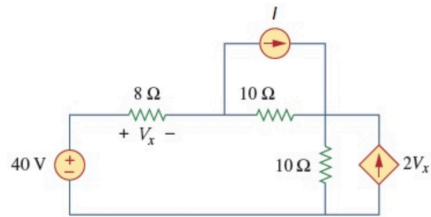7.

value:  
10.00 points


Use source transformation to find the voltage  $V_x$  in the given circuit where  $I = 7$  A.



The voltage  $V_x$  in the given circuit is  V.

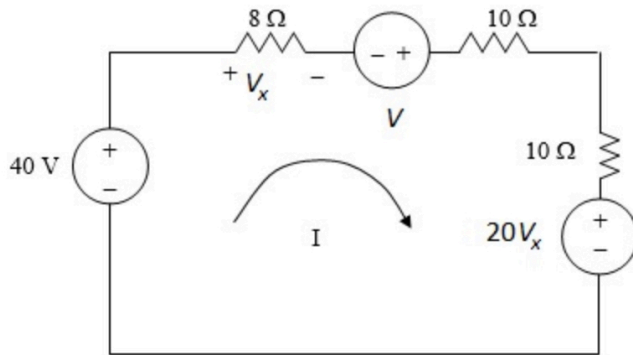**Explanation:**

Transforming the two current sources in parallel with the resistors into their voltage source equivalents yields a 70-V source in series with a 10-Ω resistor and a  $20V_x$ -V sources in series with a 10-Ω resistor. We now have the following circuit.



In the above figure,  $V = 7 \times 10 = 70$  V.

We now write the following mesh equation and constraint equation, which will lead to a solution for  $V_x$ ,

$$28I - (40 + 70) + 20V_x = 0 \text{ or } 28I + 20V_x = 110$$


But,  $V_x = 8I$ , which leads to  $28I + 160I = 110 \rightarrow I = 0.585$  A or  $V_x = 4.681$  V.

The voltage  $V_x$  in the given circuit is 4.681 V.

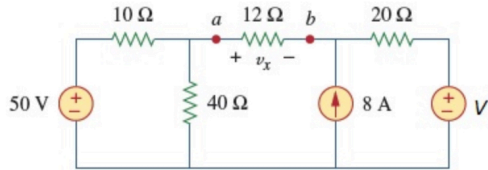8.

value:  
10.00 points


Apply source transformation to find  $v_x$  in the given circuit where  $V = 55$  V.




The value of  $v_x$  in the given circuit is  V.

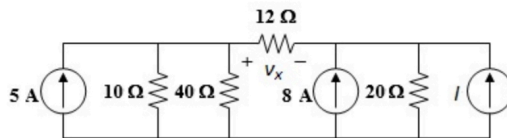**Explanation:**

Transforming the voltage sources to current sources gives the following circuit where  $10 \parallel 40 = 8 \Omega$  and  $I = 55 / 20 = 2.75$  A.



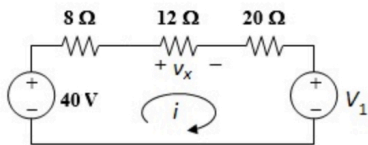Transforming the current sources to voltage sources yields the following circuit where  $V_1 = (2.75 + 8) \times 20 = 215$  V.




Applying KVL to the loop,  
 $-40 + (8 + 12 + 20)i + 215 = 0$  leads to  $i = -4.375$  A  
 Therefore,  $v_x = 12i = 12 \times -4.375 = -52.5$  V.

The value of  $v_x$  in the given circuit is -52.5 V.

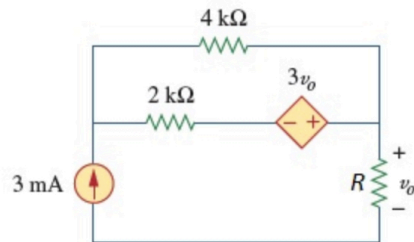9.

value:  
10.00 points


Use source transformation to find  $v_o$  in the circuit in the following figure if  $R = 2 \text{ k}\Omega$ .



The voltage  $v_o$  is  V.

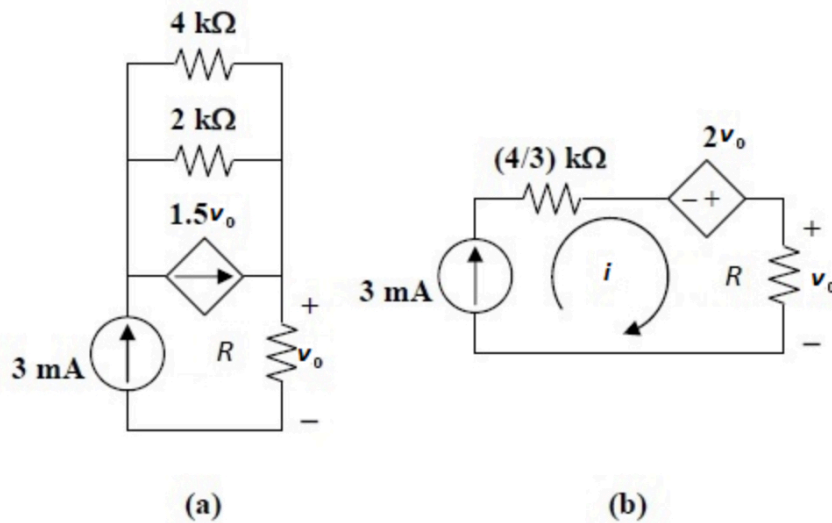**Explanation:**

Transform the dependent voltage source to a current source as shown in Fig. (a).  
The resistances  $3 \text{ k}\Omega$  and  $4 \text{ k}\Omega$  are in parallel. The equivalent resistance =  $2 \parallel 4 = (4/3) \text{ k}\Omega$ .




It is clear that  $i = 3 \text{ mA}$ , which leads to  $v_o = 2 \times 1000 i = 6 \text{ V}$ .

The voltage  $v_o$  is 6 V.

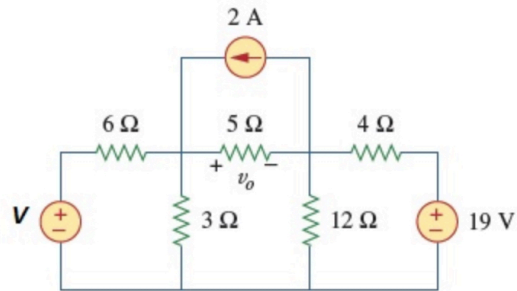10. value:  
10.00 points


Use Thevenin's theorem to find  $v_o$  in the given circuit where  $V = 8$  V.




The value of  $v_o$  in the given circuit is  mV.

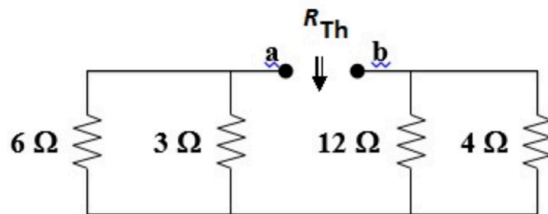**Explanation:**

To find  $R_{\text{Th}}$ , consider the following circuit.



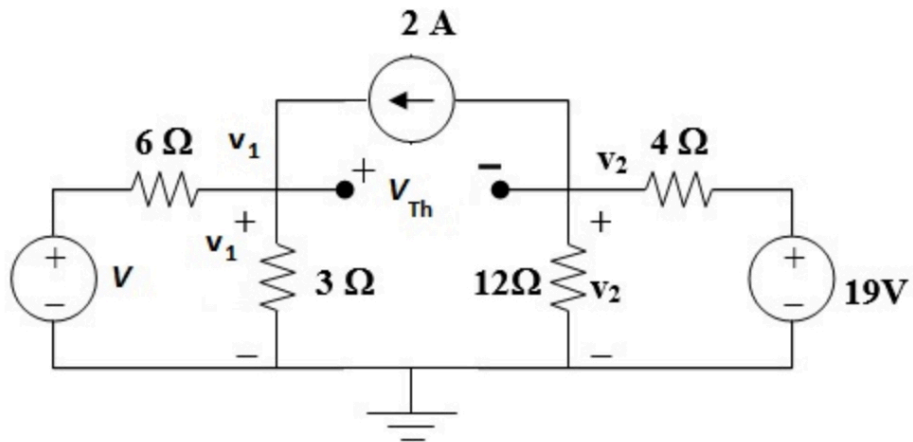$R_{\text{Th}} = R_{ab} = 6 \parallel 3 + 12 \parallel 4 = 2 + 3 = 5\ \Omega$   
To find  $V_{\text{Th}}$ , consider the following circuit.




At node 1,

$$2 + (8 - v_1) / 6 = v_1 / 3, \text{ or } v_1 = 6.67$$

At node 2,

$$(19 - v_2) / 4 = 2 + v_2 / 12, \text{ or } v_2 = 33 / 4$$
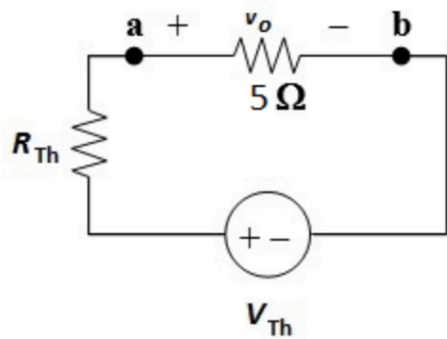
$$\text{But, } -v_1 + V_{Th} + v_2 = 0, \text{ or } V_{Th} = v_1 - v_2 = 6.67 - 33 / 4 = -1.58 \text{ V.}$$




$$v_o = V_{Th} / 2 = -1.58 \times 1000 / 2 = -792 \text{ mV}$$

The value of  $v_o$  in the given circuit is -792 mV.

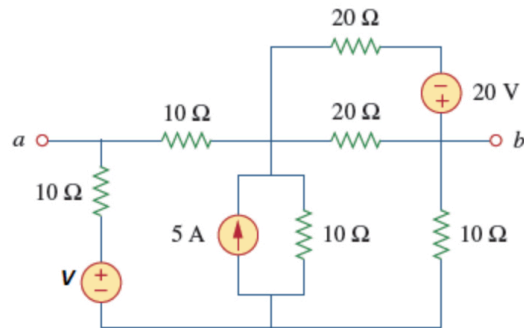11.

value:  
10.00 points

For the circuit given below, find the Thevenin equivalent between terminals  $a$  and  $b$ , where  $V = 34$  V.




$$R_{\text{Th}} = 10 \pm 2\% \ \Omega$$

$$V_{\text{Th}} = 12.0 \pm 2\% \ \text{V}$$

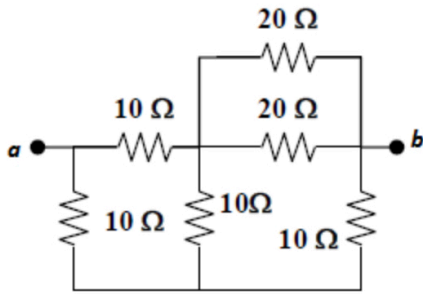
**Explanation:**

The Thevenin equivalent between terminals  $a$  and  $b$  is calculated as follows:  
To find  $R_{\text{Th}}$ , consider the circuit given below:



$$20 \parallel 20 = 10 \Omega$$

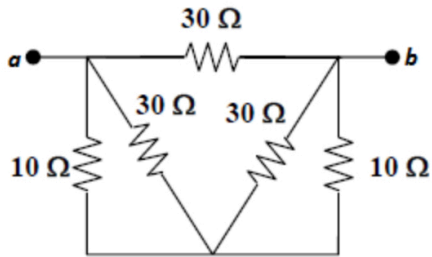
Transform the ywe sub-network to a delta as shown in the circuit given below:



$$10 \parallel 30 = 7.5 \Omega$$

$$R_{Th} = R_{ab} = 30 \parallel (7.5 + 7.5) = 10 \Omega$$

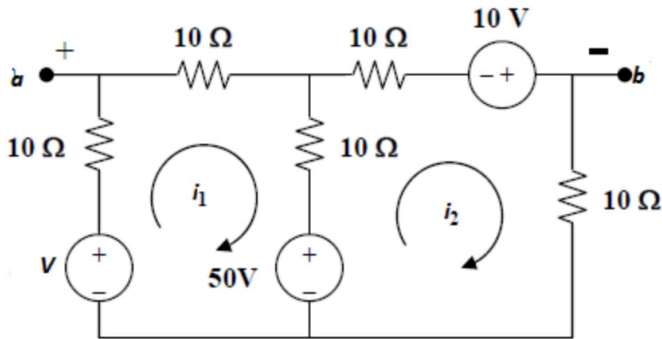To find  $V_{Th}$ , we transform the 20-V and the 5-A sources. We obtain the circuit given below:



$$\text{For loop 1, } -34 + 50 + 30i_1 - 10i_2 = 0 \quad (1)$$

$$\text{For loop 2, } -50 - 10 + 30i_2 - 10i_1 = 0 \quad (2)$$

Solving (1) and (2),  $i_1 = 0.15 \text{ A}$  and  $i_2 = 2.05 \text{ A}$ .

Applying KVL to the output loop,

$$-V_{ab} - 10i_1 + 34 - 10i_2 = 0 \rightarrow V_{ab} = 12.0 \text{ V}$$

$$V_{Th} = V_{ab} = 12.0 \text{ V.}$$


The values of the Thevenin equivalent between terminals  $a$  and  $b$  are as follows:

$$R_{Th} = 10 \Omega$$

$$V_{Th} = 12.0 \text{ V}$$

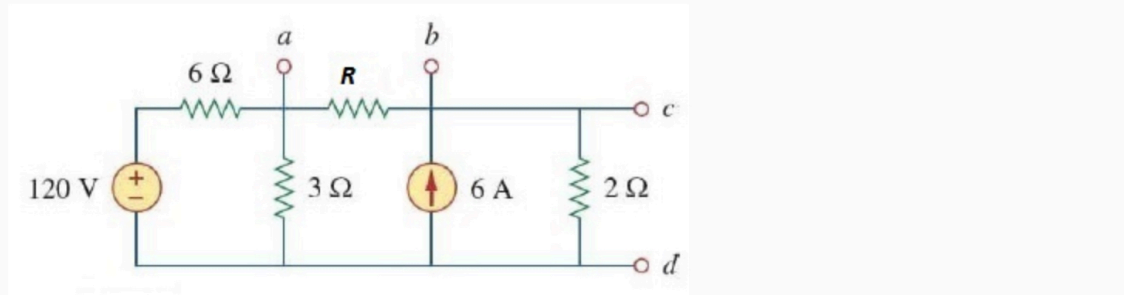12. value: 10.00 points

Given the circuit in the following figure, obtain the Norton equivalent as viewed from the following terminals if  $R = 6 \Omega$ .




Terminals  $a-b$

$$R_N = 2.40 \pm 2\% \Omega$$


$$I_N = 7.00 \pm 2\% \text{ A}$$

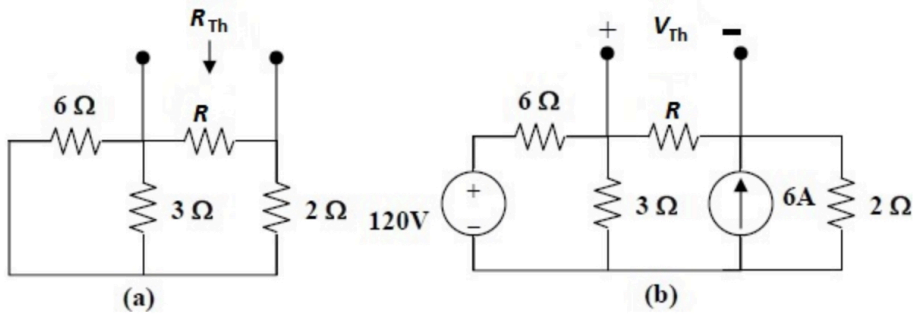**Explanation:**

From the circuit in Fig. (a),  
 $R_N = 6 \parallel (2 + 6 \parallel 3) = 2.40 \Omega$



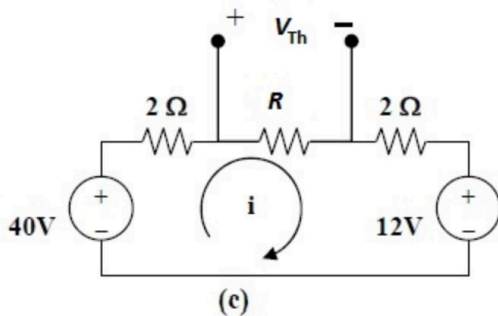For  $I_N$  or  $V_{Th}$ , consider the circuit in Fig.(b). After some transformations, the circuit becomes that shown in Fig. (c).






Applying KVL to the circuit in Fig. (c),  
 $-40 + (2.40 + 6 + 2)i + 12 = 0$ , which gives  $i = 2.80$   
 $V_{Th} = 6i = 6 \times 2.80 = 16.80$ . Therefore,  $I_N = V_{Th} / R_N = 7.00$  A.

The calculated parameters are as follows:  
 $R_N = 2.40 \Omega$   
 $I_N = 7.00$  A

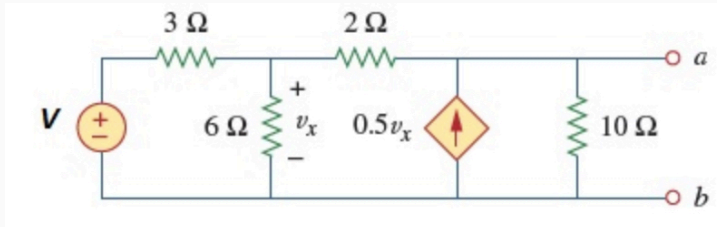13. value:  
10.00 points

Consider the given circuit where  $V = 90$  V.




Determine the Norton equivalent circuit at terminals  $a$ - $b$  of the given circuit.

$$R_N = 10.00 \pm 2\% \Omega$$

$$I_N = 30.00 \pm 2\% \text{ A}$$

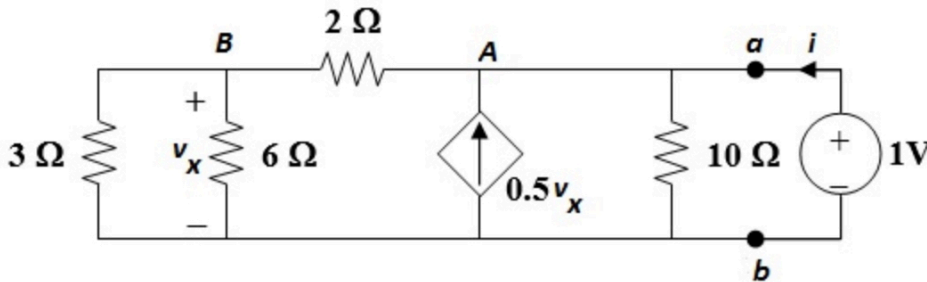**Explanation:**

To find  $R_{Th}$ , remove the 90-V source and insert a 1-V source at  $a$ - $b$ , as shown in the given figure.




We apply nodal analysis. At node A,  
 $i + 0.5v_x = (1/10) + (1 - v_x)/2$ , or  $i + v_x = 0.6$  (1)

At node B,  
 $(1 - v_o)/2 = (v_x/3) + (v_x/6)$ , and  $v_x = 0.5$  (2)

From (1) and (2),  $i = 0.1$  and  $R_{Th} = 1/i = 10.00 \Omega$

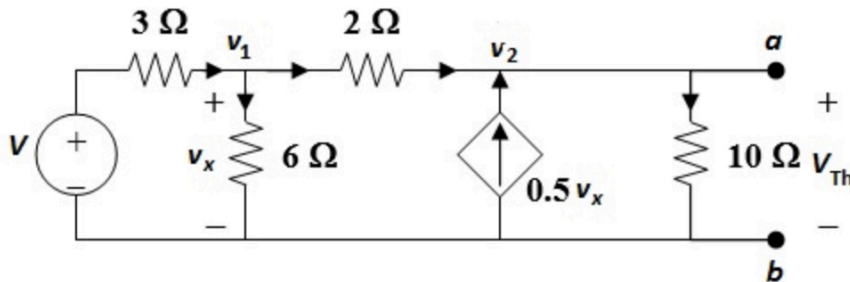To get  $V_{Th}$ , consider the circuit in the figure below.



At node 1,  $(90 - v_1) / 3 = (v_1 / 6) + (v_1 - v_2) / 2$ , or  $180 = 6v_1 - 3v_2$  (3)

At node 2,  $0.5v_x + (v_1 - v_2) / 2 = v_2 / 10$ ,  $v_x = v_1$  and  $v_1 = 0.6v_2$  (4)

From (3) and (4),  $v_2 = V_{Th} = 300.00 \text{ V}$

$I_N = V_{Th} / R_{Th} = 30.00 \text{ A}$

$R_N = R_{Th} = 10.00 \Omega$


The calculated parameters are as follows:

$R_N = 10.00 \Omega$

$I_N = 30.00 \text{ A}$

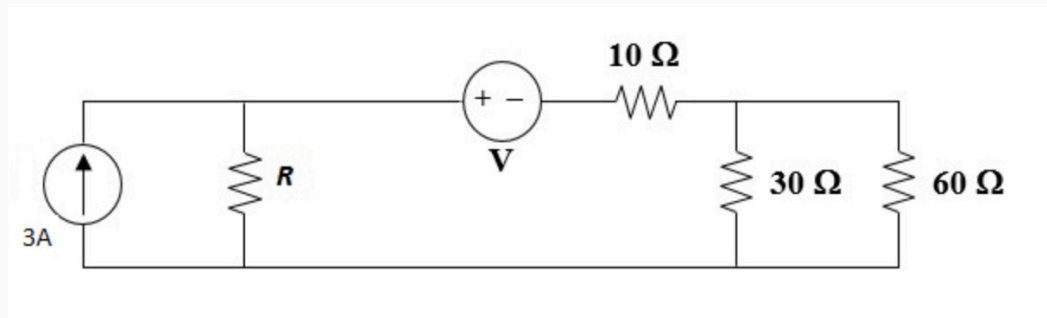14. value:  
10.00 points

Consider the given circuit where  $V = 60$  V.



Now let  $R = 0 \Omega$ ,  $110 \Omega$ , and  $\infty$ . Calculate the power delivered to the 30- $\Omega$  resistor in each case.

The power delivered to the 30- $\Omega$  resistor when  $R = 0 \Omega$  is  $53.33 \pm 2\%$  W.

The power delivered to the 30- $\Omega$  resistor when  $R = 110 \Omega$  is  $49.59 \pm 2\%$  W.

The power delivered to the 30- $\Omega$  resistor when  $R = \infty$  is  $120 \pm 2\%$  W.

#### Explanation:

When  $R = 0 \Omega$ , the Thevenin equivalent resistance is calculated by the formula  
 $R_{eq} = 60(0 + 10) / (0 + 10 + 60) = 8.5714 \Omega$ .

The Thevenin voltage is calculated by the formula:

$$V_{oc} = 60[(3R - 60)/(R + 10 + 60)] = -51.43 \text{ V.}$$

The power is calculated by the formula:

$$P = \frac{\left(\frac{V_{oc} \times 30}{R_{eq} + 30}\right)^2}{30} = 53.33 \text{ W}$$

When  $R = 110 \Omega$ , the Thevenin equivalent resistance is calculated by the formula:

$$R_{eq} = 60(110 + 10) / (110 + 10 + 60) = 40 \Omega.$$

The Thevenin voltage is calculated by the formula:

$$V_{oc} = 60[(3R - 60)/(R + 10 + 60)] = 90.00 \text{ V.}$$

The power is calculated by the formula:

$$P = \frac{\left(\frac{V_{oc} \times 30}{R_{eq} + 30}\right)^2}{30} = 49.59 \text{ W}$$

When  $R = \infty$ , the Thevenin equivalent resistance is calculated by the formula:

$$R_{eq} = 60 \Omega.$$

The Thevenin voltage is calculated by the formula:

$$V_{oc} = 180 \text{ V.}$$

The power is calculated by the formula:

$$P = \frac{\left(\frac{V_{oc} \times 30}{R_{eq} + 30}\right)^2}{30} = 120 \text{ W}$$

The power delivered to the 30- $\Omega$  resistor when  $R = 0 \Omega$  is 53.33 W.

The power delivered to the 30- $\Omega$  resistor when  $R = 110 \Omega$  is 49.59 W.

The power delivered to the 30- $\Omega$  resistor when  $R = \infty$  is 120 W.