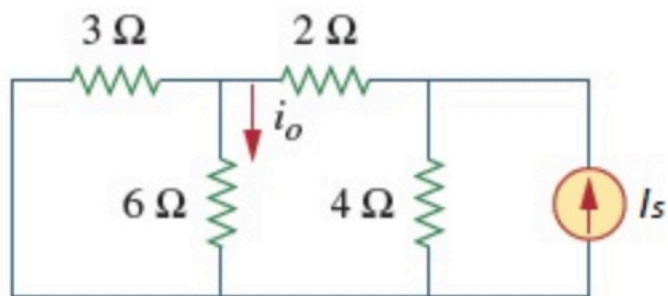


1.

value:
10.00 points

Assume $I_o = 1$ A and use linearity to determine I_o in the given circuit when $I_S = 13$ A.




The current I_o is equal to A.

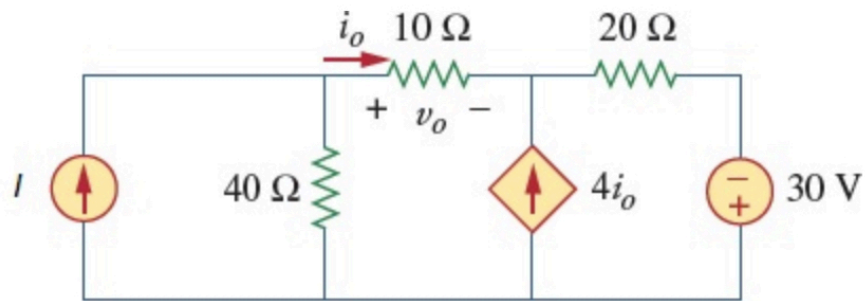2.

value:
10.00 points

Use the superposition principle to determine the voltage across $10\ \Omega$ resistor due to 5-A current source and 30-V voltage source. Determine i_o and v_o in the given circuit where $I = 5\ \text{A}$.



The voltage across $10\ \Omega$ resistor solely due to 5-A current source is V.

The voltage across the $10\ \Omega$ resistor solely due to 30-V voltage source is V.


The value of v_o is V.

The value of i_o is A.

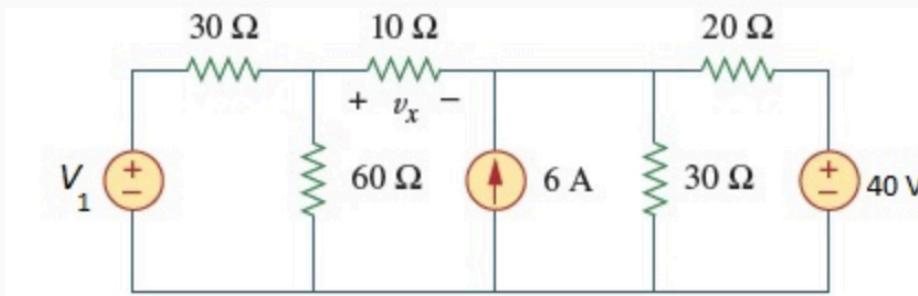3.

value:
10.00 points

Consider the circuit given below where $V_1 = 114$ V.



Use superposition to obtain v_x in the given circuit.


The value of v_x in the given circuit is V.

Assume v_{x1} , v_{x2} , and v_{x3} are due to 114-V, 6-A and 40-V sources.

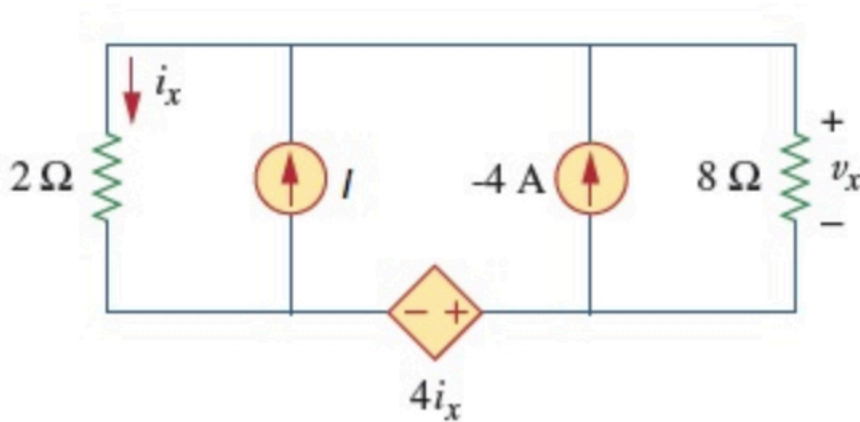5.

value:
10.00 points

Use superposition to solve for v_x in the given circuit where $I = 24$ A.




The value of v_x in the given circuit is V.
Assume v_1 and v_2 are due to 4-A and 24-A sources.

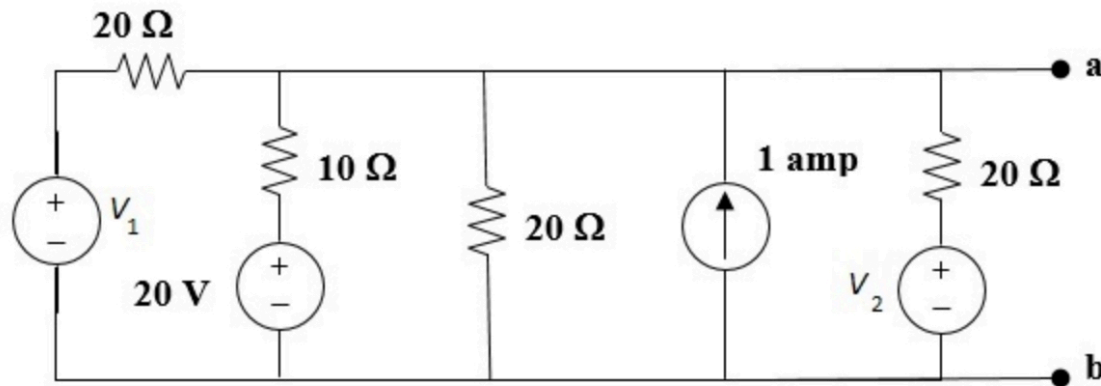6.

value:
10.00 points

Consider the given figure where $V_1 = 40\text{ V}$ and $V_2 = 30\text{ V}$. Use source transformations to reduce the circuit between terminals a and b to a single voltage source in series with a single resistor.




The equivalent resistor is Ω.
The equivalent voltage is V.

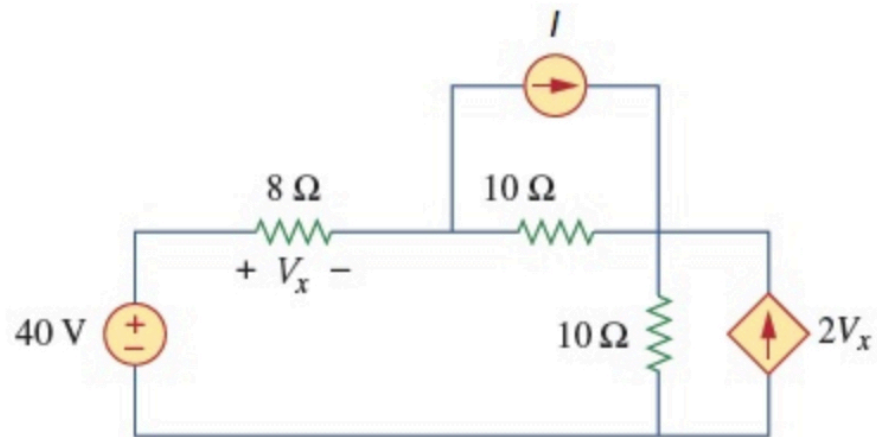7.

value:
10.00 points

Use source transformation to find the voltage V_x in the given circuit where $I = 9$ A.




The voltage V_x in the given circuit is V.

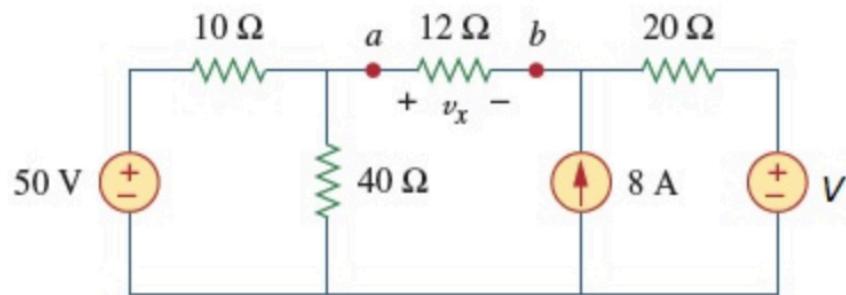8.

value:
10.00 points

Apply source transformation to find v_x in the given circuit where $V = 70$ V.




The value of v_x in the given circuit is V.

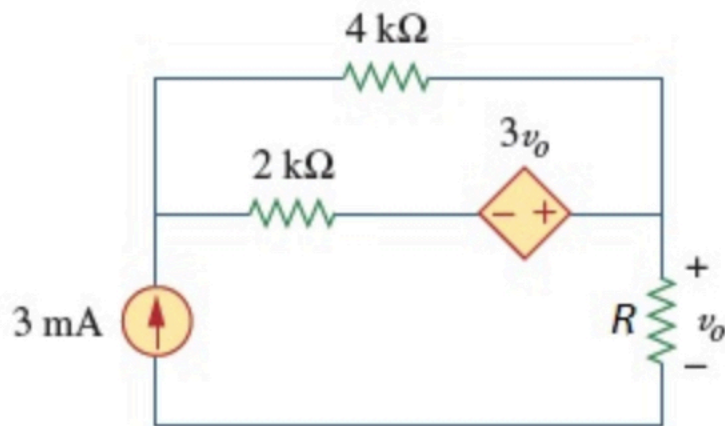9.

value:
10.00 points

Use source transformation to find v_o in the circuit in the following figure if $R = 5 \text{ k}\Omega$.




The voltage v_o is V.

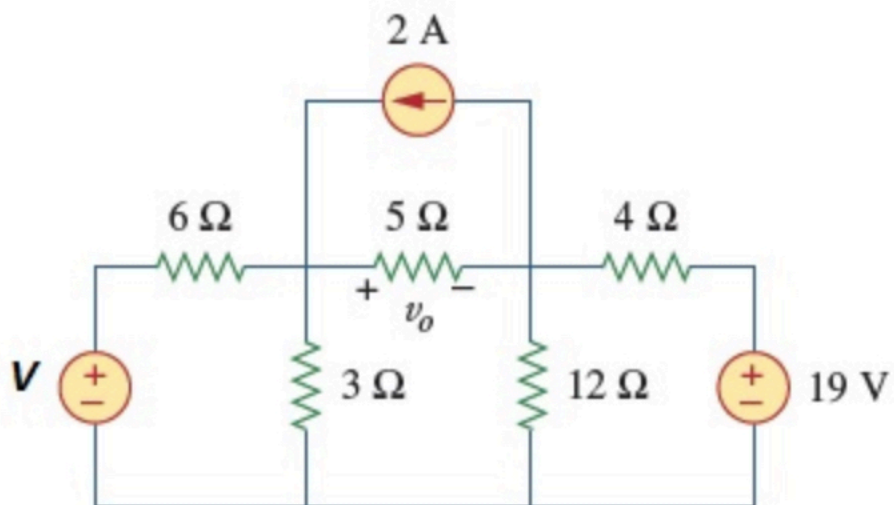10.

value:
10.00 points

Use Thevenin's theorem to find v_o in the given circuit where $V = 8$ V.




The value of v_o in the given circuit is mV.

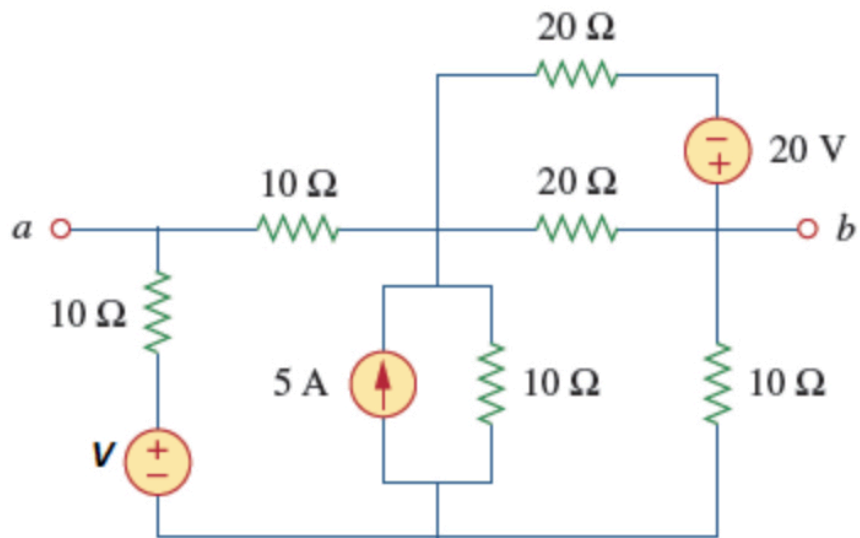11.

value:
10.00 points

For the circuit given below, find the Thevenin equivalent between terminals a and b , where $V = 42$ V.




$R_{Th} =$ Ω

$V_{Th} =$ V

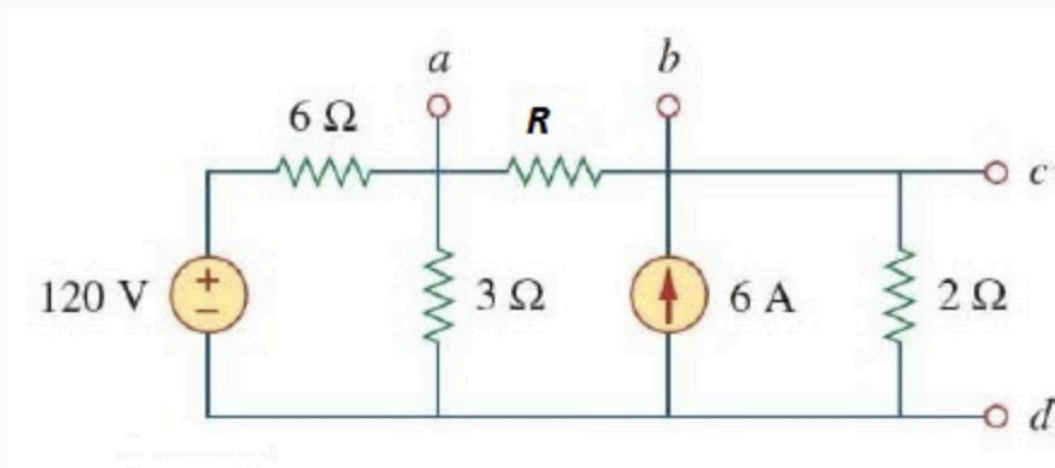12.

value:
10.00 points

Given the circuit in the following figure, obtain the Norton equivalent as viewed from the following terminals if $R = 12 \Omega$.




Terminals $a-b$

$$R_N = \boxed{} \Omega$$

$$I_N = \boxed{} \text{ A}$$


13.

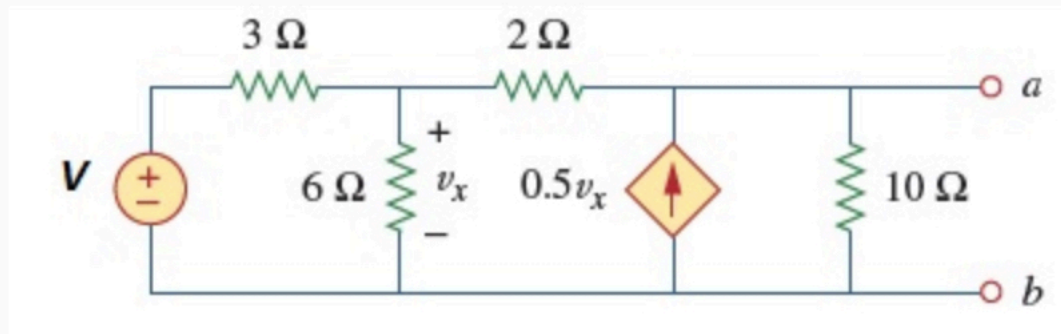value:
10.00 pointsConsider the given circuit where $V = 85 \text{ V}$.Determine the Norton equivalent circuit at terminals a - b of the given circuit.

$$R_N = \boxed{} \Omega$$

$$I_N = \boxed{} \text{ A}$$

14.

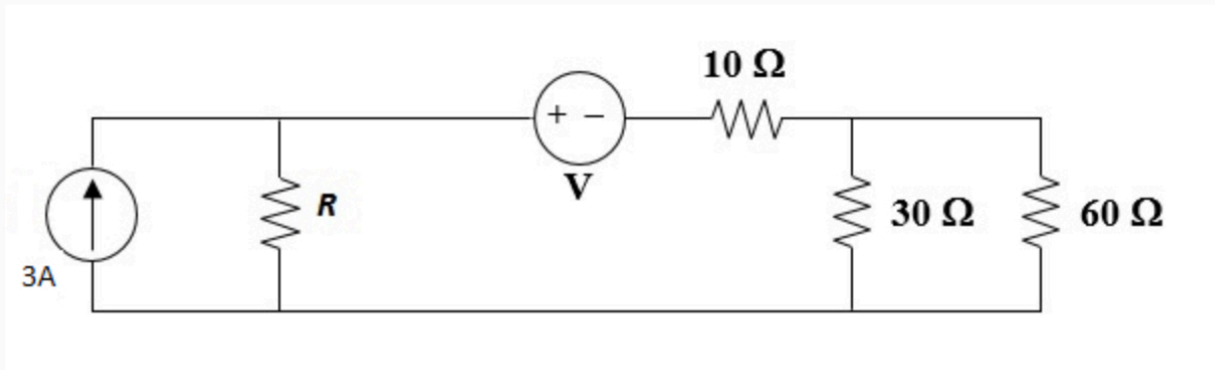value:
10.00 pointsConsider the given circuit where $V = 80$ V.

Now let $R = 0\ \Omega$, $110\ \Omega$, and ∞ . Calculate the power delivered to the $30\text{-}\Omega$ resistor in each case.

The power delivered to the $30\text{-}\Omega$ resistor when $R = 0\ \Omega$ is W.

The power delivered to the $30\text{-}\Omega$ resistor when $R = 110\ \Omega$ is W.

The power delivered to the $30\text{-}\Omega$ resistor when $R = \infty$ is W.