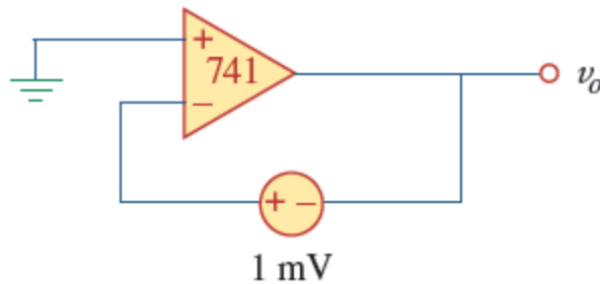


1.

value:
10.00 points


A 741 op amp shown in the circuit given below has an open-loop voltage gain of 70000, an input resistance of 2 M Ω , and an output resistance of 150 Ω . Calculate the output voltage v_o in the op amp circuit.



The output voltage of the op amp is mV.

Explanation:

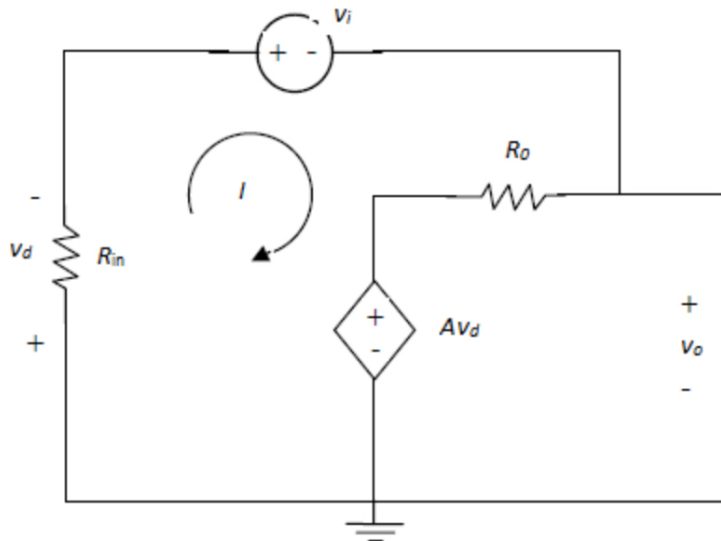The formula to find the output voltage is derived as follows:



$$(R_o + R_i)I + v_i + Av_d = 0$$

$$\text{But } v_d = R_i I$$

$$v_i + (R_o + R_i + R_i A)I = 0$$

$$I = \frac{-v_i}{R_o + (1 + A)R_i} \quad \text{_____ (1)}$$

$$-Av_d - R_o I + v_o = 0$$

$$v_o = Av_d + R_o I = (R_o + R_i A)I$$

Substituting for I in equation(1),

$$v_o = - \left(\frac{R_o + R_i A}{R_o + (1 + A)R_i} \right) v_i$$

Then, the output voltage is calculated as follows:

$$v_o = - \left(\frac{R_o + R_i A}{R_o + (1 + A)R_i} \right) v_i$$

$$v_o = - \left(\frac{150 \Omega + (2 \text{ M}\Omega \times 70000)}{150 \Omega + (1 + 70000) \times 2 \text{ M}\Omega} \right) \times 1 \text{ mV}$$


$$v_o = - 0.999986 \text{ mV}$$

The output voltage is - 0.999986 mV.

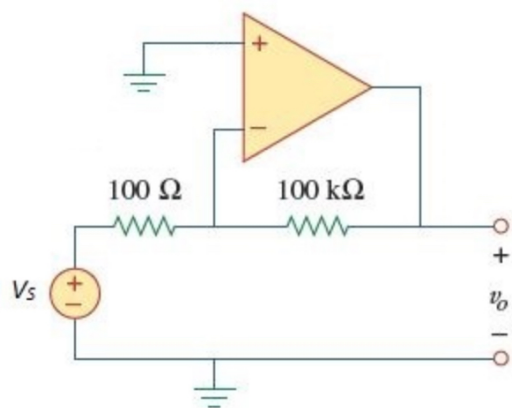2.

value:
10.00 points


The op amp in the circuit given below has $R_f = 100 \text{ k}\Omega$, $R_o = 100 \Omega$, $v_s = 1 \text{ mV}$, and $A = 100,000$.



Calculate the output voltage v_o for the given op amp circuit.

The output voltage v_o for the given op amp circuit is mV.

Explanation:

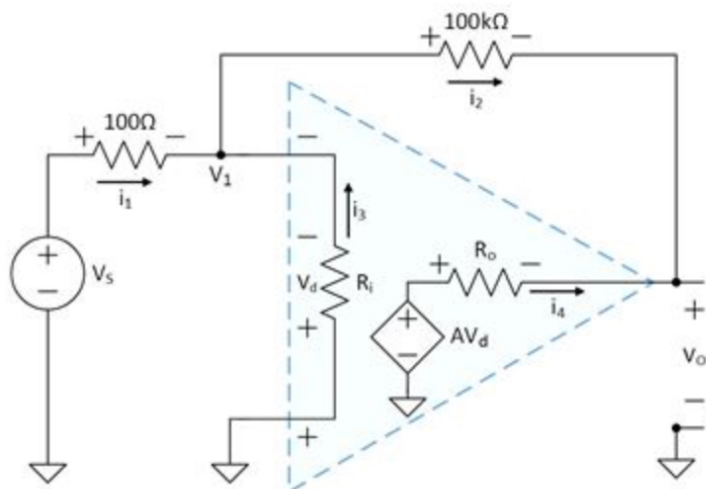

At node V_1 , $i_1 - i_2 + i_3 = 0 \text{ A}$

$$\frac{v_s - V_1}{100 \Omega} - \frac{V_1 - v_o}{100 \text{ k}\Omega} + \frac{-V_1}{R_i} = 0 \text{ A}$$

which leads to $V_1 = \frac{1000 v_s + v_o}{1002}$

At node v_o , $i_2 + i_4 = 0 \text{ A}$

$$\frac{V_1 - v_o}{100 \text{ k}\Omega} + \frac{AV_d - v_o}{R_o} = 0 \text{ A}$$

But, $V_d = -V_1$ and $A = 100,000$ so

$$V_1 - v_o + 1000(-100,000V_1 - v_o) = 0$$

$$v_o = \frac{-99,999,999}{1001} V_1 = \frac{-99,999,999}{1001} \left[\frac{1000 v_s + v_o}{1002} \right]$$

This gives us $\frac{v_o}{v_s} = -990.07$


If $v_s = 1 \text{ mV}$, then $v_o = -0.9901 \text{ mV}$

The output voltage v_o for the given op amp circuit is -0.9901 mV .

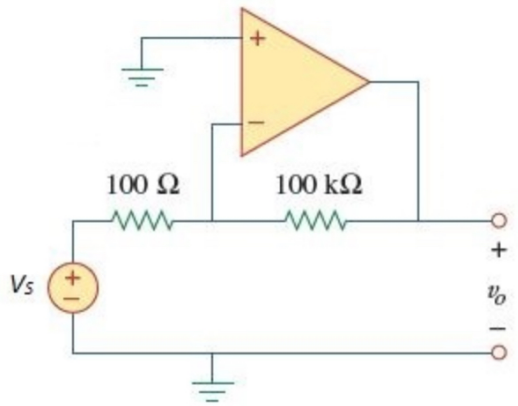3.

value:
10.00 points

The op amp in the circuit given below has $R_i = 100 \text{ k}\Omega$, $R_o = 100 \Omega$, $v_s = 1 \text{ mV}$, and $A = 100,000$.



Calculate the differential voltage v_d .

The differential voltage v_d is nV.


Explanation:

The differential voltage is calculated as follows:

$$v_o = Av_d = 100,000 v_d$$

$$\text{Then, } v_d = -\frac{v_o}{10^5} = -\frac{-0.99 \text{ mV}}{10^5} = -9.90 \text{ nV}$$

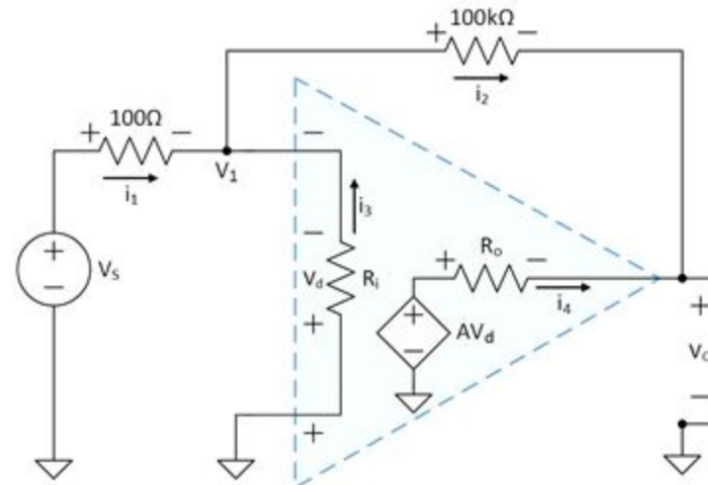
The differential voltage v_d is -9.90 nV .



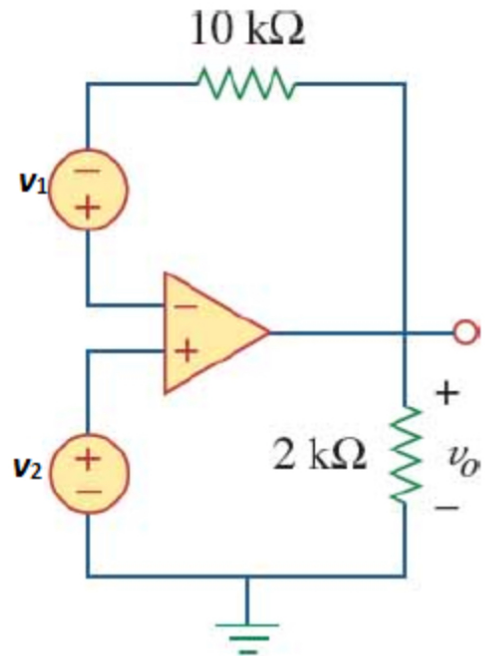4.

value:
10.00 points

Calculate the output voltage of the op amp circuit given below, where $v_1 = 2.0$ V and $v_2 = 1.4$ V.



The output voltage of the op amp circuit is V.

Explanation:

The output voltage is calculated as follows:


Since $v_a = v_b = 1.4$ V and $i_a = 0$, no current flows through the $10\text{-k}\Omega$ resistance.

Using the compensatory circuit concept, from the given figure we get, $-v_a + 2.0 + v_o = 0$.

$$v_o = v_a - 2.0 = 1.4\text{ V} - 2.0\text{ V} = -0.6\text{ V}$$

The output voltage of the op amp circuit is -0.6 V.

5.

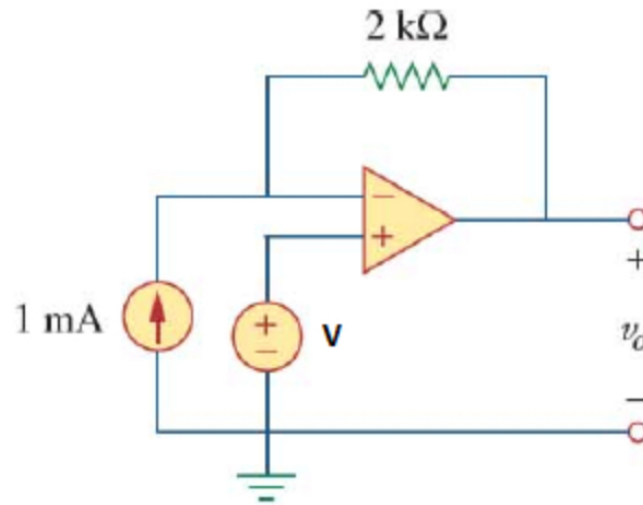value:
10.00 pointsFind the output voltage v_o for the op amp circuit given below, where $V = 12$ V.The output voltage v_o for the given op amp circuit is V.**Explanation:**Let v_a and v_b be respectively the voltages at the inverting and the noninverting terminals of the op amp.

$$v_a = v_b = 12 \text{ V}$$

At the inverting terminal,

$$1 \text{ mA} = \frac{12 \text{ V} - v_o}{2 \text{ k}\Omega}$$


$$v_o = 10 \text{ V}$$

The output voltage v_o for the given op amp circuit is 10 V.

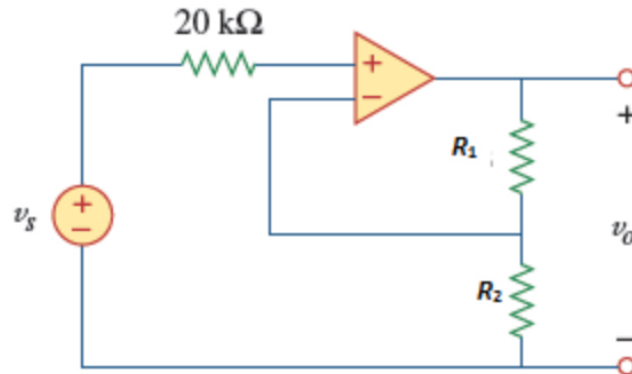6.

value:
10.00 points

Find the voltage gain v_0/v_s of the circuit given below, where $R_1 = 19 \text{ k}\Omega$ and $R_2 = 19 \text{ k}\Omega$.



The voltage gain v_0/v_s of the circuit is .

Explanation:

Since no current enters the op amp, the voltage at the input of the op amp is v_s .

Hence,

$$v_s = v_o \left(\frac{19 \text{ k}\Omega}{19 \text{ k}\Omega + 19 \text{ k}\Omega} \right)$$


$$\frac{v_o}{v_s} = 2.00$$

The gain v_0/v_s of the circuit is 2.00.

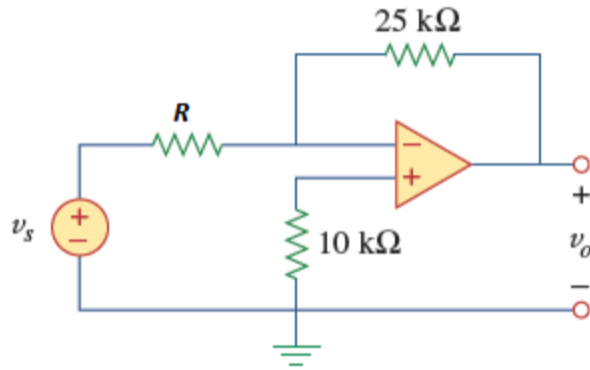7.

value:
10.00 points


Calculate the voltage ratio v_o/v_s for the op amp circuit given below, where $R = 6 \text{ k}\Omega$. Assume that the op amp is ideal.



The voltage ratio v_o/v_s for the op amp circuit is .

Explanation:

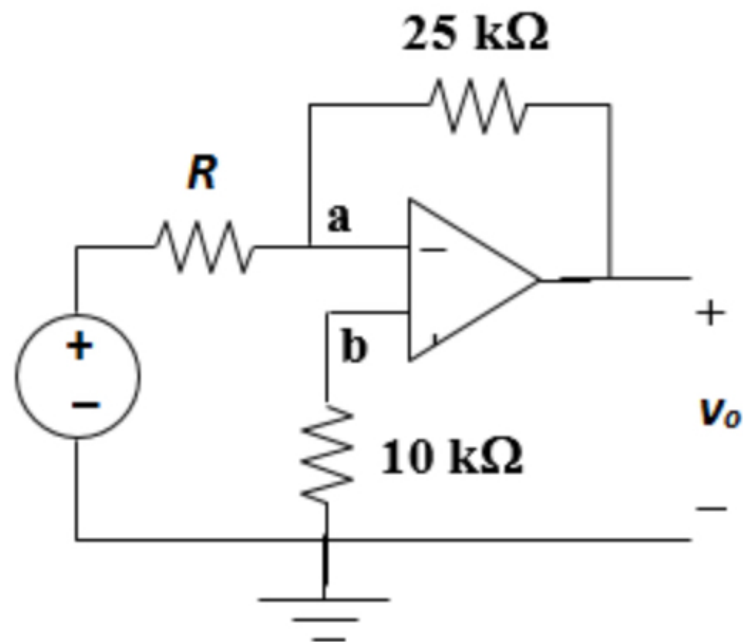Step 1: Label the unknown nodes in the op amp circuit. Next we write the node equations and then apply the constraint $v_a = v_b$. Finally, solve for v_o in terms of v_s .



Step 2:

$$\frac{v_a - v_s}{6\text{ k}\Omega} + \frac{v_a - v_o}{25\text{ k}\Omega} + 0 = 0 \quad \text{and} \quad \frac{v_b - 0}{10\text{ k}\Omega} + 0 = 0 \quad \text{or} \quad v_b = 0 = v_a$$

Thus,

$$\frac{-v_s}{6\text{ k}\Omega} + \frac{-v_o}{25\text{ k}\Omega} = 0$$

or



$$v_o = \frac{-25\text{ k}\Omega}{6\text{ k}\Omega} v_s$$

or

$$v_o/v_s = -4.17$$

The voltage ratio v_o/v_s is -4.17.

8.

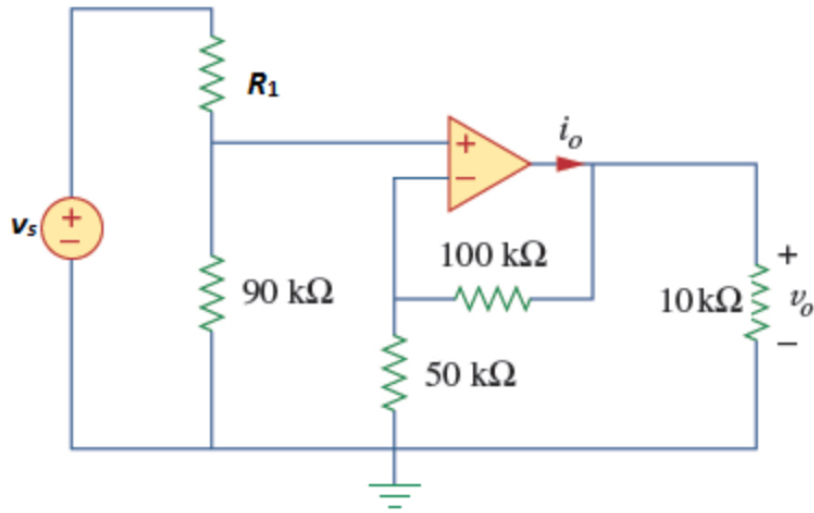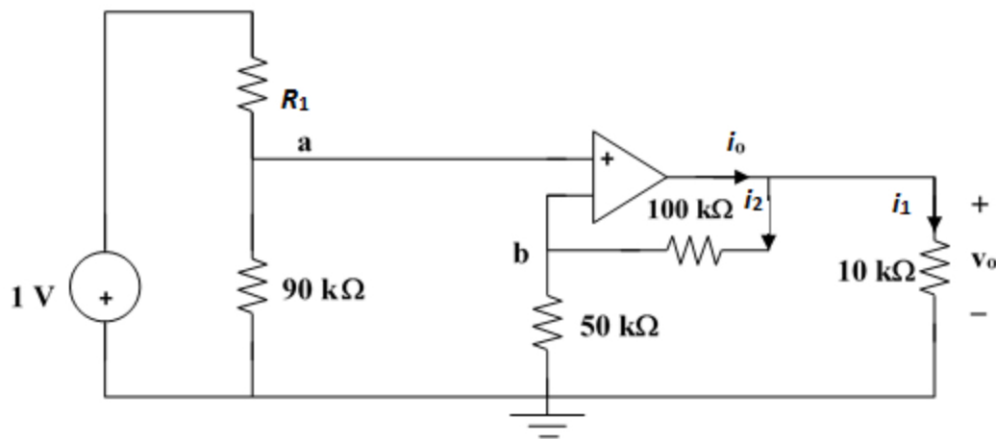value:
10.00 pointsConsider the op amp circuit given below, where $R_1 = 12 \text{ k}\Omega$ and $v_s = 1 \text{ V}$.Calculate the output voltage v_o for the given circuit.The output voltage v_o is V.**Explanation:**

By voltage division,

$$v_a = \frac{90 \text{ k}\Omega}{90 \text{ k}\Omega + 12 \text{ k}\Omega} \times 1 \text{ V} = 0.88 \text{ V}$$

$$v_b = \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 100 \text{ k}\Omega} = \frac{v_o}{3}$$

$$\text{But } v_a = v_b \rightarrow \frac{v_o}{3} = 0.88 \text{ V}$$


$$v_o = 2.65 \text{ V}$$

The output voltage v_o is 2.65 V.

9.

value:
10.00 points

Consider the circuit below.

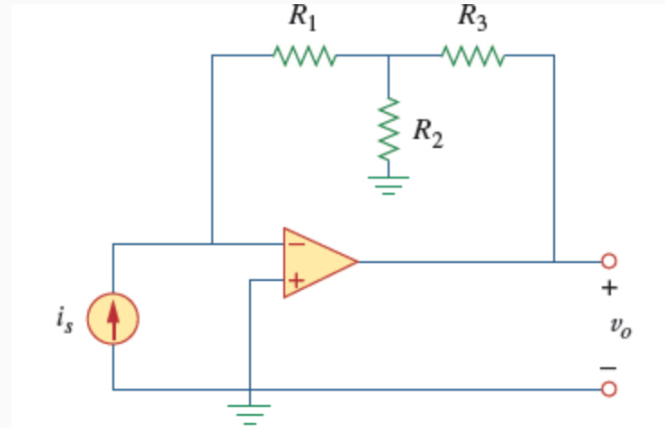Identify the ratio $\frac{v_o}{i_s}$ in the given op amp circuit.

- $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + R_2 + \frac{R_1}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + \frac{R_3}{R_1}\right)$
- $\frac{v_o}{i_s} = -\left(R_2 + R_3 + \frac{R_2 R_3}{R_1}\right)$

Explanation:Let v_1 be the voltage at the node where the three resistors meet. Applying KCL at this node gives

$$i_s = \frac{v_1}{R_2} + \frac{v_1 - v_o}{R_3} = v_1 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{v_o}{R_3} \text{ -----(1)}$$

At the inverting terminal,

$$i_s = \frac{0 - v_1}{R_1}$$

$$v_1 = -i_s R_1 \text{ -----(2)}$$

Combining (1) and (2) leads to

$$i_s \left(1 + \frac{R_1}{R_2} + \frac{R_1}{R_3} \right) = -\frac{v_o}{R_3}$$


$$\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$$

The ratio $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$.

10.

value:
10.00 points

Consider the circuit below.

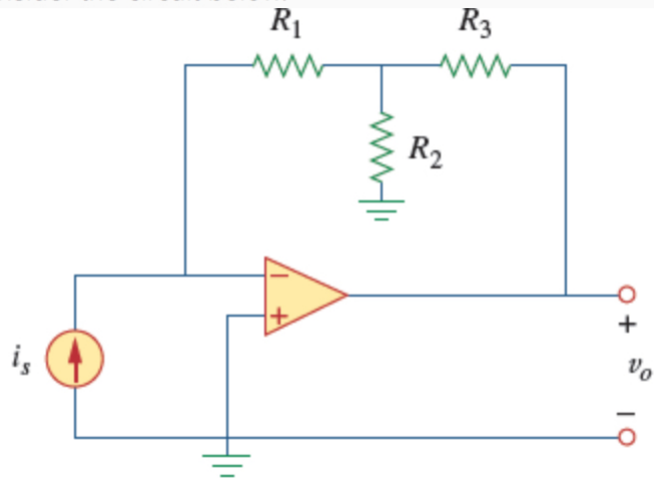

Find the value of the ratio $\frac{v_o}{i_s}$ for $R_1 = 18 \text{ k}\Omega$, $R_2 = 26 \text{ k}\Omega$, and $R_3 = 34 \text{ k}\Omega$.

The value of the ratio $\frac{v_o}{i_s} = \boxed{-75.54 \pm 2\%} \text{ k}\Omega$.

Explanation:

The ratio is calculated as follows:


$$\frac{v_o}{i_s} = - \left((18 \text{ k}\Omega + 34 \text{ k}\Omega) + \left(\frac{18 \text{ k}\Omega \times 34 \text{ k}\Omega}{26 \text{ k}\Omega} \right) \right) = - 75.54 \text{ k}\Omega$$

The value of the ratio $\frac{v_o}{i_s} = - 75.54 \text{ k}\Omega$.

11.

value:
10.00 points

Consider the circuit below.

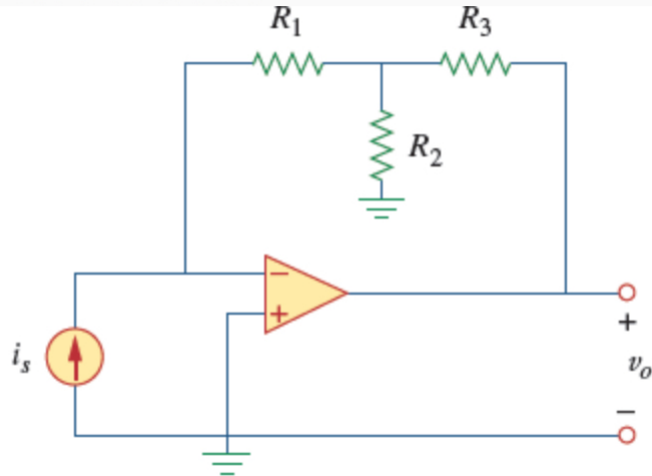Identify the ratio $\frac{v_o}{i_s}$ in the given op amp circuit.

→ $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2}\right)$

$\frac{v_o}{i_s} = -\left(R_1 + R_2 + \frac{R_1}{R_2}\right)$

$\frac{v_o}{i_s} = -\left(R_1 + \frac{R_3}{R_1}\right)$

$\frac{v_o}{i_s} = -\left(R_2 + R_3 + \frac{R_2 R_3}{R_1}\right)$

Explanation:Let v_1 be the voltage at the node where the three resistors meet. Applying KCL at this node gives

$$i_s = \frac{v_1}{R_2} + \frac{v_1 - v_o}{R_3} = v_1 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{v_o}{R_3} \quad \text{-----(1)}$$

At the inverting terminal,

$$i_s = \frac{0 - v_1}{R_1}$$

$$v_1 = -i_s R_1 \quad \text{-----(2)}$$

Combining (1) and (2) leads to

$$i_s \left(1 + \frac{R_1}{R_2} + \frac{R_1}{R_3} \right) = -\frac{v_o}{R_3}$$


$$\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$$

The ratio $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2} \right)$.

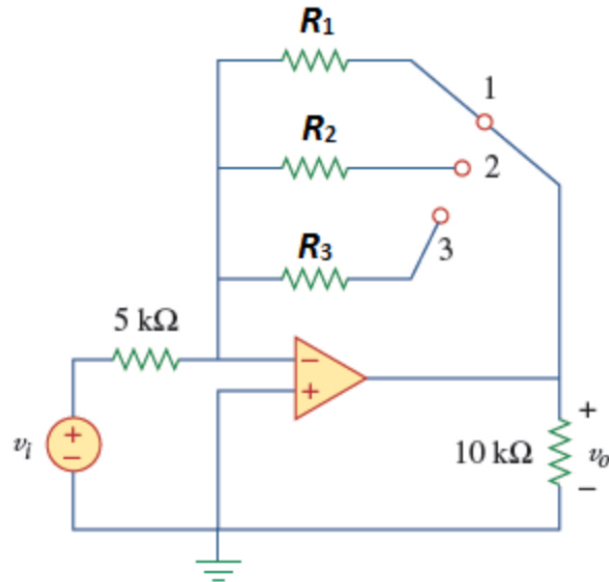12.

value:
10.00 points

In the circuit given below, $R_1 = 18 \text{ k}\Omega$, $R_2 = 80 \text{ k}\Omega$, and $R_3 = 2 \text{ M}\Omega$. Calculate the gain $\frac{v_o}{v_i}$ when the switch is in position 1, position 2, and position 3.



The gain $\frac{v_o}{v_i}$ at the position 1 is .

The gain $\frac{v_o}{v_i}$ at the position 2 is .

The gain $\frac{v_o}{v_i}$ at the position 3 is .

Explanation:

The gain is calculated as follows:

Position 1:

$$G = \frac{v_o}{v_i} = -\frac{R_f}{R_i} = -\frac{18 \text{ k}\Omega}{5 \text{ k}\Omega} = -3.6$$

Position 2:

$$G = \frac{v_o}{v_i} = -\frac{80 \text{ k}\Omega}{5 \text{ k}\Omega} = -16.0$$

Position 3:

$$G = \frac{v_o}{v_i} = -\frac{2 \text{ M}\Omega}{5 \text{ k}\Omega} = -400$$

The gain $\frac{v_o}{v_i}$ at the position 1 is - 3.6.

The gain $\frac{v_o}{v_i}$ at the position 2 is - 16.0.

The gain $\frac{v_o}{v_i}$ at the position 3 is - 400.