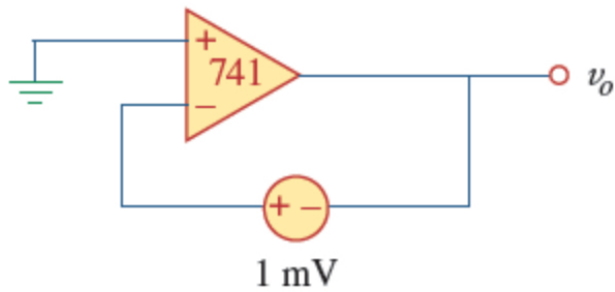


1.

value:
10.00 points

A 741 op amp shown in the circuit given below has an open-loop voltage gain of 80000, an input resistance of $2\text{ M}\Omega$, and an output resistance of $140\ \Omega$. Calculate the output voltage v_o in the op amp circuit.




The output voltage of the op amp is mV.

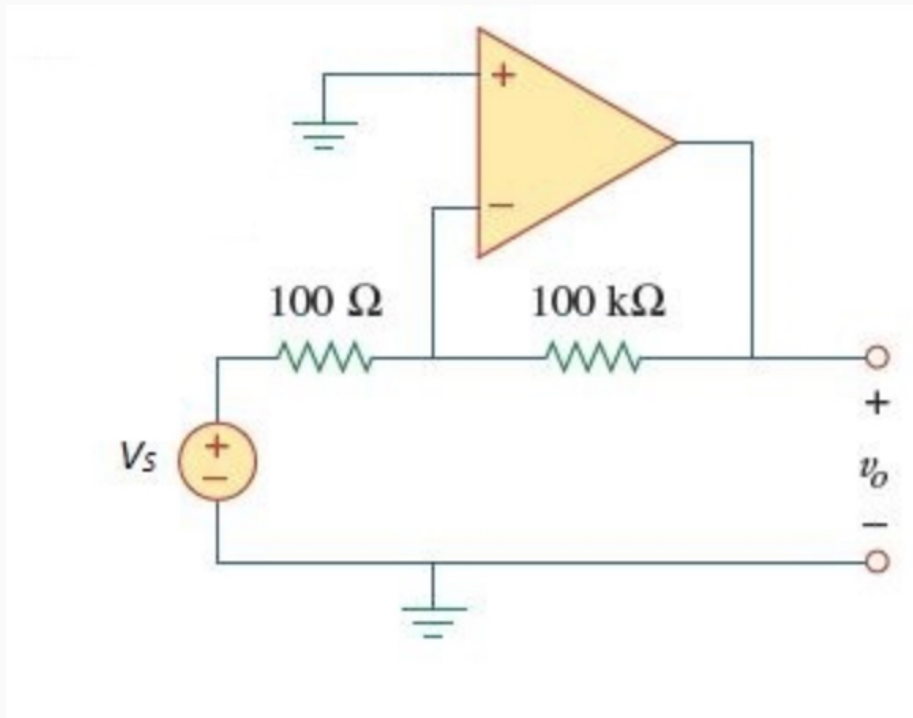2.

value:
10.00 points

The op amp in the circuit given below has $R_i = 100 \text{ k}\Omega$, $R_o = 100 \text{ }\Omega$, $v_S = 2 \text{ mV}$, and $A = 100,000$.




Calculate the output voltage v_o for the given op amp circuit.

The output voltage v_o for the given op amp circuit is mV.

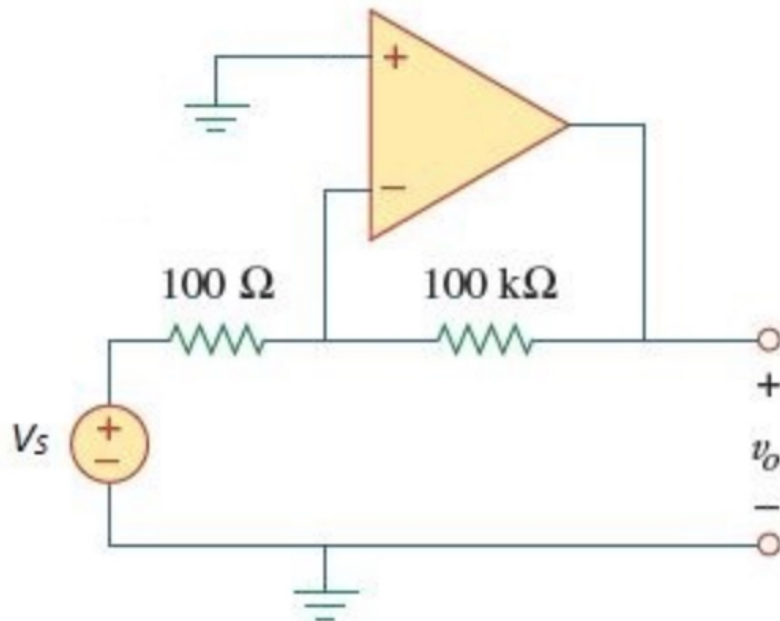3.

value:
10.00 points

The op amp in the circuit given below has $R_i = 100 \text{ k}\Omega$, $R_o = 100 \Omega$, $v_S = 2 \text{ mV}$, and $A = 100,000$.




Calculate the differential voltage v_d . (v_d = voltage between +ve and -ve input)

The differential voltage v_d is nV.

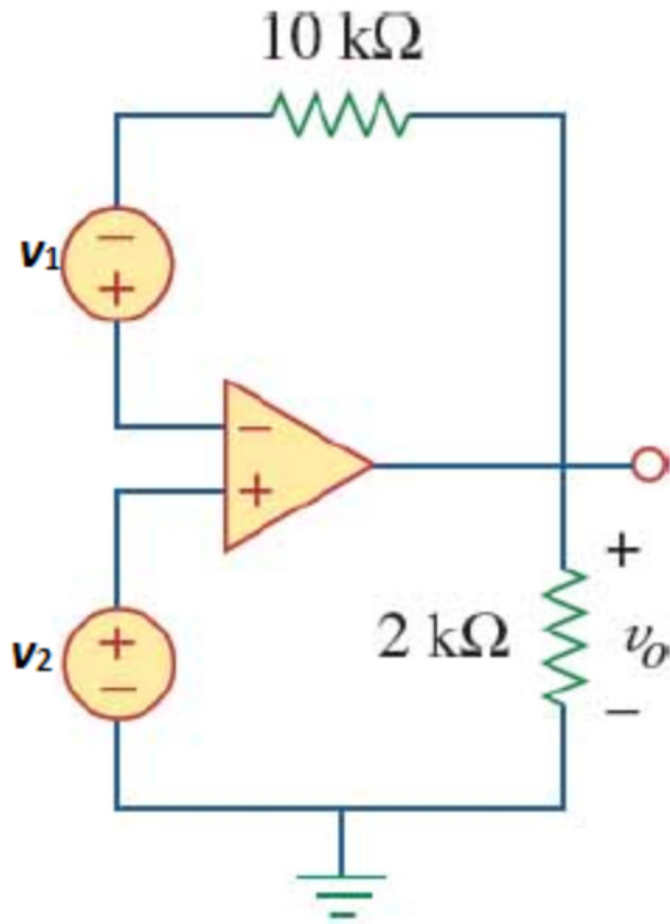4.

value:
10.00 points

Calculate the output voltage of the op amp circuit given below, where $v_1 = 2.6$ V and $v_2 = 1.3$ V.




The output voltage of the op amp circuit is V.

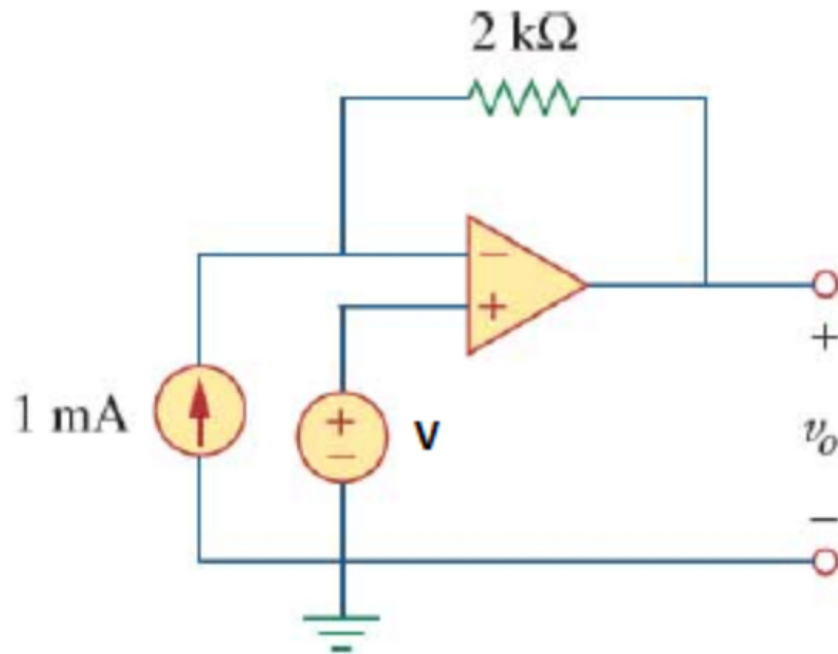5.

value:
10.00 points

Find the output voltage v_o for the op amp circuit given below, where $V = 4$ V.




The output voltage v_o for the given op amp circuit is V.

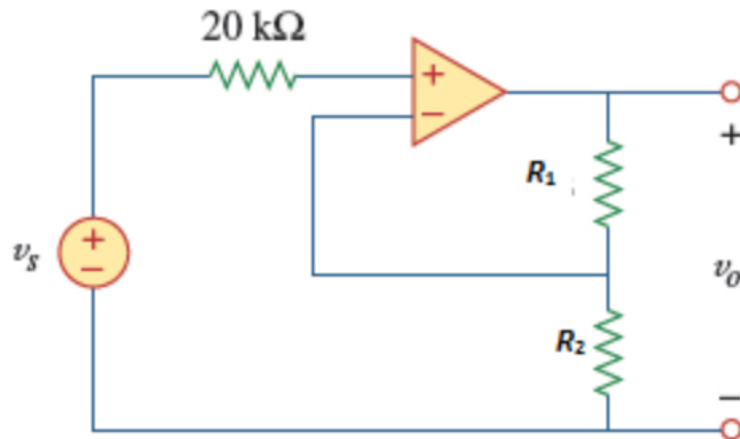6.

value:
10.00 points

Find the voltage gain v_0/v_s of the circuit given below, where $R_1 = 10 \text{ k}\Omega$ and $R_2 = 14 \text{ k}\Omega$.




The voltage gain v_0/v_s of the circuit is .

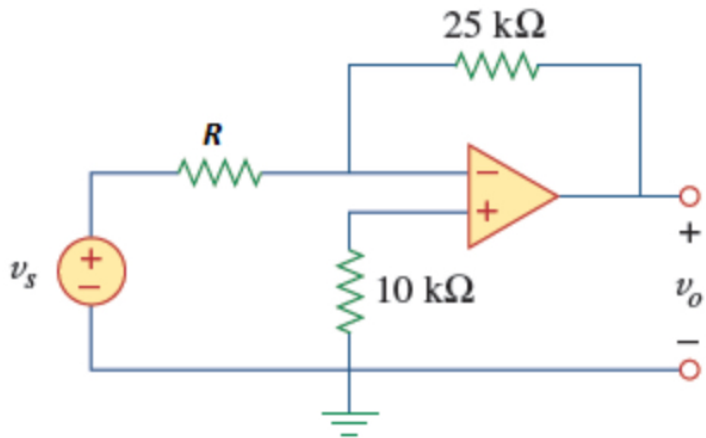7.

value:
10.00 points

Calculate the voltage ratio v_0/v_s for the op amp circuit given below, where $R = 12 \text{ k}\Omega$. Assume that the op amp is ideal.




The voltage ratio v_0/v_s for the op amp circuit is .

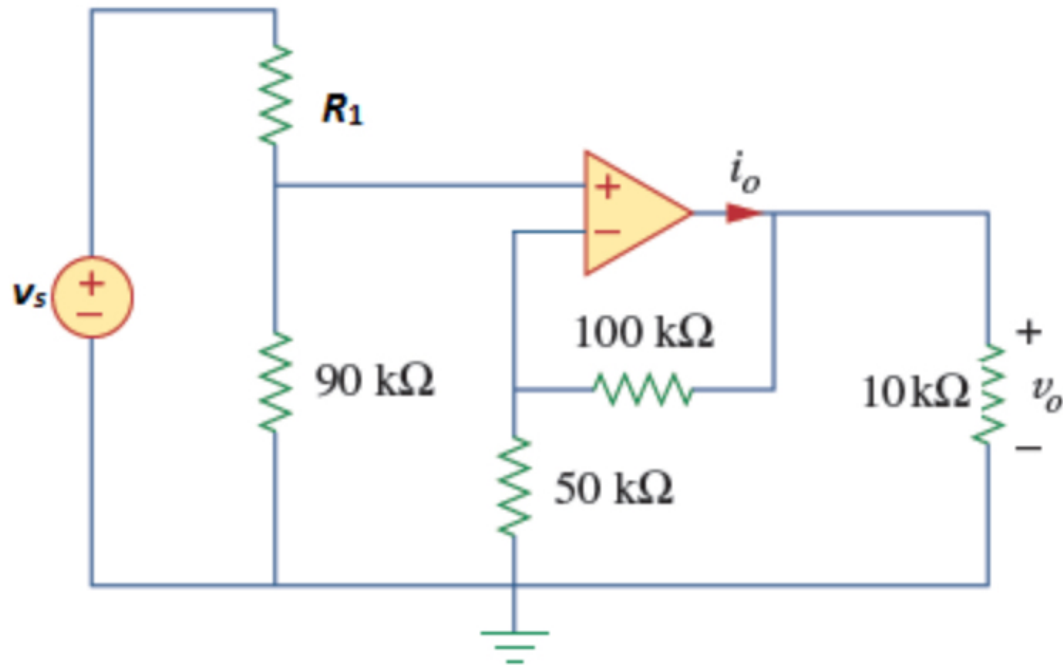8.

value:
10.00 points

Consider the op amp circuit given below, where $R_1 = 17 \text{ k}\Omega$ and $v_s = 1 \text{ V}$.




Calculate the output voltage v_o for the given circuit.

The output voltage v_o is V.

9.

value:
10.00 points

Consider the circuit below.

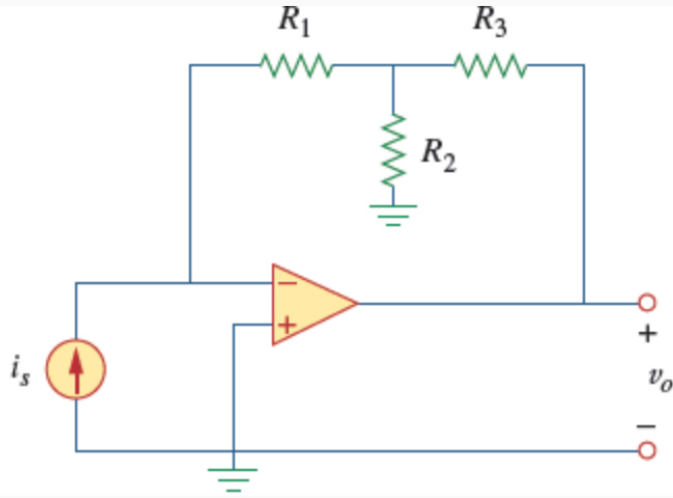
Identify the ratio $\frac{v_o}{i_s}$ in the given op amp circuit.

- $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + \frac{R_3}{R_1}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + R_2 + \frac{R_1}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_2 + R_3 + \frac{R_2 R_3}{R_1}\right)$

10.

value:
10.00 points

Consider the circuit below.

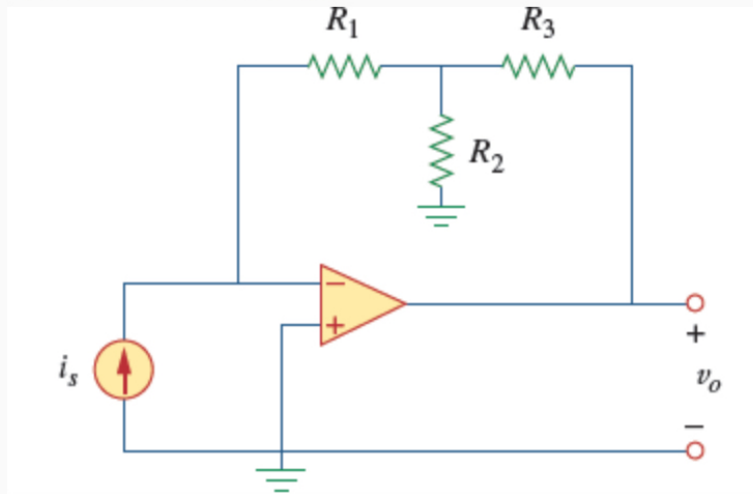


Find the value of the ratio $\frac{v_o}{i_s}$ for $R_1 = 17 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, and $R_3 = 36 \text{ k}\Omega$.

The value of the ratio $\frac{v_o}{i_s} =$ $\text{k}\Omega$.

11.

value:
10.00 points

Consider the circuit below.

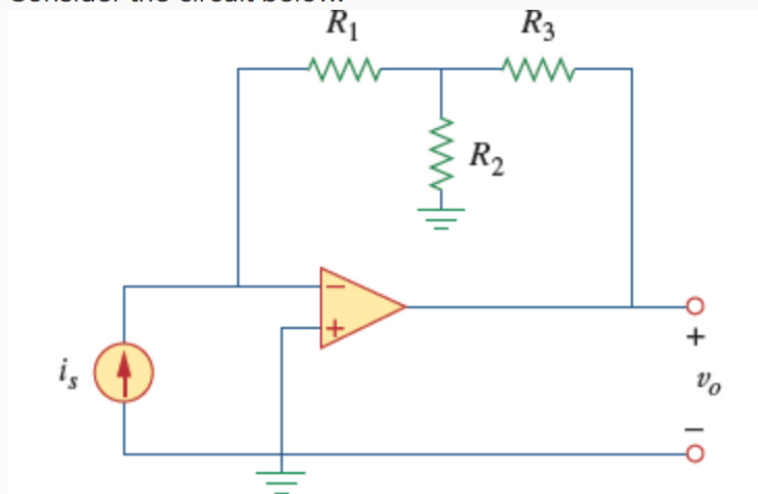
Identify the ratio $\frac{v_o}{i_s}$ in the given op amp circuit.

- $\frac{v_o}{i_s} = -\left(R_1 + R_2 + \frac{R_1}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + R_3 + \frac{R_1 R_3}{R_2}\right)$
- $\frac{v_o}{i_s} = -\left(R_1 + \frac{R_3}{R_1}\right)$
- $\frac{v_o}{i_s} = -\left(R_2 + R_3 + \frac{R_2 R_3}{R_1}\right)$

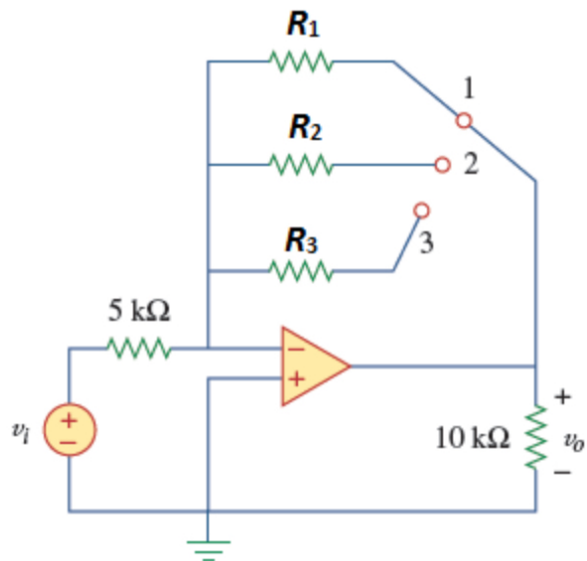12.

value:
10.00 points

In the circuit given below, $R_1 = 20 \text{ k}\Omega$, $R_2 = 76 \text{ k}\Omega$, and $R_3 = 12 \text{ M}\Omega$. Calculate the gain $\frac{v_0}{v_i}$ when the switch is in position 1, position 2, and position 3.



The gain $\frac{v_0}{v_i}$ at the position 1 is .

The gain $\frac{v_0}{v_i}$ at the position 2 is .

The gain $\frac{v_0}{v_i}$ at the position 3 is .