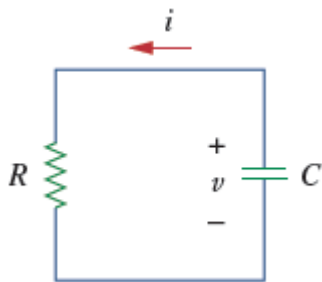


In the given circuit,
 $v(t) = 56 e^{-280t} \text{ V}, t > 0$

$i(t) = 7 e^{-280t} \text{ mA}, t > 0$



References

Section Break

Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.

1.

Award: 10.00 points

Calculate the time constant τ .

The time constant τ is ms.

Explanation:

The time constant is given by $\tau = RC = \frac{1}{280} = 3.57$ ms

The time constant τ is 3.57 ms.

Hints[Hint #1](#)**References****Worksheet**


Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.

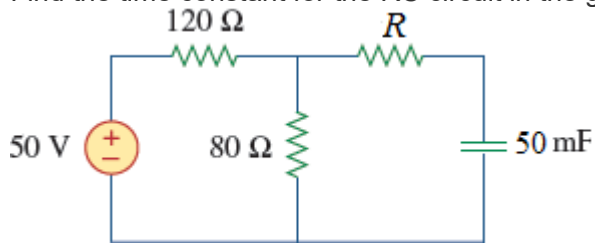2.

Award: 10.00 points

Find the time constant for the RC circuit in the given figure. Assume $R = 12 \Omega$.



The time constant for the RC circuit in the given figure is s.

Explanation:

The time constant is given by $\tau = R_{th}C$, where R_{th} is the Thévenin equivalent at the capacitor terminals.

The value of R_{th} can be determined as follows:

$$R_{th} = 120 \Omega \parallel 80 \Omega + 12 \Omega = \left(\frac{120 \Omega \times 80 \Omega}{120 \Omega + 80 \Omega} \right) + 12 \Omega = 60.00 \Omega$$

$$\text{Therefore, } \tau = 60.00 \Omega \times 0.05 \text{ F} = 3.00 \text{ s}$$

The time constant for the RC circuit in the given figure is 3.00 s.

Hints[Hint #1](#)**References****Worksheet**


Difficulty: Easy

Learning Objective: Understand solutions to unforced, first order linear differential equations.

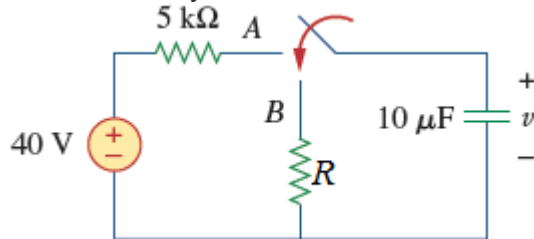3.

Award: 10.00 points

The switch in the given figure has been in position A for a long time. Assume the switch moves instantaneously from A to B at $t = 0$. Find v for $t > 0$. Assume $R = 2 \text{ k}\Omega$.



The voltage $v(t) = v(0) e^{-t/\tau}$, where $v(0) =$ V and $\tau =$ s.

Explanation:

For $t < 0$, $v(0) = 40 \text{ V}$

For $t > 0$, we have a source-free RC circuit.

$$\tau = RC = 2 \text{ k}\Omega \times 10 \text{ }\mu\text{F} = 0.02 \text{ s}$$

$$v(t) = v(0) e^{-t/\tau} = 40 e^{-50.0t} \text{ V}$$

The voltage $v(t) = v(0) e^{-t/\tau}$, where $v(0) = 40.0 \text{ V}$ and $\tau = 0.02 \text{ s}$.

Hints[Hint #1](#)**References****Worksheet**


Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

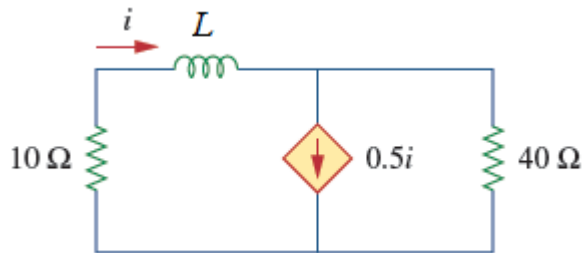4.

Award: 10.00 points



In the given circuit, find the unknown quantities of $i(t)$ for $t > 0$ if $i(0) = 5$ A. Assume $L = 8$ H.



The current $i(t) = 5 e^{-t/\tau}$ A, where $\tau =$ s.

Explanation:

The given circuit is as shown below:

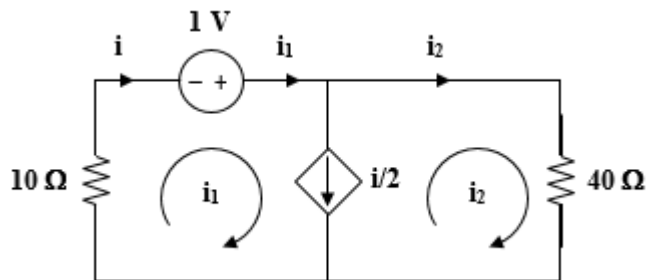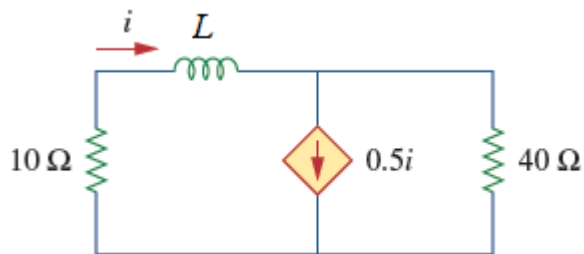

To find R_{TH} , we replace the inductor by a 1-V voltage source as shown above.

$$10i_1 - 1 + 40i_2 = 0$$

$$\text{But } i = i_2 + \frac{1}{2} \text{ and } i = i_1$$

$$\text{i.e., } i_1 = 2i_2 = i$$

$$10i - 1 + 20i = 0 \rightarrow i = \frac{1}{30} \text{ A}$$

The Thévenin resistance is given as

$$R_{TH} = \frac{1}{i} = 30 \Omega$$

The time constant is given by

$$\tau = \frac{L}{R_{TH}} = \frac{8 \text{ H}}{30 \Omega} = 0.27 \text{ s}$$

Therefore, the current $i(t) = 5 e^{-t/0.27} \text{ A}$

The current $i(t) = 5 e^{-t/\tau} \text{ A}$, where $\tau = 0.27 \text{ s}$.

Hints

[Hint #1](#)

References

Worksheet


Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

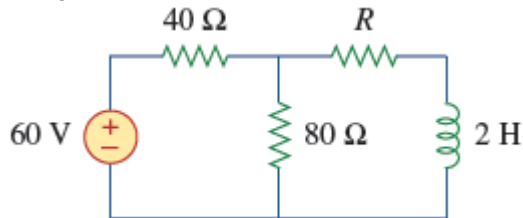5.

Award: 10.00 points


In the given circuit, find the value of R for which the steady-state energy stored in the inductor will be 1.1 J.



The value of R is Ω.

Explanation:

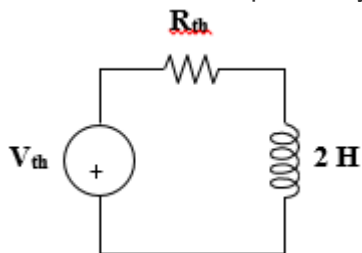The circuit can be replaced by its Thévenin equivalent shown below.



$$V_{TH} = \frac{80 \Omega}{80 \Omega + 40 \Omega} (60 \text{ V}) = 40 \text{ V}$$

$$R_{TH} = 40 \Omega \parallel 80 \Omega + R = \frac{80 \Omega}{3} + R$$

$$I = i(0) = i(\infty) = \frac{V_{TH}}{R_{TH}} = \frac{40 \text{ V}}{\frac{80 \Omega}{3} + R}$$

The value of R can be calculated as follows:

$$w = \frac{1}{2} LI^2 = \left(0.5\right) \times \left(2\right) \times \left(\frac{40 \text{ V}}{\frac{80 \Omega}{3} + R}\right)^2 = 1.10 \text{ J}$$

$$\rightarrow \frac{40 \text{ V}}{R + \frac{80 \Omega}{3}} = 1.05$$

$$\rightarrow R + \frac{80 \Omega}{3} = 38.14$$

$$\rightarrow R = 38.14 - \frac{80 \Omega}{3}$$

$$\rightarrow R = 11.472 \Omega$$

The value of R is 11.472 Ω.

[Hints](#)

[Hint #1](#)

[Hint #2](#)

[Hint #3](#)

References


Worksheet

Difficulty: Medium

Learning Objective: Understand solutions to unforced, first order linear differential equations.

6.

Award: 10.00 points

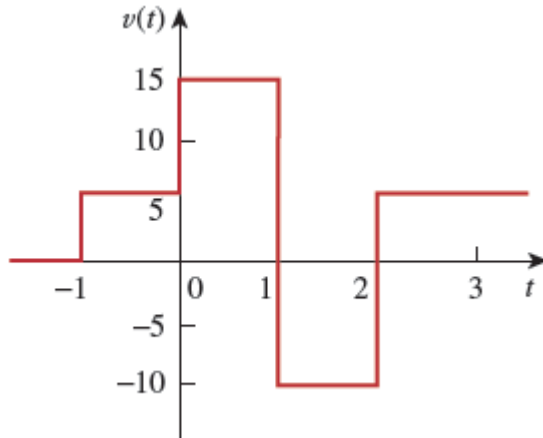Express $v(t)$ in the given figure in terms of step functions.

- $v(t) = (5u(t+1) + 10(t-1) - 25u(t) + 15u(t-2))$ V
 $v(t) = (5u(t-1) + 10u(t) - 25u(t+2) + 15u(t+2))$ V
 $v(t) = (5u(t+1) + 10u(t) - 25u(t-1) + 15u(t-2))$ V
 $v(t) = (5u(t-2) + 10u(t-1) - 25u(t) + 15u(t+1))$ V

Hints

[Hint #1](#)

References

Multiple Choice Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

7.

Award: 10.00 points

The voltage across a 10-mH inductor is $42\delta(t-2)$ mV. Find the inductor current, assuming that the inductor is initially uncharged.

The inductor current is $i(t) =$ $u(t-2)$ A.

Explanation:

The inductor current can be determined as follows:

$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0)$$

$$i(t) = \frac{10^{-3}}{10 \times 10^{-3}} \int_0^t 42\delta(\tau-2) d\tau + 0 = 4.2u(t-2) \text{ A}$$

It should be noted that the integration of the impulse function $\delta(t-t_0)$ produces the unit step $u(t-t_0)$. Whatever the multiplier, $f(t)$ of the impulse function at $t = t_0$ ends up multiplying the unit step by the same amount $f(t_0)$. In this case $f(2) = 4.2$.

$$i(t) = 4.2 u(t-2) \text{ A}$$

The inductor current is $4.2 u(t-2)$ A.

Hints[Hint #1](#)**References****Worksheet**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

8.

Award: 10.00 points

Find the solution of the differential equation $\frac{dv}{dt} + 6v = 0$, $v(0) = -1$ V.

The solution of the given differential equation is $-(e^{-\boxed{6 \pm 2\%} t})$ V.

Explanation:

The given differential equation can be solved as follows:

$$v = A e^{-6t}, \quad v(0) = A = -1$$

Therefore, $v(t) = -e^{-6t}$ V.

The solution of the given differential equation is $-e^{-6t}$ V.

Hints[Hint #1](#)**References****Worksheet**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

9.

Award: 10.00 points

Identify the solution of the following differential equation, subject to the stated initial condition.

$$2\frac{dv}{dt} - v = 3u(t), \quad v(0) = -6$$

- $v(t) = -3(1 + e^{t/2})V, \quad t < 0$
- $v(t) = -3(1 + e^{t/2})u(t)V, \quad t > 0$
- $v(t) = 3(1 - e^{t/2})u(t)V, \quad t > 0$
- $v(t) = 3(1 - e^{t/2})V, \quad t < 0$

The given differential equation can be solved as below:

$$v(t) = A + B e^{t/2}, \quad t > 0$$

$$A = -3,$$

$$v(0) = -6 = -3 + B \rightarrow B = -3$$

$$v(t) = -3(1 + e^{t/2})u(t)V, \quad t > 0$$

The solution for the given differential equation is $v(t) = -3(1 + e^{t/2})u(t)V, \quad t > 0$.

Hints

[Hint #1](#)

[Hint #2](#)

References

Multiple Choice

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

A circuit is described by

$$2 \frac{dv}{dt} + v = 10.$$

References

Section Break

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.

10.

Award: 10.00 points

If $v(0) = 3$, find $v(t)$ for $t \geq 0$.

The voltage $v(t) = \boxed{10 \pm 2\%} + (\boxed{-7 \pm 2\%}) (e^{-\boxed{0.50 \pm 2\%} t}) \times u(t)$ V.

Explanation:

Let $v = v_h + v_p$ and $v_p = 10$.

$$\dot{v}_h + \frac{1}{2}v_h = 0 \rightarrow v_h = A e^{-t/2}$$

$$v = 10 + A e^{-0.50t}$$

$$v(0) = 3 = 10 + A \rightarrow A = -7$$

$$v = 10 + (-7) e^{-0.50t} \text{ V}$$

The voltage $v(t) = 10 + (-7) (e^{-0.50 t}) u(t)$ V.

Hints[Hint #1](#)[Hint #2](#)**References****Worksheet**

Difficulty: Medium

Learning Objective: Understand singularity equations and their importance in solving linear differential equations.