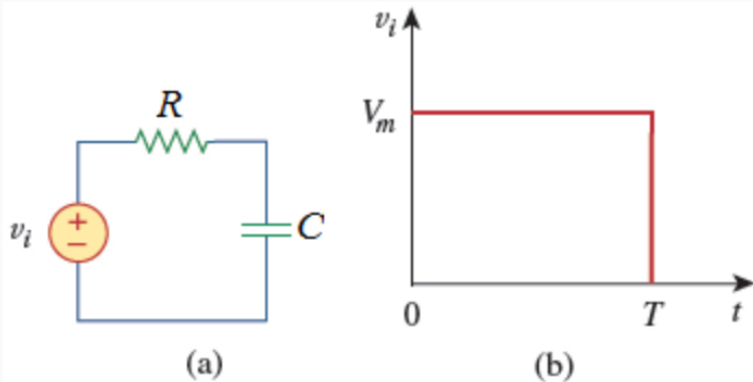


1.

value:
10.00 points

The circuit in figure (a) can be designed as an approximate differentiator or an integrator, depending on whether the output is taken across the resistor or the capacitor, and also on the time constant $\tau = RC$ of the circuit and the width T of the input pulse in figure (b). The circuit is a differentiator if $\tau \ll T$, say $\tau < 0.1T$, or an integrator if $\tau \gg T$, say $\tau > 10T$. Assume $R = 500 \text{ k}\Omega$ and $C = 400 \text{ pF}$.



What is the minimum pulse width that will allow a differentiator output to appear across the capacitor?

The minimum pulse width that will allow a differentiator output to appear across the capacitor is ms.

2.

value:
10.00 points


An RL circuit may be used as a differentiator if the output is taken across the inductor and $\tau \ll T$ (say $\tau < 0.1 T$), where T is the width of the input pulse. If R is fixed at $320 \text{ k}\Omega$, determine the maximum value of L required to differentiate a pulse with $T = 10 \mu\text{s}$.

The maximum value of L required to differentiate a pulse with $T = 10 \mu\text{s}$ is < mH.

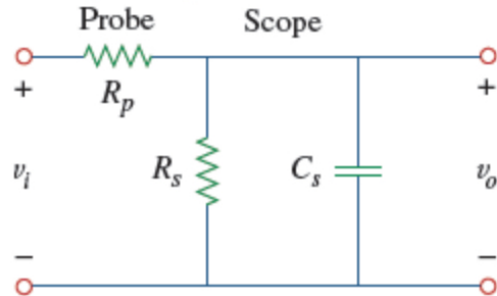3.

value:
10.00 points

An attenuator probe employed with oscilloscopes was designed to reduce the magnitude of the input voltage v_i by a factor of 10. As shown in the given figure, the oscilloscope has internal resistance R_s and capacitance C_s , while the probe has an internal resistance R_p . If R_p is fixed at $6\text{ M}\Omega$, find R_s and C_s for the circuit to have a time constant of $24\text{ }\mu\text{s}$.




The value of R_s is $\text{M}\Omega$.

The value of C_s is pF .

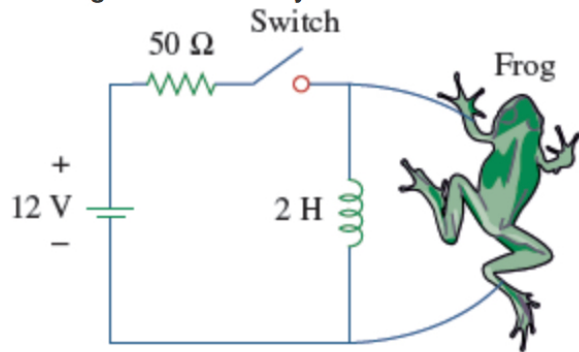4.

value:
10.00 points

The circuit in the given figure is used by a biology student to study “frog kick.” She noticed that the frog kicked a little when the switch was closed but kicked violently for 9 s when the switch was opened. Model the frog as a resistor and calculate its resistance. Assume that it takes 10 mA for the frog to kick violently.




The resistor value is Ω.

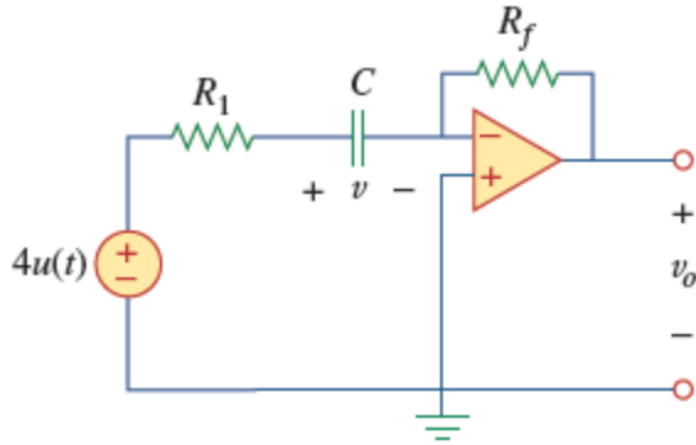5.

value:
10.00 points

For the op amp circuit of the given figure, let $R_1 = 10 \text{ k}\Omega$, $R_f = 30 \text{ k}\Omega$, $C = 40 \mu\text{F}$, and $v(0) = 1 \text{ V}$. Find v_o .



The voltage v_o is $((\text{[]})e^{-t/[\text{]}})u(t) \text{ V}$.

6.

value:
10.00 points

In the given circuit, i_s changes from 6 A to 10 A at $t = 0$, that is, $i_s = [6u(-t) + 10u(t)]$ A. Find $v(t)$ and $i(t)$.




The current $i(t) = (\text{ } + (\text{ }) e^{- \text{ } t }) u(t)$ A.

The voltage $v(t) = (\text{ }) e^{- \text{ } t } u(t)$ V.

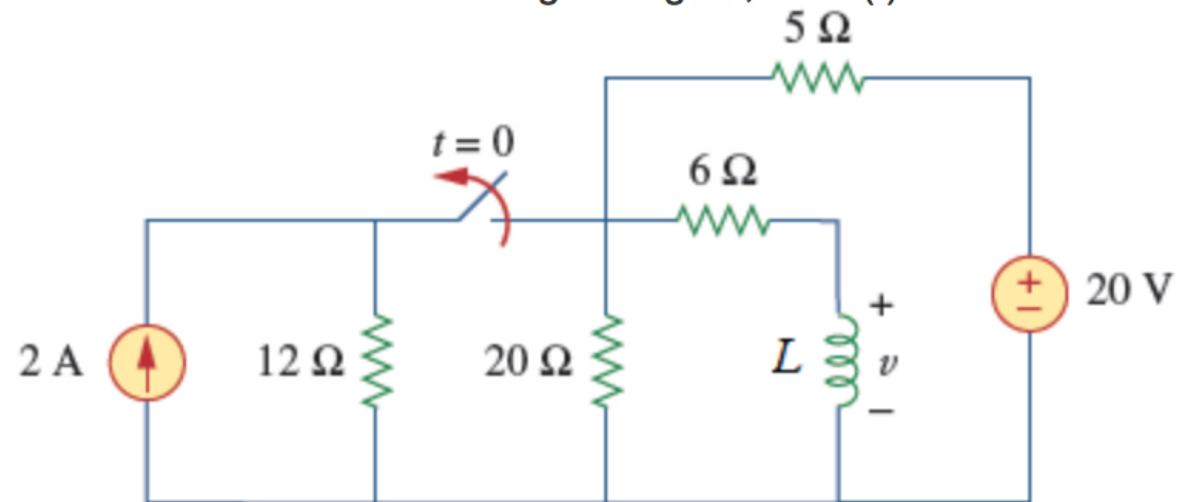7.

value:
10.00 points

For the network shown in the given figure, find $v(t)$ for $t > 0$. Assume $L = 1.3$ H.



The voltage $v(t) = \boxed{} e^{-t/\boxed{}} \text{ V for } t > 0.$

8.

value:
10.00 points

An RC circuit consists of a series connection of a 160-V source, a switch, a 34-M Ω resistor, and a 15- μ F capacitor. The circuit is used in estimating the speed of a horse running a 6-km racetrack. The switch closes when the horse begins and opens when the horse crosses the finish line. Assuming that the capacitor charges to 85.6 V, calculate the speed of the horse.

The speed of the horse is m/s.

9.

value:
10.00 points

A capacitor with a value of 70 mF has a leakage resistance of 2 M Ω . How long does it take the voltage across the capacitor to decay to 40% of the initial voltage to which the capacitor is charged? Assume that the capacitor is charged and then set aside by itself.

The voltage across the capacitor takes hours to decay to 40% of the initial voltage.