

1. Second-Order Circuit: RLC Circuit Analysis

1. Be able to find Initial and Final Values for RLC Circuits.
 - a. $v(0^-) = v(0^+) = v(0)$
 - b. $i(0^-) = i(0^+) = i(0)$
 - c. For a Series RLC Circuit with 1 Resistor, 1 Inductor, and 1 Capacitor.
 - i. $L \frac{di(0)}{dt} + Ri(0) + v(0) = 0$
 - ii. $\frac{di(0)}{dt} = \frac{1}{L} [-Ri(0) - v(0)] = -\frac{R}{L} \left[i(0) + \frac{v(0)}{R} \right] = -\frac{1}{\tau_L} \left[i(0) + \frac{v(0)}{R} \right]$
 - d. For a Parallel RLC Circuit with 1 Resistor, 1 Inductor, and 1 Capacitor.
 - i. $C \frac{dv(0)}{dt} + \frac{v(0)}{R} + i(0) = 0$
 - ii. $\frac{dv(0)}{dt} = \frac{1}{C} \left[-\frac{v(0)}{R} - i(0) \right] = -\frac{1}{RC} [v(0) + Ri(0)] = -\frac{1}{\tau_C} [v(0) + Ri(0)]$
2. Be able to derive α and ω_0 for a Source Free Series RLC Circuit.
 - a. Resistor, Inductor, and Capacitor have the -same Current.
 - b. Use KVL to write a Differential Equation for the Circuit in terms of Current.
 - i. $L \frac{d}{dt} i(t) + Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0$
 - c. Take the Time Derivative to create a Second-order Differential Equation.
 - i. $L \frac{d^2}{dt^2} i(t) + R \frac{d}{dt} i(t) + \frac{1}{C} i(t) = 0$
 - d. Simplify so that the coefficient on the highest order term is "1".
 - i. Divide the entire equation by L .
 - ii. $\frac{d^2}{dt^2} i(t) + \frac{R}{L} \frac{d}{dt} i(t) + \frac{1}{LC} i(t) = 0$
 - e. Write out the Characteristic Equation for our Differential Equation.
 - i. $x(t) \rightarrow s^0 = 1$
 - ii. $x'(t) = \frac{d}{dt} x(t) \rightarrow s^1$
 - iii. $x''(t) = \frac{d^2}{dt^2} x(t) \rightarrow s^2$
 - iv. $x^n(t) = \frac{d^n}{dt^n} x(t) \rightarrow s^n$ where $n \in \mathbb{Z}^+$.
 - v. Using the relationship between an arbitrary function $x(t)$ and s , we can write out the Characteristic Equation for our Differential Equation.
 1. $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$
 - f. Use the Quadratic Formula to solve for the Roots of the Characteristic Equation.
 - i. If $f(x) = ax^2 + bx + c$ and we want the values for x which $f(x) = 0$...
 1. Then $x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$
 - ii. Applying the Quadratic Formula.
 1. $s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$
 - iii. After simplifying the Quadratic Formula, we arrive at this conclusion.
 1. $s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$
 - g. The Roots of our Characteristic Equation can be simplified further. This will be relating our values in the Quadratic Formula with a variable α and ω_0 .

- i. Let $\alpha = \frac{R}{2L}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$
 - ii. Using the following substitution, we arrive at the Roots of our Characteristic Equation in terms of α and ω_0 .
 1. $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
3. Be able to derive α and ω_0 for a Source Free Parallel RLC Circuit.
 - a. Resistor, Inductor, and Capacitor have the same Voltage.
 - b. Use KCL to write a Differential Equation for the Circuit in terms of Voltage.
 - i. $C \frac{d}{dt} v(t) + \frac{v(t)}{R} + \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau = 0$
 - c. Take the Time Derivative to create a Second-order Differential Equation.
 - i. $C \frac{d^2}{dt^2} v(t) + \frac{1}{R} \frac{d}{dt} v(t) + \frac{1}{L} v(t) = 0$
 - d. Simplify so that the coefficient on the highest order term is "1".
 - i. Divide the entire equation by C .
 - ii. $\frac{d^2}{dt^2} v(t) + \frac{1}{RC} \frac{d}{dt} v(t) + \frac{1}{LC} v(t) = 0$
 - e. Write out the Characteristic Equation for our Differential Equation.
 - i. Refer to (2.e.i-iv) to understand how to write out the Characteristic Equation for our Differential Equation.
 1. $s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$
 - f. Use the Quadratic Formula to solve for the Roots of the Characteristic Equation.
 - i. If $f(x) = ax^2 + bx + c$ and we want the values for x which $f(x) = 0$...
 1. Then $x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$
 - ii. Applying the Quadratic Formula.
 1. $s_{1,2} = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$
 - iii. After simplifying the Quadratic Formula, we arrive at this conclusion.
 1. $s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$
 - g. The Roots of our Characteristic Equation can be simplified further. This will be relating our values in the Quadratic Formula with a variable α and ω_0 .
 - i. Let $\alpha = \frac{1}{2RC}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$
 - ii. Using the following substitution, we arrive at the Roots of our Characteristic Equation in terms of α and ω_0 .
 1. $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
4. Be able to understand the characteristics of α and ω_0 for a Second-order Circuit.
 - a. The general roots for a Second-order Circuit is defined as follows.
 - i. $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
 - b. There is a relationship between α and ω_0 for a Second-order Circuit. Depending on the number of Roots (2, 1, or 0) in our Characteristic Equation, this affects the Voltage and Current equation for our Second-order Circuit. There are 3 responses a RLC Circuit.
 - c. Overdamped Response ($\alpha > \omega_0$)

- i. This means that our Characteristic Equation has 2 Real Roots.
 - 1. Think of a quadratic function that intersects the x -axis 2 times.
- ii. The Solution to our Second-order Differential Equation is the following.
 - 1. $x(t) = A_1e^{s_1t} + A_2e^{s_2t}$
- iii. $x(t)$ will be our Time Varying Current for a Series RLC Circuit.
- iv. $x(t)$ will be our Time Varying Voltage for a Parallel RLC Circuit.
- v. Even if we have the solution, that is not enough to solve for our desired function. We have A_1 and A_2 in our solution so we will need to solve for these unknown coefficients.
- vi. To solve for the coefficients, we will need a second equation to solve. In this case, we will take time derivative of our function $x(t)$.
 - 1. $x(t) = A_1e^{s_1t} + A_2e^{s_2t}$
 $x'(t) = s_1A_1e^{s_1t} + s_2A_2e^{s_2t}$
- vii. Now that we have 2 equations and 2 unknowns, we will use the initial conditions for our given RLC Circuit. We are working with a Second-order Circuit, so we need $x(0)$ and $x'(0)$ to solve for the coefficients. Refer to (1.a-d) to find the initial values for our given RLC Circuit.
 - 1. $x(0) = A_1e^{s_1(0)} + A_2e^{s_2(0)}$
 $x'(0) = s_1A_1e^{s_1(0)} + s_2A_2e^{s_2(0)}$
- viii. We can simplify the previous Equation and we can solve the following System of Equations for the coefficients A_1 and A_2 .
 - 1. $x(0) = A_1 + A_2$
 $x'(0) = s_1A_1 + s_2A_2$
- d. Critically Damped Response ($\alpha = \omega_0$)
 - i. This means that our Characteristic Equation has 1 Real Root.
 - 1. Think of a quadratic function that intersects the x -axis 1 time.
 - ii. The Solution to our Second-order Differential Equation is the following.
 - 1. $x(t) = A_1e^{-\alpha t} + A_2te^{-\alpha t}$
 - iii. $x(t)$ will be our Time Varying Current for a Series RLC Circuit.
 - iv. $x(t)$ will be our Time Varying Voltage for a Parallel RLC Circuit.
 - v. Even if we have the solution, that is not enough to solve for our desired function. We have A_1 and A_2 in our solution so we will need to solve for these unknown coefficients.
 - vi. To solve for the coefficients, we will need a second equation to solve. In this case, we will take time derivative of our function $x(t)$.
 - vii. This will be a little more difficult because we have 2 functions being multiplied with each other. We will use the Product Rule.
 - 1. If $x(t) = f(t)g(t)$, then $x'(t) = f(t)g'(t) + f'(t)g(t)$
 - viii. Using the Product Rule, we can take the time derivative of $x(t)$.
 - 1. $x(t) = A_1e^{-\alpha t} + A_2te^{-\alpha t}$
 $x'(t) = -\alpha A_1e^{-\alpha t} + A_2e^{-\alpha t} - \alpha A_2te^{-\alpha t}$
 - ix. Now that we have 2 equations and 2 unknowns, we will use the initial conditions for our given RLC Circuit. We are working with a Second-order Circuit, so we need $x(0)$ and $x'(0)$ to solve for the coefficients. Refer to (1.a-d) to find the initial values for our given RLC Circuit.

1. $x(0) = A_1 e^{-\alpha(0)} + A_2 t e^{-\alpha(0)}$
 $x'(0) = -\alpha A_1 e^{-\alpha(0)} + A_2 e^{-\alpha(0)} - \alpha A_2(0) e^{-\alpha(0)}$
- x. We can simplify the previous Equation and we can solve the following System of Equations for the coefficients A_1 and A_2 .
 1. $x(0) = A_1 + A_2$
 $x'(0) = -\alpha A_1 + A_2$
- e. Underdamped Response ($\alpha < \omega_0$)
 - i. This means that our Characteristic Equation has 0 Real Roots.
 1. Think of a quadratic function that never intersects the x -axis.
 - ii. The Solution to our Second-order Differential Equation is the following.
 1. $x(t) = [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] e^{-\alpha t}$
 - iii. An Underdamped circuit has a Damped Frequency ω_d .
 1. $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$
 - iv. $x(t)$ will be our Time Varying Current for a Series RLC Circuit.
 - v. $x(t)$ will be our Time Varying Voltage for a Parallel RLC Circuit.
 - vi. Even if we have the solution, that is not enough to solve for our desired function. We have A_1 and A_2 in our solution so we will need to solve for these unknown coefficients.
 - vii. To solve for the coefficients, we will need a second equation to solve. In this case, we will take time derivative of our function $x(t)$.
 - viii. This will be a little more difficult because we have 2 functions being multiplied with each other. We will use the Product Rule.
 1. If $x(t) = f(t)g(t)$, then $x'(t) = f(t)g'(t) + f'(t)g(t)$
 - ix. Using the Product Rule, we can take the time derivative of $x(t)$.
 1. $x(t) = [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] e^{-\alpha t}$
 $x'(t) = -\alpha [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] e^{-\alpha t} + \omega_d [A_2 \cos(\omega_d t) - A_1 \sin(\omega_d t)] e^{-\alpha t}$
 - x. Now that we have 2 equations and 2 unknowns, we will use the initial conditions for our given RLC Circuit. We are working with a Second-order Circuit, so we need $x(0)$ and $x'(0)$ to solve for the coefficients. Refer to (1.a-d) to find the initial values for our given RLC Circuit.
 1. $x(0) = [A_1 \cos(\omega_d(0)) + A_2 \sin(\omega_d(0))] e^{-\alpha(0)}$
 $x'(0) = -\alpha [A_1 \cos(\omega_d(0)) + A_2 \sin(\omega_d(0))] e^{-\alpha(0)} + \omega_d [A_2 \cos(\omega_d(0)) - A_1 \sin(\omega_d(0))] e^{-\alpha(0)}$
 - xi. We can simplify the previous Equation and we can solve the following System of Equations for the coefficients A_1 and A_2 .
 1. $x(0) = A_1 + A_2$
 $x'(0) = -\alpha A_1 + \omega_d A_2$